Electronic Engineering

Incorporating . . . ELECTRONICS, TELEVISION & SHORT WAVE WORLD

VOL. 21 No. 257 JULY 1949 PRICE 2/-

'AVO' ELECTRONIC TESTMETER

D.C. Volts : 2.5 mV to 10,000V. (Max. Input Resistance 111.1 MΩ)
D.C. Current : 0.25 μA to 1 amp. (150 mV. drop on all ranges)
A.C. Volts : 0.1V. to 2,500V. R.M.S. up to 1.5 Mc/s. With external diode probe 0.1V. to 250V. and up to 200 Mc/s.
A.C. Output Power : 5mW. to 5 watts in 6 different load resistances from 5 to 5,000 ohms.
Decibels : —10db. to + 20db. Zero level 50mW.
Capacitance : .0001 μF to 50μF.
Resistance : 0.2 ohms to 10 MΩ
Insulation : 0.1 MΩ to 1,000 MΩ.

Fully descriptive leaflet available on application:—

As up-to-date example of current instrument practice, developed to meet the demand for an instrument of laboratory sensitivity built in a robust and portable form, for use in conjunction with electronic and other apparatus where it is imperative that the instrument should present a negligible loading factor upon the circuit under test.

The instrument consists basically of a balanced bridge voltmeter. It incorporates many unique features and a wide set of ranges so that in operation it is as simple to use as a normal multi-range testmeter.

The thermionic circuit gives delicate galvanometer sensitivity to a robust moving coil movement. The instrument is quickly set up for any of the tests to be undertaken, a single circuit selector switch automatically removing from the circuit any voltages and controls which are not required for the test in question,

AVO

Precision Testing Instruments

THE AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO., LTD.
WINDER HOUSE • DOUGLAS STREET • LONDON, S.W.1. TELEPHONE: VICtoria 3404-9

VALVES For SPECIAL PURPOSES

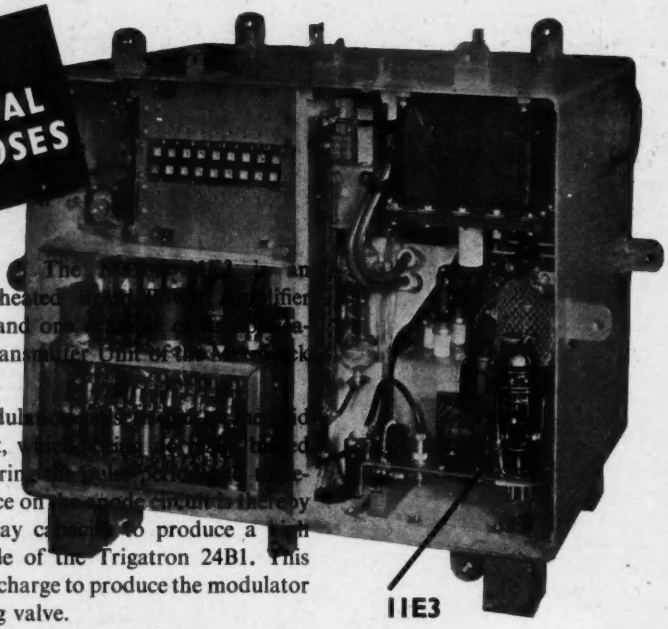

The [illegible] an indirectly heated [illegible] lifier for Pulse Amplification and o[illegible]a-tions is its use in the Modulator Trans[illegible]ck 'Seascan' Radar Equipment.

In the circuit shown a positive modul[illegible]d of the 11E3 in the transmitter unit, [illegible]d off, is caused to conduct heavily durin[illegible]e- after is cut off sharply. An inductance on [illegible] caused to "ring" with its own stray c[illegible] to produce a [illegible]h voltage pulse to the firing electrode of the Trigatron 24B1. This pulse initiates the main Trigatron discharge to produce the modulator pulse to the Magnetron transmitting valve.

The Modulator Unit also employs Mazda valves 19H1 and 24B1 and full details of these valves may be obtained on application.

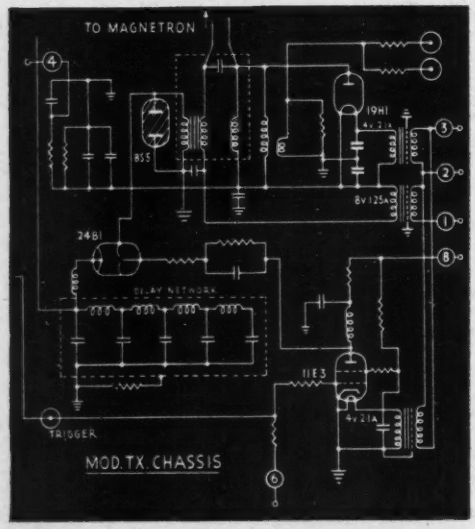

RATING:

Heater Voltage (volts)	V_h	4.2
Heater Current (amps)	I_h	2.5
Maximum Anode Voltage as Series Modulator (volts DC)	$V_{a(max)}$	3,500
Maximum Peak Anode Voltage as Break Modulator (volts)	$V_{a(pk)max}$	12,500
Maximum Screen Voltage (volts)	$V_{g2(max)}$	700
Maximum Control Grid Negative Bias (volts)	$V_{g1(max)}$	-700
Maximum Peak Cathode Current (amps)	$I_{k(pk)max}$	† 3.5
Inner μ	μ_{g1-g2}	‡ 9.0
Maximum Anode Dissipation (watts)	$W_{a(max)}$	10.0
Maximum Screen Dissipation as Series Modulator (watts)	$W_{g2(max)Series}$	0.9
Maximum Screen Dissipation as Break Modulator (watts)	$W_{g2(max)Break}$	2.0
Maximum Potential Heater/Cathode (volts DC)	$V_{h-k(max)}$	150

† Taken under Pulse Conditions of approximately 10 micro-seconds duration and 400:1 minimum off-on ratio.

‡ Taken at $V_a = 200$; $V_{g2} = 200$; $I_a = 40$ mA.

List Price £1.5.0

EDISWAN **MAZDA Radio Valves & Cathode Ray Tubes**

THE EDISON SWAN ELECTRIC CO. LTD., 155 CHARING CROSS ROAD, LONDON, W.C.2
RA136

Vacan
ments
Engag

THE
from :
Mecha
for pos
Establ
develo
Midlan
£705-£
Experi
for wo
pay as
Duties
flutter
includi
ments,
nique,
tion, co
experie
Higher
or equi
ing sub
library
fields.
to com
Write f
and Sci
London
Closing

ADMI
mental
Draugh
Mechan
Enginee
will, in
capacity
compete
salary v
and loc
£283-£5
and hav
had equ
They sh
and if ov
Higher
tions, st
and app
and dra
Admiralt
Original
applicati
London
within tw

BUSH
from ex
positions
and do
work on
duction
giving ag
required,
Ltd., Pow

THE F
Hayes, M
electro-m
or auto-p
Australia
taking re
Universit
Personnel

TECHN
or Radar,
tion and
electronic
and salar
addressed
Copper W

QUALIF
research
Experienc
Full deta
required,
17 Moorg

A

CLASSIFIED ANNOUNCEMENTS

The charge for these advertisements is twelve words or less 5/- and 4d. for every additional word. Box number 2/- extra, except in the case of advertisements in "Situations Wanted" when it is added free of charge. A remittance must accompany the advertisement. Replies to box numbers should be addressed to: Morgan Bros. (Publishers) Ltd., 28, Essex Street, Strand, London, W.C.2 and marked "Electronic Engineering." Advertisements must be received before the 10th of the month for insertion in the following issue.

OFFICIAL APPOINTMENTS

Vacancies advertised are restricted to persons or employments excepted from the provisions of the Control of Engagement Order, 1947.

THE MINISTRY OF SUPPLY invites application from: Electrical, Electronic Engineers (Ref. D6/49A); Mechanical and Aeronautical Engineers (Ref. C12/49A); for posts in the following grades at the Royal Aircraft Establishment, Farnborough, and other research and development establishments in S. England and the Midlands:—Senior Experimental Officer, salary range £705-£895. Experimental Officer £495-£645, Assistant Experimental Officer £220 (at age 18)-£460. (Rates for women are somewhat lower). Grade and starting pay assessed on age, qualifications, and experience. Duties mainly connected with aircraft structures, flutter and vibration and performance, aerodynamics, including wind tunnel work and flight testing, armaments, combustion, radio and radar, electronic technique, measurements, instruments and instrumentation, control gear, etc. Applicants should have practical experience in one of these fields and possess at least Higher National Certificate, Higher School Certificate or equivalent, in mathematics or a science or engineering subject. There are a few posts for duties on library and information work connected with the above fields. The posts are unestablished, but opportunities to compete for established posts may occur later. Write for application form, obtainable from Technical and Scientific Register (K), York House, Kingsway, London, W.C.2, quoting appropriate reference above. Closing date on 30th July, 1949.

ADMIRALTY require for services at various experimental establishments in the south of England, Draughtsmen experienced in Electrical and/or Mechanical Engineering. A knowledge of Electronic Engineering will be an advantage. Appointments will, in the first instance, be in an unestablished capacity, but there will be an early opportunity to compete for established appointments. Commencing salary will be assessed according to age, experience, and location of employment, within the range of £283-£525. Candidates must be British subjects and have served an engineering apprenticeship or had equivalent workshop experience of at least 3 years. They should possess the Ordinary National Certificate, and if over 23 years of age should normally possess the Higher National Certificate (or equivalent). Applications, stating age and details of technical qualifications and apprenticeship (or equivalents), and workshop and drawing office experience, should be sent to Admiralty (C.E.11, Room 88), Empire Hotel, Bath. Original testimonials should not be forwarded with application. Candidates required for interview (at London or Bath, whichever is nearest) will be advised within two weeks of receipt of application.

SITUATIONS VACANT

BUSH RADIO LIMITED. Applications are invited from experienced radio engineers for the following positions: (a) Development work on communications and domestic radio receivers; (b) Development work on test gear for quality control television production and laboratory use. Apply in writing only, giving age, details of experience, qualifications, salary required, etc., to the Labour Manager, Bush Radio Ltd., Power Road, Chiswick, W.4.

THE FAIREY AVIATION COMPANY LTD., Hayes, Middx., requires Engineers with experience of electro-mechanical servomechanism control circuits or auto-pilot design for Research Divisions, U.K. and Australia. Applicants should be capable of undertaking research and development work on the above. University Degree or equivalent an advantage. Apply Personnel Manager.

TECHNICIAN, with experience in Electronics, Radio or Radar, is required to assist in the design, construction and maintenance of laboratory and process control electronic instruments. Applications, giving experience and salary required, to be marked "Personal" and addressed to the Chief Metallurgist, The Yorkshire Copper Works, Ltd., Pontefract Road, Leeds.

QUALIFIED PHYSICIST required for instrument research by West London Aero Engine Manufacturers. Experience of industrial instrumentation desirable. Full details of qualifications, experience and salary required, to Box No. A.C. 551 c/o The Central News, 17 Moorgate, London, E.C.2.

RADIO ENGINEER for Technical Publications Dept., with experience of compiling service literature on Domestic Radio and Television Receivers. Applications by letter only, stating age, experience and qualifications, salary, etc., to the Personnel Manager, Bush Radio Ltd., Power Road, Chiswick, W.4.

A RESEARCH ENGINEER is required as assistant to Chief of Research in a well equipped electro-acoustic laboratory. Must have good training and experience, sound knowledge of electronics and electro magnetism, and be capable of original inventive work. First class toolroom available. Interesting work. Salary £500-£600 p.a. Write full details, age, experience, etc., Amplivox Ltd., Abbey Mfg. Estate, Alperton, Middx.

REQUIRED by a firm engaged in the development and design of telecommunication equipment near Maidenhead, Engineers having Degrees in Physics or Engineering Science, preferably with experience of electronic switching technique. Salary scale with annual increments and pension fund. Starting salary according to experience and qualifications. Apply in writing, Box 454, Dorland Advertising Ltd., 18-20, Regent Street, S.W.1.

WANTED IMMEDIATELY, Electronic Draughtsmen with at least 2/3 years' experience in diagrams, mechanical design and layout of electronic industrial and laboratory equipment; permanent positions offered in the Midlands area; salary according to qualifications and experience. Apply, quoting Ref. D6/58, to Box No. 549, E.E.

ELECTRONIC TECHNICIAN required by Oxford University laboratory to design, construct and maintain apparatus and test-gear used for research. Experience of electronics other than radio desirable. Wages according to University scale. Apply, giving full details to Box No. 550, E.E.

STANDARD TELEPHONES & CABLES, LTD. invite applications for the following situations in their Valve Works at Foots Cray, Sidcup, Kent: (1) A Technical Assistant for factory valve engineering with at least 10 years' experience of this kind of work, and having minimum academic qualifications equivalent to Higher National Certificate. (2) A fully-qualified Development Engineer with suitable Degree and having substantial experience in electron optics. (3) A Chemist with the necessary experience and qualifications for undertaking important process development studies concerning the chemistry of valve production. Good salaries will be paid to those engaged. Applications for the above situations should give full details of qualifications and experience, and be addressed to the Personnel Officer at the above address.

TECHNICAL EDITOR required to edit and prepare reports for publication. Qualifications: a good general training in electronics, with wide practical experience, marked critical faculty and ability to write good English. Acquaintance with the various printing and photographic reproduction processes would be an advantage. Applications, giving full details of experience, etc., should be sent to the Personnel Department, E.M.I. Engineering Development, Ltd., Blyth Road, Hayes, Middx.

THE United Newcastle-upon-Tyne Hospitals and King's College, University of Durham. Applications are invited for the post of Technician (Electronics) in the Section of Electroencephalography in the joint Department of Psychological Medicine, Medical School, King's College and the Royal Victoria Infirmary. Applicants must have radio or comparable experience. The technician will work under the direction of the Professor of Psychological Medicine and the Research Assistant in Electroencephalography. His work will be concerned with the maintenance of an electroencephalograph and the construction and development of related apparatus. There is considerable scope for ingenuity. Arrangements will be made for the successful candidate to attend a course of training in the more specialised side of the work. The salary will be as follows in accordance with the Medical Laboratory Technicians scale—£360 per annum, rising by £15 per annum to £435 per annum. Applications, giving age, qualifications and experience, with the name and addresses of three referees, should be sent to the undersigned within one week of the date of appearance of this advertisement. A. W. Sanderson, House Governor and Secretary, Royal Victoria Infirmary, Newcastle-upon-Tyne.

RADIO ENGINEER in Bristol-Bath area, familiar with u.s.w. transmission and reception and with C.R. tube operation, wanted to co-operate in research. Box 555, E.E.

SALES ENGINEER to initiate and expand sales of oscillographic equipment. London area. Box 554, E.E.

DRAUGHTSMAN, about 21 years old, required for electronic measuring instruments. Must be fully conversant with circuit diagrams, radio components, etc. Salary £350-£400 per annum, depending upon experience. Write, enclosing full particulars to L.M.K. Mfg. Co., Ltd., Harlequin Avenue, Great West Road, Brentford, Middx.

AN ENGINEER required for the design and construction of special purpose electronic test gear by large company in East London. Applicants should have technical education to at least Higher National standard, and previous experience of this work. State age, experience and salary required, to Box 556, E.E.

RADIO AND ELECTRONIC Development Engineers, Senior and Junior Draughtsmen, Radar Mechanics, H.F. Repairers, Radio Prototype Wireman, Inspectors, Testers, Television Service and P.A. Equipment Service Engineers, and other positions vacant: Technical Employment Agency, 179, Clapham Road, S.W.9 (BRIxton 3487).

TECHNICAL WRITERS required by well-known rapidly expanding precision engineering organisation in outer West London. Individuals who combine writing ability with adequate technical qualifications. (a) One to specialise in mechanical and electrical technical writing—practical and theoretical experience essential. (b) One to specialise in radar and electronics—practical and theoretical experience essential. Write, with full details of age, qualifications, experience and salary required to Box 558, E.E.

UNIVERSITY GRADUATES are required now, and new openings will occur during the next six months, at the Research Laboratories of the General Electric Co., Ltd., East Lane, North Wembley, Middx. Physicists, mechanical and electrical engineers, and physical chemists are needed for research and development work. Details of vacancies will be sent to applicants who write to the Personnel Officer, stating age, academic qualifications and experience. Both senior and junior graduates will be considered.

APPLICATIONS are invited from Engineering and Physics Graduates by the Research Laboratories of the General Electric Co., Ltd., East Lane, North Wembley, Middx., for work on telecommunications equipment and radio navigation aids. Details of age, academic record and experience should be sent to the Personnel Officer.

JUNIOR PHYSICISTS are required by Boots Pure Drug Co., Ltd., Nottingham, for two positions in their plant laboratory. (1) Physics Section: Candidates should possess a Degree in Physics and have had some previous experience in dust filtration problems, industrial electronics and general physical measurements. (2) Instrument Section: Candidates should possess a Degree in Physics or Engineering and have had some previous experience in industrial instrumentation. Salary in the range of £450-£550, depending on qualifications and experience. Applications to Personnel Manager, Station Street, Nottingham.

PROGRESSIVE FIRM of radio and electronic manufacturers, in N.W. London area, require Senior Design Draughtsman to take charge of Drawing Office. Experience in radio and television design essential. Apply in writing, stating experience, salary required, etc., to Box 553, E.E.

INTERESTING VACANCIES now exist for Senior, Intermediate and Junior Draughtsmen on industrial electronic equipment with large well-known engineering company in their office near Victoria Station, London. Please quote Ref. D6/59 and apply, giving full particulars to Box 552, E.E.

CABLE & WIRELESS LTD. have vacancies on technical staff for service overseas. Applications invited from men with technical and practical experience in radio communications, in possession of 1st Class P.M.G. or City and Guilds Radio/Telecommunications certificates. Good pay and prospects, permanent status after probationary period. Under 30 preferred. Apply in writing, giving full qualifications, experience, etc., to Staff Manager, Electra House, Victoria Embankment, London, W.C.2.

CLASSIFIED ANNOUNCEMENTS (Cont'd.)

RESPONSIBLE Electronic Engineer by a well-known firm in London for work on computors required. Applicant must be a graduate aged 25-35 years and experienced in the development for production of pulse circuits of all kinds; he must be able to write test specifications for, and supervise the manufacture by a contractor of unusually elaborate electronic equipment. Write, stating age, experience and salary required, to Box 551 E.E.

DRAUGHTSMAN with knowledge of circuit diagrams and mechanical design. Edgware district. Tel.: WORdsworth 4474.

ENGINEERS required for test and development work on electronic test equipment. Inter B.Sc. standard preferred. Apply Furzehill Laboratories, Ltd., Boreham Wood. ELStree 1137.

FERRANTI LTD., Moston Works, Manchester, have staff vacancies for Engineers and Scientists of all grades in connexion with long-term development work on an important radio tele-control project. (i) Development Group Leaders: To take charge of large development groups. Qualifications include a good Degree in Physics or Electrical Engineering and extensive past experience in charge of development projects. Salary according to qualifications and experience in the range £1,200-£1,600 p.a. (ii) Development Section Leaders: To take charge of sections in the above groups. Qualifications include a good Degree in Physics or Electrical Engineering or its equivalent and previous experience in any of the following fields:—radar, radio communications, microwaves, servo control, electronic circuits, etc. Salary according to qualifications and experience in the range £750-£1,200 p.a. (iii) Engineers and Scientists: Qualifications include a good Degree in Physics or Electrical Engineering or its equivalent and, preferably, some experience in the fields given in Section (ii). Salary according to age and experience in the range £400-£750 p.a. (iv) Designers and Draughtsmen: Section Leaders, Draughtsmen and Junior Draughtsmen. Preferably with previous experience in the telecommunications or allied fields. Salaries based on A.S.E.D. rates, with allowances for special qualifications and experience. The Company has a Staff Pension Scheme and will give housing assistance in special cases. Applications should be addressed to The Staff Manager, Ferranti Ltd., Hollinwood, Lancs.

RADIO—Electronics Technician required by Boots Pure Drug Co., Ltd., Nottingham, for their plant laboratory, with ability to construct, service, and trace faults in industrial electronic equipment, such as pH meters, D.C. and A.C. amplifiers and R.F. generators. Applications, stating salary required, to Personnel Manager, Station Street, Nottingham.

TECHNICAL ASSISTANT (young) required by "The Wireless Trader" Laboratory to assist with and eventually take over preparation of radio servicing information. Must be conversant with commercial radio and television practice able to convert circuit diagrams to conform to a standard style and explain technical matters clearly in writing. Sound technical knowledge essential. Applications in writing only, stating age and salary required should be addressed to the Technical Editor "The Wireless Trader" Dorset House Stamford Street London S.E.1.

SITUATIONS WANTED

RADIO ENGINEER, City and Guilds Finals, Radio Communication and Technical Electricity, old system, requires post in radio, electronics or light electrical engineering. Development and production experience Northern Area, preferably Yorkshire. Box 561, E.E.

ELECTRONIC ENGINEER, 23, B.Sc.(London), four years' experience, desires change, preferably Yorkshire. Box 564, E.E.

BUSINESS OPPORTUNITIES

OPPORTUNITY to acquire high-class Electrical Manufacturing Concern. Specialised products Plant includes moulding presses, etc. Average turnover, £3,500 per year, but capable of great expansion. Price, £3,000 a.a. (Essex area.) Box 557, E.E.

EDUCATIONAL

THE POLYTECHNIC, 309, Regent Street, W.1. Electrical Engineering Department. Head of Department: W. H. Date, B.Sc.(Eng.), M.I.E.E. Full-time day courses are provided in Electrical and Telecommunications Engineering. The courses, which extend over a period of three to four years, prepare for the Higher National Diploma and professional examinations and for the B.Sc.(Eng.), Lond. Session 1949-50 begins on September 20th, 1949. Evening courses in the above subjects and also in Radio Service Work commence on Monday, 26th September. The courses prepare for the Ordinary and Higher National Certificates and for the City and Guilds of London Institute examinations. New students will be enrolled on 21st and 22nd September, 6-8 p.m. Prospectuses may be obtained on application to the undersigned. J. C. Jones, Director of Education.

A.M.I.E.E., City and Guilds, etc., on "NO PASS—NO FEE" terms. Over 95 per cent successes. For full details of modern courses in all branches of Electrical Technology send for our 112-page handbook —FREE and post free. B.I.E.T. (Dept. 337B), 17, Stratford Place, London, W.1.

SERVICE

LOUDSPEAKER repairs, British, American, any make. Moderate prices.—Sinclair Speakers, 12, Pembroke Street, London, N.1.

RADIO MANUFACTURERS can undertake development and assembly of radio or electronic equipment. Winding shop with vacuum impregnation plant. Ample space and labour available. Box 316, E.E.

GLASSBLOWING. Scientific and Research. Capacity available. Runs or prototypes. Electronics, high vacuum, chemical apparatus, etc.—H. Stanley, 129, Lower Addiscombe Road, Croydon.

FACILITIES for the inspection by Electronic Engineers of production processes invariably results in a worthwhile time or labour saving suggestion. May we have the pleasure of an invitation to your works with such an end in view. Spencer-West, Quay Works, Great Yarmouth.

FOR SALE

WEBB'S 1948 Radio Map of World, new multi-colour printing with up-to-date call signs and fresh information; on heavy art paper, 4s. 6d., post 6d. On linen on rollers, 11s. 6d. post 9d.

IN STOCK. Rectifiers, Accumulator Chargers, Rotary Converters, P.A. Amplifiers, Mikes, Mains Transformers, Speakers of most types, Test Meters, etc. Special Transformers quoted for.—University Radio, Ltd., 22, Lisle Street, London, W.C.2. GERrard 4447.

COPPER WIRES: enamelled, tinned, Litz, cotton, silk covered. All gauges. B.A. screws, nuts, washers, soldering tags, eyelets. Ebonite and laminated Bakelite panels, tubes. Paxolin coil formers. Tufnol rod. Permanent detectors, etc. List S.A.E. Trade supplied. Post Radio Supplies, 33, Bourne Gardens, London, E.4.

ELECTRON MULTIPLIER PHOTOCELLS, gas-filled triodes and tetrodes, cold cathode tubes, position indicating mechanism etc., available from stock. Send stamp for new lists. A. McMillan, 5, Oakfield Road, Bristol, 8.

ELECTRONIC ENGINEER'S widow wishes to dispose of Televisor, complete in large superlative mahogany cabinet. 12 in. tube, 12 in. speaker. £100 or offers. Box 560, E.E.

CINE CAMERA. Technicians' 16 mm. Ensign Super, Turret, three lenses, matched finders, Thalhammer panning stand. Perfect. Documentary Cameraman needs money. Best offer buys. Box 559, E.E.

"PROC. I.R.E.," May, 1946, to April, 1949, 36 copies. Offers to Box 562, E.E.

MAGSLIPS AND SELSYNS, many types available. Selsyns up to 45 lb. per inch torque. Send for list giving full technical data on application. Hopton Radio, 1, Hopton Parade, Streatham High Road, London, S.W.16. STReatham 6165.

BUILD a Portable Radio this summer. Extremely simple switch oscillator unit with frame aerial for medium and long-wave super-het. Commercial performance. 22/6. Type M.1 from Component Dealers or send S.A.E. for details to Hobbies Division, Douglas Electronic Industries, Ltd., Brinklow, near Rugby.

TELEVISION—EHT1 transformer, 2,500V and 2V, tropicalized, no flash-over, insulation test 8,000V, guaranteed the very best, 35/-. EHT2 as above, with a 4V winding, 37/6. MT1, 275-0-275V, 80 mA, 6.3V, 5V interleaved, impregnated, unbeatable value, 16/6. Hillfields Mail Radio, 8, Burnham Road, Whitley, Coventry.

WANTED

WE WILL BUY at your price used radios, amplifiers, converters, test meters, motors, pick-ups, speakers, etc.,radio and electrical accessories. Write, phone or call, University Radio Ltd., 22, Lisle Street, London, W.C.2. GERrard 4447.

CARRIER TELEPHONE and Telegraph Equipment of all types in any condition wanted; also Teleprinter or Teletypewriter apparatus. Harris and Gillow, 93, Wardour Street, W.1.

WANTED. Six Valves, American type 8020 high voltage vacuum rectifier. Box 563, E.E.

MISCELLANEOUS

£25 REWARD. Stolen 13th/14th May at B.I.F., Olympia, Airmec Telecom Master Station serial 1030 and two Electronic Test Equipments, serials 1031 and 1067. Frank Brown & Co., 79, Bishopsgate, E.C.2, will pay the above reward to the first person giving them information leading to the conviction of the thief and recovery of the property intact or pro rata.

COLE-BERNARD Ltd. would like to notify their many clients of a change in address. All communications regarding amplifiers, etc., should be addressed to Cole-Bernard Productions Ltd., 12, Chelverton Road, London, S.W.15.

FESTIVAL OF BRITAIN. The Council of Industrial Design have opened a 1951 Stock List to which they invite manufacturers to send photographs or drawings of their best products. Address to Stock List, Council of Industrial Design, Tilbury House, Petty France, London, S.W.1.

LINE OUTPUT TRANSFORMERS and FOCUS COILS
from stock, tested and approved for use in
Electronic Engineering Televisor
36/- each
WALPOLE NORMAN ENGINEERING Co. Ltd.
33, Montpelier Vale,
Blackheath, London, S.E.3.

SHEET METAL CASES
accurately made and finely finished
We cannot supply 100,000, but if you want
1, or
100, or
1000, or more,
please contact—
CLEVELAND ART METAL WORKS
Architectural Metal Workers and Engineers
23 & 23a, Martimer Märket, Tottenham Court Road, LONDON, W.C.1
Tel.: EUSton 4169

INDEX TO ADVERTISERS
SEE **PAGE 32**

Can *anyone* use TUFNOL?

As a material Tufnol asks no favours. Using the same tools as for metal, it can be machined accurately and quickly. The pre-fabricated forms, tubes, bars, rods and channels may help reduce your production costs. Tufnol is also supplied in sheets or specially moulded shapes.

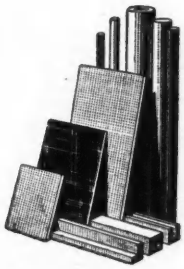

The uses of Tufnol are legion. It presents a valuable combination of chemical resisting, electrical insulating and mechanical qualities. Where a material is required to withstand moisture and corrosion or extremes of climate, to mate with metals yet have long life to resist tensile, shear, and impact stresses — there you will find Tufnol giving unfailing service.

Are your competitors using Tufnol?

FOR YOUR INFORMATION

Data already collected in the various Tufnol Publications may prove of use to you. If your problem is a NEW one, our Technical Staff will co-operate enthusiastically. Why not write TODAY?

TUFNOL
REGISTERED TRADE MARK
An ELLISON Product

TUFNOL LTD · PERRY BARR · BIRMINGHAM · 22B

232

PHOTO-ELECTRIC RELAY

for "ON" or "OFF" control of ELECTRIC POWER

The standard relay is extremely sensitive and responds to the incidence or interruption of a beam of light, the intensity of which may be as low as 1-Foot candle and the duration as short as one-tenth of a second.

Applications to industrial processes include :—

Control of temperature, liquid level, lighting, register, dimensions, weighing, counting, etc. ; also alarm devices.

Delivery from stock

ACTUATED BY LIGHT

BRITISH THOMSON-HOUSTON

THE BRITISH THOMSON-HOUSTON COMPANY LIMITED · RUGBY · ENGLAND

A3854

EDISWAN
LOW FREQUENCY OSCILLATOR
TYPE R 666

★ VERY LOW FREQUENCIES
★ HIGH STABILITY
★ WIDE RANGE
★ PURE WAVEFORM
★ PUSH-PULL OUTPUT
★ FREQUENCY INCREMENT SWITCH
★ CONSTANT OUTPUT VOLTAGE
★ OUTPUT ATTENUATOR
★ COMPACT AND PORTABLE
★ STANDARD RACK MOUNTING

THIS is a much-needed oscillator designed specifically for testing, calibration and set-up of biological amplifiers and recorders, strain and vibration recorders, and low frequency wave analysers.

It has a resistance/capacity circuit of special design with automatic amplitude control to ensure constant output and good waveform at frequencies from 1.1 to 5,000 c.p.s. The circuit is remarkably free from trouble associated with change of valve characteristics, ensuring that accuracy is dependent only upon the frequency selective network components.

An incremental frequency switch is included specifically for the measurement of 'Q' in frequency selective circuits of filters or wave analysers.

Further details will be given on request.

EDISWAN

THE EDISON SWAN ELECTRIC CO. LTD., 155 CHARING CROSS ROAD, LONDON, W.C.2
RA.116

4 NEW PUBLICATIONS

. . . each of importance in its own sphere—ALL of importance to radio and television engineers.

They contain useful technical information on the latest developments in B.I.C.C. Radio Connecting Wires (No. 247R), Television Downlead Cables (No. 244R), Microphone and Loudspeaker Cables (No. 245R) and Copper Earth Rods for Radio (No. 243R).

Write to-day for a free copy of the Publication you need.

B.I. Callender's

RADIO EQUIPMENT

BRITISH INSULATED CALLENDER'S CABLES LIMITED
NORFOLK HOUSE, NORFOLK STREET, LONDON, W.C.2

THE "BELLING-LEE" PAGE

Providing technical information, service and advice in relation to our products, and the suppression of electrical interference

The Siting of Aerials

We claim that "Belling-Lee" television aerials are mechanically and electrically superior, but if erected without due regard to local interference, and/or the proximity of a corrugated iron shed or gas holder, then the "Belling-Lee" best is no better than the cheapest worst.

No aerial is a "cure-all," some are made better than others, stand up to the weather, without leaning away from the prevailing winds, etc. Some have had superior electrical knowledge built into them, which tells when used in fringe areas.

We consider it bad practice to recommend the most expensive aerial of a range when a cheaper model will suffice.

Both the "H" type*1 and the "Veerod"*2 (inverted "V") are, in their own way, ideal for the elimination of interference; the "H" is the most expensive in our range and the "Veerod" one of the cheapest.

We have seen an announcement in a Midland paper to the effect that it is not possible to know what will be the best television aerial to erect on a site until the Midland Transmitter is on the air. "Belling-Lee" have put up many hundreds of aerials for the Midland Transmitter and many hundreds more have been erected by worthy competitors. If the installations are entrusted to recognised firms with plenty of experience of this work in London and the home counties, then there is no need to worry.

If, however, someone without the necessary experience puts up a television aerial, then there may be trouble from double images or "ghosts," or the obvious local source of interference may be ignored and consequently the wrong type of aerial installed. To take a case in point, the "Belling-Lee" "Veerod" has sharp minima at right angles to the direction in which it is pointing, whereas the "H" type has a minimum behind the dipole: one experienced in these matters makes full use of such characteristics for the removal of "ghosts" or interference. Again, sometimes it is advantageous to use the building on which the erection is being carried out to screen the dipole from obvious interference such as a busy cross road and in other cases height is the most important thing. Experience of hundreds of such cases is most useful. The average wireless dealer will not make mistakes that he cannot rectify when the time comes.

A "Viewrod" 'H' type aerial

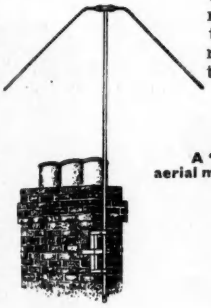

A "Veerod" television aerial mounted on a chimney

Hum in the Receiver

We have heard a lot about humming aerials, and we have cured this trouble, but we have recently had a number of requests to cure hum in the receiver. Now, this is a form of interference that we do not claim to cure. The hum is a low frequency phenomenon which may be mains borne on D.C. mains or an inherent property of the receiver itself.

Our interests are in radio frequency interference which, as readers of this page know show up on the picture of a television receiver as "ghosts," spots, feathering, or bars, and on the sound channel, or on broadcast receivers as crackles, plops, bangs and sizzling noises which may be eliminated from the receiver by the use of one or more of the following methods:

1. Correct choice and siting of an outdoor aerial.
2. For broadcast reception, an anti-interference aerial.*3
3. Fitting a mains filter.*4

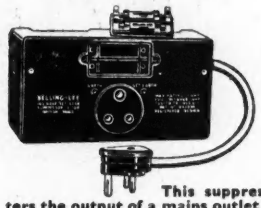

This suppressor filters the output of a mains outlet socket. List No. L300/3 1 amp.

Wires that carry and re-radiate Interference

We have recently been asked to confirm whether or not "wires used for wired wireless" radiated interference. The answer is that they can and do. So do telephone wires, and overhead fire alarm wires, but, of course, the worst offenders are overhead mains, in villages where the houses are wired with V.I.R. taken in at roof level.

*1 "Viewrod" television aerials for Midland frequencies. L652/LM "H" type with 8 ft. light alloy mast and chimney lashings. £6 5s.

L652/C "H" type with mast-head cap for customers' own wooden mast. £2 17s. 6d.

L652/L "H" type with mast-head cap and chimney lashings (less mast). £5 7s. 6d.

The London equivalents for items 2 and 3 are L502/C £4 8s. L502/L £6 6s.

*2 "Veerod" television aerial. Attic mounting. L605 London £2 12s. 6d. L646 Midland £2 5s.

"Veerod" chimney mounting with metal mast. L606 London. £4 10s. L635 Midland £4 2s. 6d.

*3 "Skyrod" vertical collector with "Eliminoise" anti-interference transformers and cable. L638/K Chimney mounting. £10. L638/CK Mast mounting (less mast). £8 15s.

L308/K "Eliminoise" kit with 60 ft. wire span and cable, etc. Complete, £6 6s.

*4 Set lead suppressors L300/3 (1 amp) £2 19s. 6d. L305 (2 amp). Sometimes suitable for television. £3 3s.

BELLING & LEE LTD
CAMBRIDGE ARTERIAL RD., ENFIELD, MIDDX., ENGLAND

60 'CINTEL' Photo-Electric Cells

The most comprehensive range of Cells in the World...

Available with three types of cathode surfaces :—

TYPE A—Antimony-Caesium. (British Patent No. 522.752 1938). Sensitive to blue light and daylight.

TYPE B—Bismuth etc.—Caesium. Sensitivity similar to human eye.

TYPE S—Silver-Oxygen-Caesium. Red-infra-red sensitive.

Cells for use in the ultra violet region of the spectrum • Cells of high insulation, linearity and stability for accurate photometric work • American type equivalents • Push-Pull types for double sound tracks • Special cells for dye image sound tracks, multipliers, etc. *Please write for catalogue.*

Sixty different types of Photo-Electric Cells

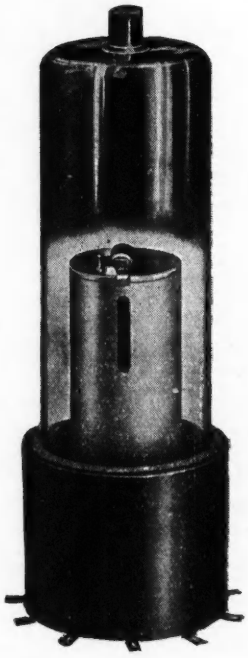

—from miniature to multiplier—

CINTEL

Registered Trade Mark

FOREMOST IN THE MANUFACTURE OF

- COUNTERS & CHRONOMETERS
- METAL DETECTORS
- OSCILLOSCOPES
- PHOTO-ELECTRIC CELLS
- CATHODE RAY TUBES
- GEIGER-MULLER TUBES
- ELECTRONIC INSTRUMENTS

CINEMA-TELEVISION LIMITED

WORSLEY BRIDGE ROAD, LONDON, S.E.26

Telephone: HITher Green 4600

WIDE-RANGE TRANSFORMERS

TYPES D-106 & D-139

For Modern Communications Equipment

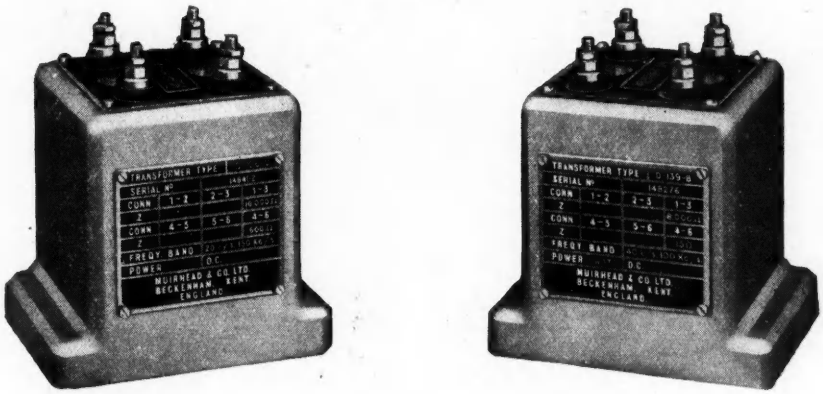

FREQUENCY CHARACTERISTICS
Practically linear from the lower audio frequencies to over 100 kc/s. (See representative curves)

IMPEDANCE RATIOS: Many impedance ratios are available, from 1 : 1 to 500 : 1.

POWER: Types D-139 will handle up to one watt AC power above 40 c/s. Types D-106 are designed as input and interstage transformers where the power is negligible.

SCREENING: Inner case—nickel-iron. Outer case—cast aluminium.

DIMENSIONS: $2\frac{5}{8}'' \times 3\frac{1}{2}'' \times 3''$ high overall. **WEIGHT:** $2\frac{1}{2}$ lb.

Full information is given in Bulletin B-538-C which will gladly be sent on request.

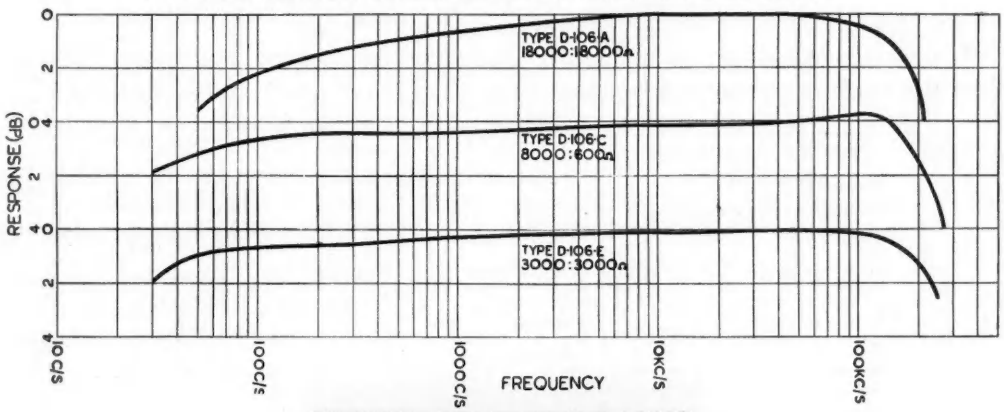

MUIRHEAD

Muirhead & Co. Limited, Elmers End, Beckenham, Kent. Tel. Beckenham 0041-2

FOR OVER 60 YEARS DESIGNERS & MAKERS OF PRECISION INSTRUMENTS

B

C.R.C.391

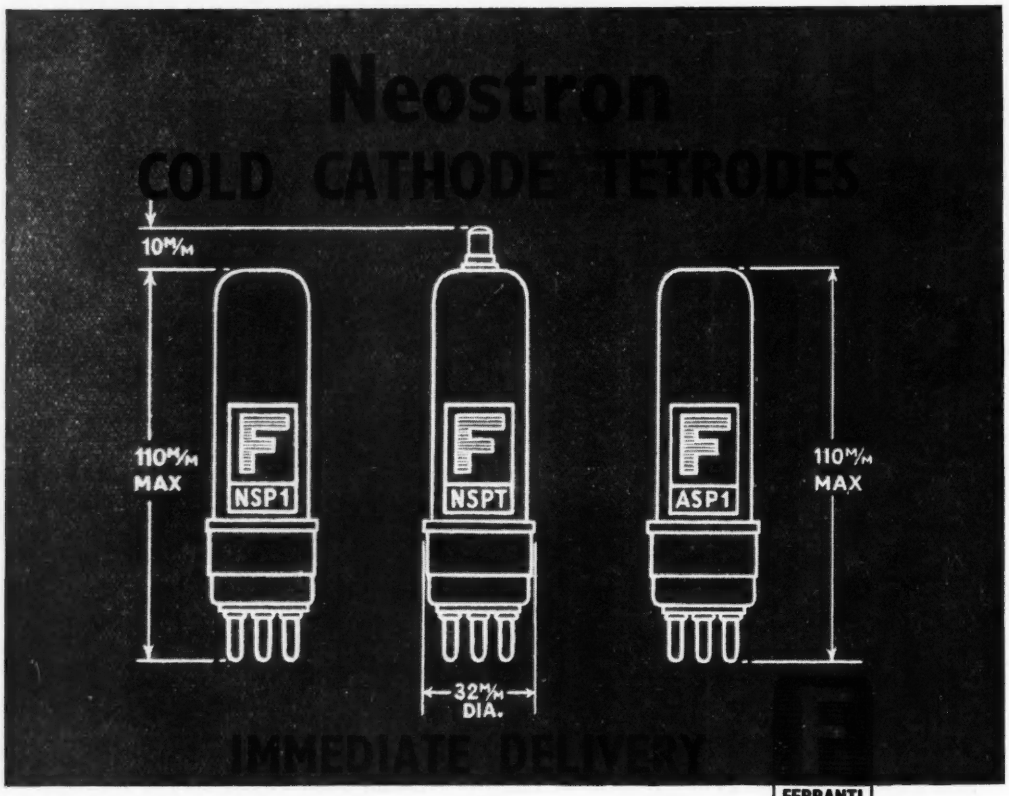

The Ferranti Neostron is a cold cathode tetrode filled with neon, designed for use as a stroboscopic light source, a flashing indicator, or an electronic relay.

The discharge in the anode is started by initiating a glow discharge between the screen and grid electrodes, the screen being at a fixed positive bias, a negative impulse being applied to the grid.

Operating Characteristics	NSP1	NSPT	ASP1
Max. Anode Voltage	400	650	400
Normal Anode Voltage	300	600	300
Mean Anode Current	40-100* mA	40-100* mA	40-100* mA
Peak Anode Current	250 Amps.	250 Amps.	250 Amps.
Max. Operating Frequency	250 c.p.s.	250 c.p.s.	300 c.p.s.
Anode Connection	in base	Top cap	in base
Gas Filling	Neon	Neon	Argon

**Dependent upon frequency of operation*

All types can be supplied with English 4 pin or American 4 pin bases.

FERRANTI LTD ELECTRONICS DEPT. MOSTON MANCHESTER 10

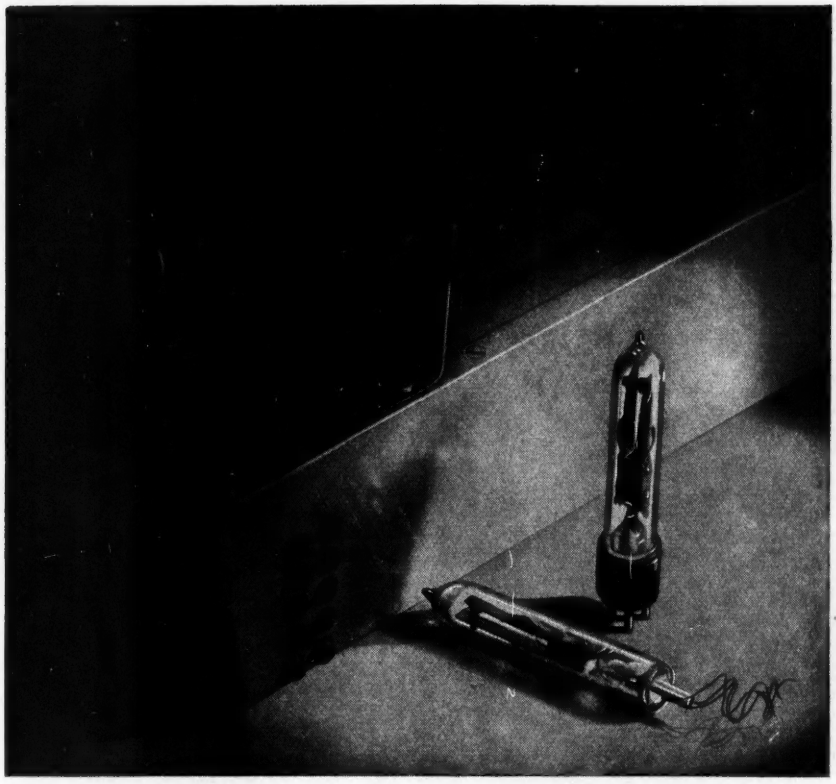

SUNVIC

MINIATURE TIME-DELAY SWITCHES

Reliable, compact, bimetal switches, glass-sealed and evacuated, to operate after a time-delay (such as may be needed to allow valve-filaments to heat-up). The switch operates on 6.3 volts and switches in a maximum of 1 amp. at up to 380 volts AC or 600 volts DC. Time-delay 25 to 100 seconds. Available unmounted (Type 2TQV) or with English miniature 4-pin base (Type 2TQVM). For full specification please write for Publication TV10/16. Other time-delay switches, Publication MS10/16.

SUNVIC CONTROLS LTD.

10 ESSEX STREET, STRAND, LONDON, W.C.2.

TAS/SCI93

CERAMICS

FOR RESISTORS
and all radio components
FREQUENTITE – FARADEX – TEMPRADEX

STEATITE & PORCELAIN PRODUCTS LTD.

Stourport on Severn, Worcester Telephone: Stourport 111 Telegrams: Steatain, Stourport

S.P.50

Why we designed the

STEREOPHONIC AMPLIFIER

In our search for really high quality we had already built an amplifier of 0.01 per cent distortion and 40 times damping factor, which we believe is the finest straight amplifier in the world. Unfortunately we have been unable to obtain a single speaker which will faithfully reproduce the whole range, and when used to drive twin speakers via a cross-over network these introduced more distortion and peaks than could be tolerated. From this we drew the following conclusions.

The attainment of really high quality had always been marred by defects at the speaker end of the reproducer, which were :—

(*a*) The inability to cover the whole audio range with handling capacity of 8 to 10 watts at the lowest piano frequency of 26 cycles.

(*b*) The interference caused by the Doppler effect, or where this has been minimised, the lack of speech coil feedback and damping at frequencies where that particular speaker should be silent.

(*c*) The variation in acoustic power at the ends of the audio band, or the difference in efficiency of the two speakers when fed by cross-overs after the amplifier.

(*d*) The resonance of the choke and capacitor network at various frequencies which in one case gave a variation of 5 ohms to 105 ohms for a nominal 15 ohms impedance.

All these points were considered, and an amplifier was then designed and built to overcome all these deficiencies, the audible results exceeded expectations and a stereophonic effect was noticed on some records and the amplifier accordingly called " Stereophonic."

The requirements of triode cathode follower and 8 to 10 watts output is best met by PX4's, since their mains consumption is low compared to pentodes strapped as triodes and heater hum does not bother a cathode follower. A single valve is capable of the equivalent acoustic requirements at the higher frequencies. The cross-over is fitted in the middle of the amplifier where it is not concerned with power transfer and does not introduce resonance or distortion.

Superlatives fail in the description of the quality of reproduction from this new amplifier, but may we just say it gives the finest quality reproduction of any unit, some costing almost a thousand pounds, that we and many others have heard. This is due to the lack of resonances from the loudspeakers, with the result that needle scratch is barely audible, even with the full audible frequency range.

Unlike most reproducers where bass is reduced to ensure good unmodulated treble it is possible in this case to retain the full richness of the bass without interfering in any way with the treble response, and the lowest organ note to the highest strings can be reproduced at the same time without modulation distortion. This high quality is maintained even at whisper strength to an abnormal degree.

In these few words we cannot convey just how good this quality of reproduction really is, but we do invite you to a demonstration, and if possible bring your own well-known test records, upon which to base your judgment.

Chassis complete with valves

Price 36½ gns.

VORTEXION LIMITED, 257-261 THE BROADWAY, WIMBLEDON, LONDON, S.W.19

Telephones: LIB 2814 and 6242-3 **Telegrams: " Vortexion, Wimble, London "**

CLIX

A 'FLUON' INSULATED VALVEHOLDER

Fluon is non-hygroscopic
Fluon is chemically inert
Fluon has high dielectric qualities
Fluon can be moulded to extremely close tolerances
Fluon resists temperature as high as 250°c
Beryllium copper, silver plated contac
Fluon has high impact resist

Typical of Clix leadership is their Fluon insulated valveholder—the only one of its kind which effectively meets the stringent requirements of the B.7.G. glass based valves. Its exceptionally close dimensional tolerances made possible by the Clix method of moulding the Polytetrafluoroethylene insulation entirely obviates the necessity of wiring jigs for making solder connections.

The Silver plated Beryllium Copper Contacts are specially designed to require only a small amount of distention when the pins are inserted to produce a good electrical connection. Undesirable capacities and inductances are reduced to a minimum yet the flashover gap is increased. Valve breakage through misalignment is avoided.

We manufacture a wide range of components for the Radio, Electronics and Television industries. In addition to Stock lines, a few of which are illustrated below, we can also manufacture special components designed for individual specifications.

THE CLIX B.7.G. (Button Base) VALVE HOLDER

With Fluon (P.T.F.E.) Insulation with or without skirt and screening can. Made to meet the most exacting conditions required in all types of Radio, Radar, Television, Inter-Communication and Electronic Equipment.

FROM THE WIDE RANGE OF CLIX COMPONENTS

5-pin English Valve Holder. Other types are available for most British and American Valves.

Clix "Flexipin" Radio Master Plug supplied in a Range of colours: for ¼ in. 4 m.m. or 3/16ths in. Sockets.

Tag Strips. Types are available with from 1 to 9 Tags. Tropical or Commercial Grade, in various combinations, also Miniature types.

Clix Heavy Duty Spade terminals. Other types available to cover terminal diameters of from 3/16ths in. — 19/64ths in. Black and Red only.

4-way Voltage Selector Panel with solid or fused shorting Plug, 3-way also available with Rectangle or Circular Plate.

Panel-Mounting Sockets can be supplied in sizes for ¼ in.—3/16ths in. Plugs with or without Insulator.

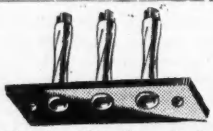

Chassis-Mounting Socket Strips with from 2—6 Sockets in various standard markings or to Customers' needs.

Coil-pin or Resilient Plug made in 3 sizes ¼ in.—3/16ths in. all complete with two nuts.

BRITISH MECHANICAL PRODUCTIONS LIMITED

(in association with General Accessories Ltd.)

21 BRUTON STREET • LONDON • W.1

Room for a little 'un

A mass of resistances, wires and condensers — how do you squeeze a switch in there? We'll tell you. Use our Type B.T. switch. It has been specially designed for small spaces and simple switching. You'll find it a godsend. It's an even better switch too since it has had an overhaul in our Development Section. Here are some improvements we have made to it:

The contact blades are fixed in a new way. This makes them rigid all the time.

The drive spindle is positioned definitely in the wafer. This provides double bearing.

Steady contact resistance.

Improved insulation between contacts.

Positive contact.

Self-cleaning action.

All these help to make the Type B.T. an efficient and lasting switch. Why not try it?

WALTER SWITCHES—MADE FOR LIFE

Walter Instruments
LIMITED

GARTH ROAD, LOWER MORDEN, SURREY. Telephone: DERWENT 4421-2-3

CRC46

FOR ALL ELECTRONIC APPLICATIONS

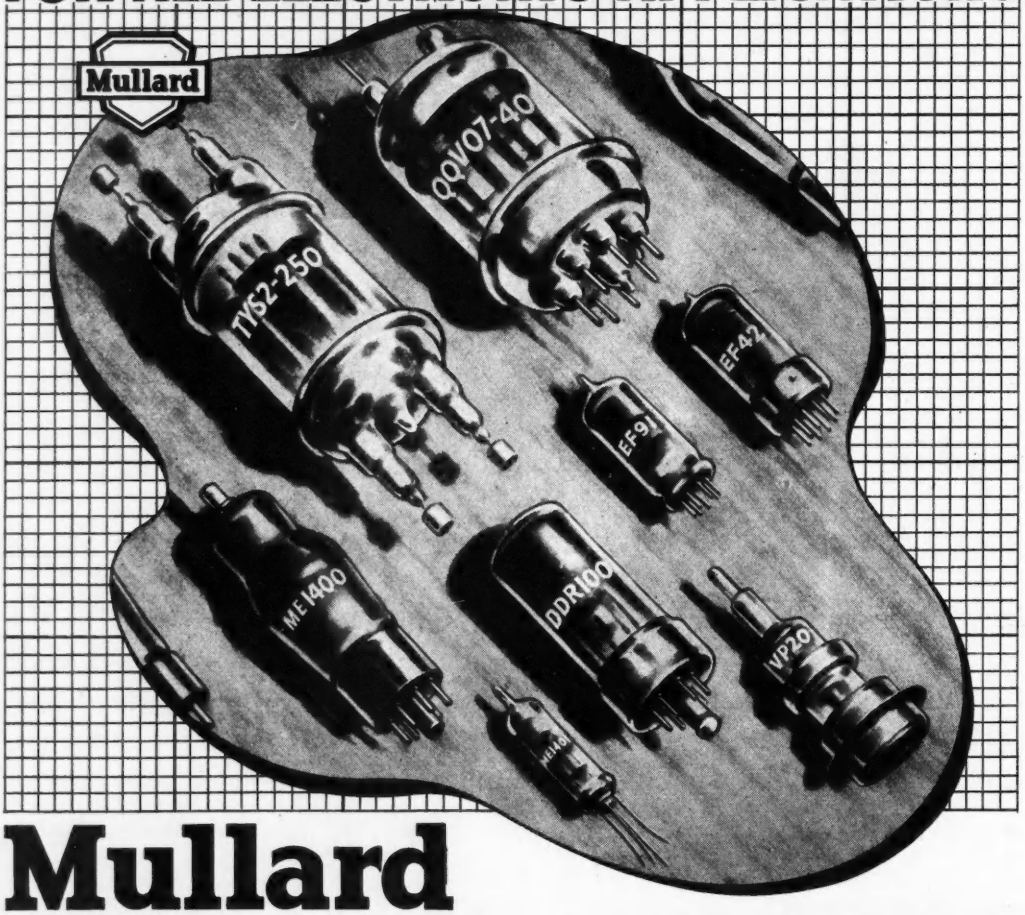

Mullard

THERMIONIC VALVES & ELECTRON TUBES

Mullard
NEWS LETTER
If you are not already receiving this service of advance information on new valves, please ask to be added to the mailing list.

INDUSTRIAL POWER VALVES, INDUSTRIAL RECTIFIERS, THYRATRONS, PHOTOCELLS, ELECTRONIC PHOTO FLASH TUBES, ACCELEROMETERS, CATHODE RAY TUBES, STABILISERS AND VOLTAGE REFERENCE TUBES, COLD CATHODE TUBES, ELECTROMETERS, V.H.F. AND OTHER VALVES FOR COMMUNICATIONS, GENERAL PURPOSE VALVES.

When in Glasgow please visit our permanent exhibit at the Engineering Centre.

MULLARD ELECTRONIC PRODUCTS LIMITED, CENTURY HOUSE, SHAFTESBURY AVENUE, LONDON, W.C.2
MVT 55

Electronic Engineering

EDITORIAL, ADVERTISING AND PUBLISHING OFFICES, 28, ESSEX STREET, STRAND, W.C.2.

TELEPHONE: CENTRAL 6565 (10 LINES) *EDITOR:* H. G. FOSTER, M.Sc., M.I.E.E. *TELEGRAMS:* LECTRONING, ESTRAND, LONDON

Monthly (published last Friday of preceding month) 2/- net. Subscription Rate: Post Paid 12 months 26/-.

Vol. 21. No. 257 July, 1949

CONTENTS

A Magnetic Digital Storage System 234
By Andrew D. Booth, Ph.D.

A High Voltage Ring Modulator 239
By M. Tucker

Voltage Stabilisers—Part 3 243
By F. A. Benson, M.Eng., A.M.I.E.E.

A New Visual Null Indicator 248
By Major E. H. Banner, M.Sc., M.I.E.E., F.Inst.P.

Projective Three-dimensional Displays—Part I 249
By D. M. MacKay, B.Sc., A.Inst.P.

The Electromagnetic Horn—Part I 255
By W. D. Oliphant

Panoramic Display—Design Considerations ... 259
By Donald W. Thomasson

Magnetron Awards 262

Notes from the Industry 263

Electronic Equipment 264

Book Reviews 266

Made in America 269

Correspondence 270

Decline and Fall

IN the April issue of our American contemporary *Electronics* there appeared a message from James McGraw, President of the McGraw Hill Publishing Co. Inc., to American Industry entitled "Now is the time to fight Socialism in Washington." This apostrophe was continued in the May issue and has as its theme "the rapid progress down the dreary road of industrial stagnation" (to quote from Mr. McGraw) of British Industry due, in the main, to the pre-war short-sightedness of our Industrialists and to bad planning of our Socialists since 1945.

All this, of course, may make good material for the American reader, but such statements can be dismissed as generalisations, and like all generalisations, they are false and misleading.

While we do not claim that British industry has a monopoly of all the virtues, neither has it a monopoly of all the vices.

We admit that Britain's industrial and economic position is perilous and that without American help in the form of Marshall Aid we should be "in the red," but without penetrating the arcana of present-day economics and politics, we should like to be permitted to say a word or two about British Industry in reply. On the material side there is much replanning and rebuilding to be done before Britain can regain her economic independence, and on the human side among employer and employed alike there is a sense of frustration and lack of enterprise which is more frequently referred to as lack of incentive.

Although not qualified to speak for British Industry as a whole, we should have said that there are in it still some very bright spots. There does not, for example, appear to be anything wrong with the shipbuilding industry, and the Austin "A90" has already given its message from the motor industry.

In the Electronic industry, of which we can claim to have intimate knowledge, there is ample evidence that it is live and active, and the industry which leads the world in television, which has produced such notable "firsts" as the Magnetron and Radar, is showing no signs of decay.

To the foreigner our methods often appear tortuous and tempo seems to be in keeping with the notice bearing the words "Dead Slow" which appears at the entrance to Somerset House in the Strand, but this is illusory; Britain has no need yet for a Gibbons.

A Magnetic Digital Storage System

By ANDREW D. BOOTH, Ph.D.*

DESCRIPTIONS have appeared[1,2] of storage devices for use in serial operation calculating machines, but in this country at least, little emphasis has been placed on the other possible type of computing system, namely, that employing parallel operation. It is not proposed to give any discussion of computing machines in this paper but for completeness it must be stated that in serial operation machines the digits of a number become available, and are used, one at a time starting usually from the least significant, whereas in a parallel operation machine all the digits of any number become available at the same time.

Without wishing to become controversial, it may be remarked that von Neumann, who was the originator of many of the current ideas on calculating machines, has abandoned the serial operation machine in favour of its parallel operation counterpart.

Requirements for a Storage Device

In either type of calculating machine the requirements of the storage device are similar, and are as follows:

(1) The storage should be permanent if desired.

(2) The contents of any position must be erasible at will and capable of replacement by new data.

(3) The volumetric efficiency should be high.

(4) The access and replacement time of stored data should be small.

The delay line storage device of Wilkes[1] and the cathode-ray tube memory of Williams[2] satisfy all of the above requirements except (1) and to a less extent (3). Either of these devices loses all its stored data if a power supply failure occurs. In addition, in the forms described by the authors, neither is directly suitable for a parallel operation machine.

The idea of using the well known principles of magnetic sound recording for the storage of digital data seems to have occurred to a number of designers at about the same time, the system to be described in this paper, however, is thought to be the first in actual operation.

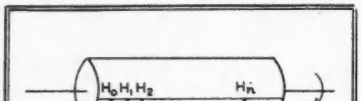

Fig. 1. Magnetic drum and read/record heads

Fig. 2. Magnetic state of clock pulse track

Principles of the Magnetic Memory

Essentially, the storage device consists of a cylindrical drum coated with permanent magnetic material and rotating under a series of read/record heads arranged along a generator of the cylinder. In Fig. 1 H_1-H_n are a set of these heads.

All of the digits of any particular number, which is in binary form (*e.g.*, Wilkes[1]), are recorded and read off simultaneously by the heads.

Successive numbers are recorded in sequence as the drum rotates and to distinguish between them an extra track (H_0) is added which contains a set of equispaced positive "clock" pulses.

In order to determine the position of the first number it is necessary to indicate the start of this clock pulse track. This could be done in various ways; for example, it might start with a single negative pulse, or alternatively a separate track might contain a single pulse to indicate the zero position of the clock pulse track. In fact, it turns out to be much simpler to leave a small gap, clear of any pulses, at the end of the clock pulse track, and to use this as a zero indication. The general appearance of the magnetic state of the clock pulse track is then shown in Fig. 2.

In order to go to any position on the drum and to read or record there, all that is necessary is to count from the zero position on the clock track and to arrange that the counter emits a pulse when it reaches the given position. A schematic diagram of the whole memory is given in Fig. 3.

The positive pulse input from the clock track head is amplified and sent to the binary counter C, which is arranged to zero on receipt of a pulse from the shaping circuit contained in A_0.

The contents of C are compared with the required memory location as shown by a set of position number inputs; when the two numbers

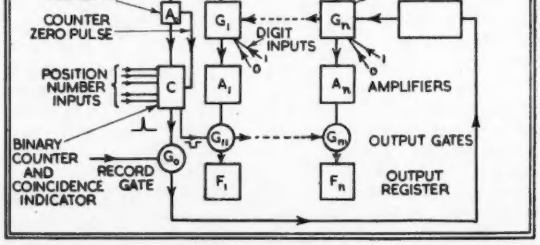

Fig. 3. Schematic of magnetic storage

* Director, Birkbeck College Electronic Computer Project, Visiting Professor of Physics, University of Pittsburgh, U.S.A.

agree a pulse is emitted by a circuit. Normally this pulse opens a set of gates G_{11}-G_{n1}, which allow the output pulses from the digit track heads H_1-H_n to set a series of flip-flop storage elements F_1-F_n to the digit pattern recorded under the heads in the given position. When it is desired to record in a given position a gate G_0 allows the above coincidence pulse to trigger a "record pulse" generator which sends either positive ("1") or negative ("0") pulses, via the input gates G_1-G_n, to the heads. It should be noted that prior to the record operation the input gate will have been set to "0" or "1" positions from digit input leads, and that the nature of the storage is such that the input data automatically erases that already present.

In the present memory, intended for use with A.R.C. (Automatic Relay Computer), the input gates G_1-G_n, the record gate G_0 and part of the counter-coincidence circuit are relay elements, and the output flip-flops set relays to operate the remainder of the machine.

The Magnetic Circuit

While many highly specialised magnetic recording media exist, these are at present difficult to obtain in suitable form, and it was decided to use a thin plating of electrolytic nickel. Although the magnetic properties of this seem to leave much to be desired, the medium is quite good enough for the purpose in hand. In the final design a plated layer between .0005 in. and .001 in. in thickness was used. Extensive experiments showed that up to 100 digits/in. could be recorded, but for safety it was decided to use only a 50 digits/in. packing as this allowed for considerable variations in head construction. The surface speed of the drum was 25 ft./sec.

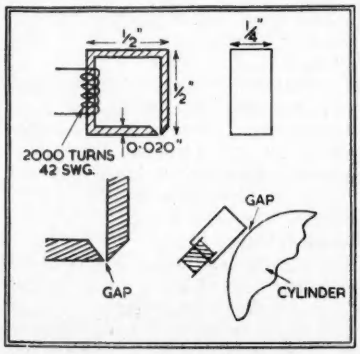

Fig. 4. Early recording head

The first models of the recording heads were of the form shown in Fig. 4.

Single laminations of .020 in. silicon iron were used and the heads were run in contact with the cylinder as shown. Using 2,000 turns on the magnetising coils it was found that the shortest recording pulse which could be used was 35 μsec. This left much to be desired and further experiments were instituted.

About this time Dr. Julian Bigelow* suggested using a single, very fine wire as recording head.

This was to be mounted in close proximity to the drum surface and pulsed with a current of between 10 and 50 amps. Since the current flows for considerably less than 1 μsec. this does not damage the wire. It can be shown that if the input pulse is short enough for the recording medium not to move appeciably during the pulse, the output voltage follows the law:

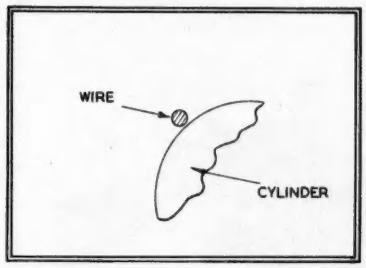

Fig. 5. Single wire head

Fig. 6. Output voltage from single wire head

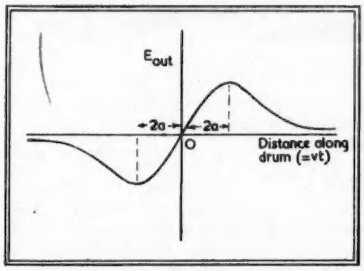

$$E_{out} = K v^2 i t / (4a^2 + v^2 t^2)$$

where

v = surface speed of medium
i = recording current
a = distance of wire centre from drum surface
t = time.

The general form of this function is shown in Fig. 6.

In the present memory, with digit packing of 50 in., it follows that for non-interference of pulses $4a << .020$ in. or $a << .005$ in.; this means that wires of diameter less than .002 in. must be used. Handling becomes difficult with .001 in. diameter wire and problems arise in the design of step-up transformers for ratio of 1:100 and bandwidths of 250 Kc/s. where the input impedance is about 1Ω.

As a comparison, tests were made using a .002 in. diameter single wire and a single lamination head of the general type shown in Fig. 4, but reduced to one-half the linear dimensions. With ten turns this gave precisely the same output as the single wire, thus indicating losses of about 90 per cent.

It had been evident that the performance improved as the linear dimensions of the heads decreased and a series of experiments were tried with very small heads. These resulted in the design shown in Fig. 7.

Using a single 32-gauge wire as magnetising source, the output signal was three times greater than that from a .001 in. diameter wire, indicating that the loss in efficiency is no longer important. With the same design it proved possible to insert four turns of 42-gauge wire through the window and 12 times the single wire head output was obtained. The output pulse shape is identical with that of Fig. 6.

In order to record "1" and "0" on the medium the simple procedure of pulsing the head with sufficient current to cause magnetic saturation of the nickel was adopted. Thus, if "1" is recorded with a pulse of +20 amps., to record "0" a −20 amp. pulse is superimposed.

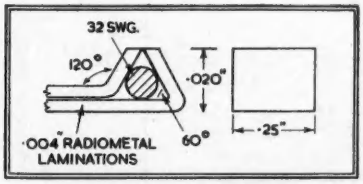

Fig. 7. Final head design

* Chief Engineer, Electronic Computer Project, Institute for Advanced Study, Princeton, U.S.A.

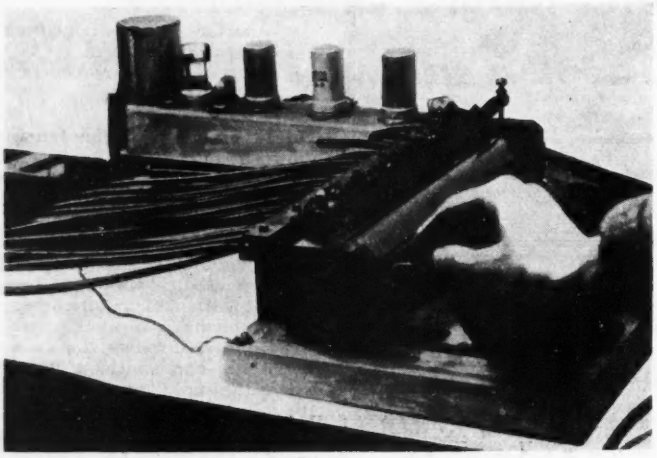

Fig. 8. Model of drum with heads mounted in position

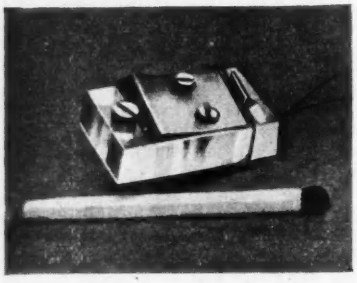

Fig. 9. One of the final read/record heads

Mechanical Construction

A photograph of the cylinder and head assembly is given in Fig. 8.

For mathematical reasons it was decided to have 21 binary digit numbers and to store 256 such quantities. With the packing of 50 digits/in. and surface speed of 25 ft./sec., this resulted in a cylinder 2 in. in diameter and 12 in. long rotating at 3,000 r.p.m. The maximum waiting time for reading or recording is 20 m.sec. and the mean time 10 m.sec.

The heads, shown in detail in Fig. 9, are mounted on a brass bar and are individually adjustable by means of a simple screw assembly. Coarse adjustment is provided for aligning the main bar and the drum surface.

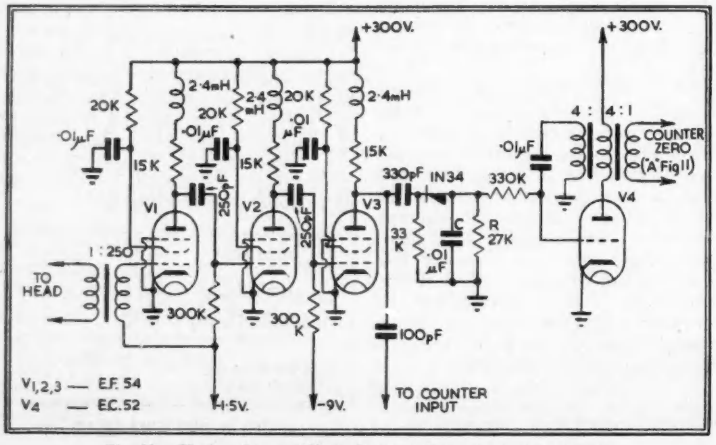

Fig. 10. Clock pulse amplifier, shaper and counter zero generator

Circuits

At the outset it can be stated that all relays are of the Siemens high speed variety with 1000 + 1000Ω coils. The measured time of closure or operation of these is less than 2 m.sec. Relays are drawn in the normal position.

The Clock Track Amplifier.

On this track it is necessary to reproduce with accuracy the sharp transition between the two turning points in output voltage shown in Fig. 6, and it was decided that a bandwidth of at least 200 Kc/s. was needed. The amplifier circuit of Fig. 10 proved adequate.

It will be noticed that the grid coupling and screen resistor by-pass time constants are so chosen that there is a steep reduction in gain below 10 Kc/s. This makes the amplifier very much more stable and makes inter-stage decoupling unnecessary. In particular, 50 c/s. pick-up and microphonic noise from V_1 are imperceptible. V_2 is biased below cut-off to enable the noise background from the medium to be clipped off. This is necessary, since the gap at the end of the clock pulse track (Fig. 2) may contain a noise pulse of sufficient amplitude to trigger the counter after it has been set to zero.

The output of V_3 is fed directly to the input of the binary counter and a portion is rectified by the IN34 germanium diode and applied as a negative potential to the grid leak of the blocking oscillator tube V_4. This keeps the latter from firing until the clock pulse track gap is reached, when the charge on C leaks away via R. The firing of V_4 sends a pulse via the output winding of T to the grid load resistor of the counter, thus "zero-ing" the latter.

The Counter and Coincidence Senser.

The counter used is an ordinary scale-of-two circuit with buffer amplifier to remove unwanted pulses. The circuit constants are chosen so that the counter is reliable up to 100 Kc/s.

Counter Unit

It will be seen from Fig. 11 that when any one of the counter stages C_n is in the same state ("0" or "1") as its associated relay H_n, the potential of the grid of the corresponding coincidence valve falls below cut off. When counter con-

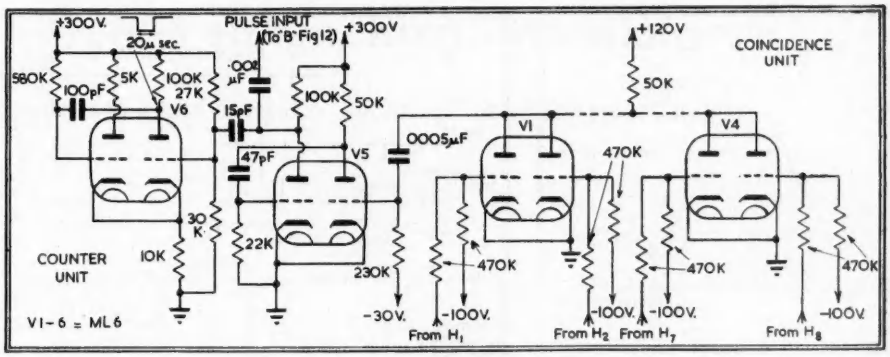

Fig. 11. Counter and coincidence unit

tents and relay do not agree, however, the coincidence valve conducts. Since the resistance of any coincidence valve is only about 7 KΩ, if at least one valve is conducting the potential at the common anode load cannot rise above $7/57 \times 120 = 15$ volts, which is well below the cut-off of the first stage of V_5. The second stage of V_5 acts as an inverter and pulse shaper, since a sharp positive trigger pulse is required for the input pulse generator.

V_6 generates a negative pulse of 220 volts amplitude and 15 μsec. duration which is used to gate the outputs from the digit amplifiers into their respective flip-flops.

The Input Pulse Generator.

Since the heads have an input impedance of less than 0.1 Ω and require pulse currents of 10-20 amps., a special generator had to be designed. Thyratron circuits were tried, but were found to be unreliable and liable to parasitic oscillation. Eventually the circuit shown in Fig. 12 was devised and gives completely satisfactory results.

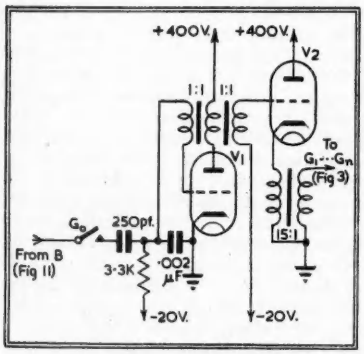

Fig. 12. Input pulse generator

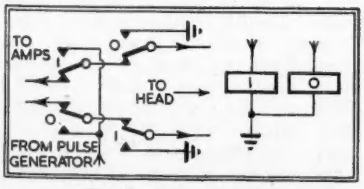

Fig. 13. Relay input gate

In the present memory the record gate G_o is a relay, but it would be simple to substitute an electronic element. In the absence of a gating pulse via G_o the blocking oscillator is held off by the bias. The transformer produces a pulse of less than 1 μsec. duration and the cathode follower transformer enables the whole head array to be pulsed.

The Input Gates.

These are constructed from relay elements and are shown in Fig. 13.

Each gate element consists of two relays having two change-over contacts which are activated from the main circuits of the machine. When relay "1" is operated the head is pulsed in the positive sense, and when relay "0" is operated in the negative sense.

The gate action isolates the digit track amplifiers during pulsing, as the stray pulse which crosses the relay contacts due to capacitative coupling does not effect the input transformers, which have extremely low input impedance.

The Digit Amplifiers.

These are perfectly straightforward R-C coupled amplifiers, again constructed to give low gain below 10 Kc/s. A typical circuit is shown in Fig. 14.

The Output Gate.

It is desired to gate the amplifier output into a flip-flop circuit at a given position only, the two possible amplifier output pulse shapes being shown in Fig. 15.

Since the clock pulse occurs at the origin in the above sketches, it is

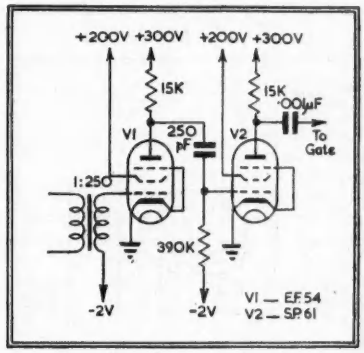

Fig. 14. Typical digit amplifier

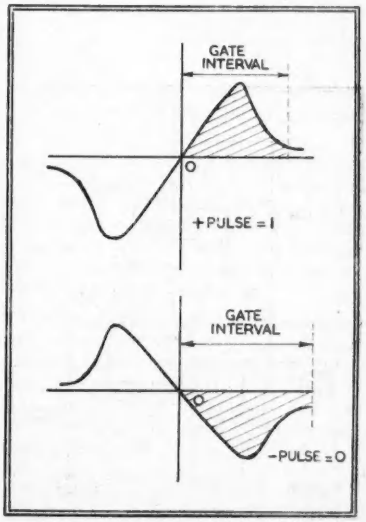

Fig. 15. Output waveforms for "1" and "0"

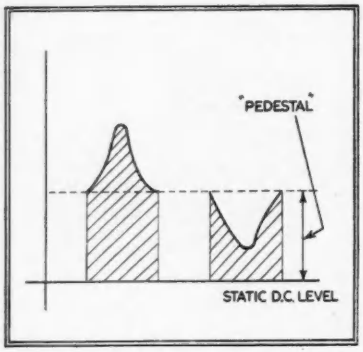

Fig. 16. Output from common gate circuits

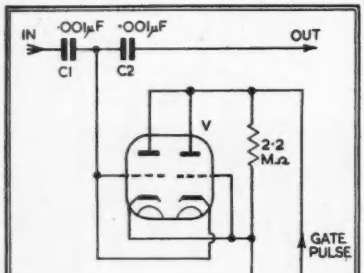

Fig. 17. Gate circuit

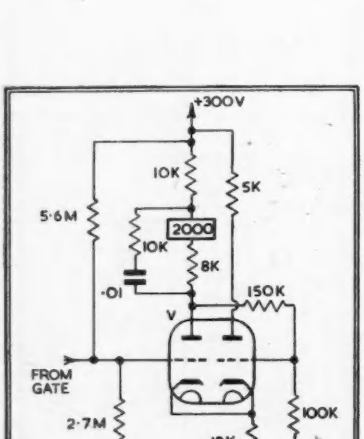

Fig. 18. Toggle output circuit

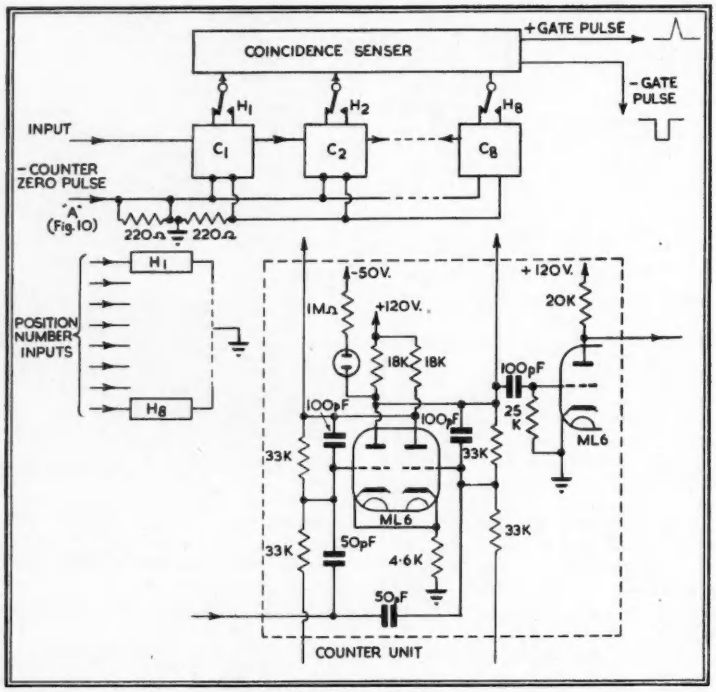

Fig. 19. Counter and coincidence senser

possible to generate a gate signal which extends over one-half of the output pulse only, and thus to select a positive or negative pulse corresponding to unity or zero. Most of the published gate circuits have the disadvantage of placing the output on a "pedestal" as shown in Fig. 16, or else of transmitting pulses of one sign only.

To remedy this defect the circuit of Fig. 17 was devised.

In the absence of a gate pulse the twin triode grids act as diodes and short-circuit incoming signals of either sign to earth. On applying a large negative pulse to the two anodes the electrons are repelled to the cathodes and the resistance of the grid circuits rises sharply. If, in this condition, a voltage variation occurs on C_1 it is transmitted via C_2 to the flip-flop; in the absence of the gate pulse, however, nothing passes.

The Output Stage.

This consists of the standard cathode-coupled toggle, shown in Fig. 18.

For reliable operation it was necessary to compensate the inductance of the relay coil, and the network shown behaves like a pure resistance.

Conclusion

It will be seen from the above circuit descriptions and from the photograph of Fig. 8 that the storage system described in this paper is considerably more compact than any hitherto disclosed. Although in its present form it is somewhat slow in operation it is quite easy to speed up the rotation of the cylinder and to record and read data at several stations around the drum. In this way availability times of better than 1 millisecond could be realised. Work is at present proceeding along these lines and it appears that the necessary modifications are trivial in nature.

The author wishes to express his sincere thanks to Dr. Geoffrey Gee, Director of Research, and to the Board of the British Rubber Producers' Research Association for supporting this work, and also to Miss X. Sweeting and Dr. R. W. Williams for assistance in construction.

References

[1] Wilkes and Renwick ELECTRONIC ENGINEERING 20, 208, (1948).
[2] Williams and Kilburn, *Journal I.E.E.* (In press.)

A High Voltage Ring Modulator

For Use as a "Phase-conscious Rectifier" in Electronic Circuits

By M. J. TUCKER, B.Sc.*

THE need for "phase-conscious rectification" occurs in the design of certain instruments and servo systems, and a similar problem can occur in the design of "Synchrodyne" receivers,[1] particularly in the phase-control circuit.[2] Two voltages are provided: a reference, or "polarising" voltage of constant amplitude, and the signal voltage which is initially derived from the same source, but whose amplitude has been modulated and varies about zero. "Phase-conscious rectification" of the signal produces an output proportional to its amplitude and positive or negative according to the sign of the amplitude—changing this sign is equivalent to a phase change of π, hence the term "phase-conscious." The process is basically one of multiplication, i.e., modulation, of the signal by the reference voltage, and may be performed by the conventional methods of modulation.

The ring-modulator is one of the best devices for this purpose but the conventional design will not handle signals of more than a fraction of a volt, whereas, since D.C. amplification usually adds considerable complication to a circuit, it would often be preferable to apply the output of the modulator directly to the grid of an output stage. D. G. Tucker[3] has recently shown how the performance of a ring modulator may be improved by the use of biases of a fraction of a volt in the modulator arms. It is shown in this article that such bias also increases the voltage handling capacity of the modulator, and that much larger bias may be used for this purpose. Under suitable conditions these very large biases also have the advantage of "swamping" the rectifier characteristics, thus making them behave more nearly as true switches, so that the modulator efficiency is less dependent on the carrier or polarising voltage (*see* Figure 9).

* Royal Naval Scientific Service.

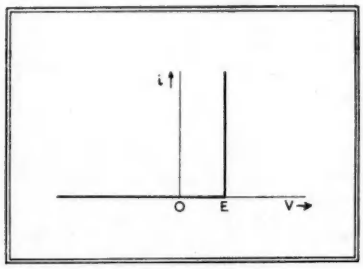

Fig. 1. Idealised rectifier characteristic

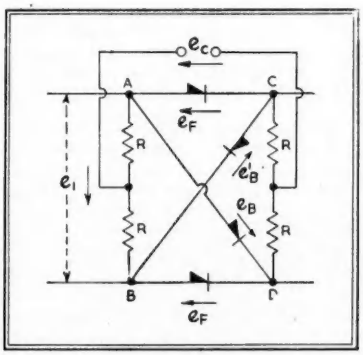

Fig. 2. Simple ring modulator circuit. The voltages marked are instantaneous values

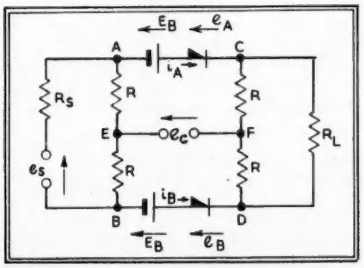

Fig. 3. The circuit is considered when AC and BD are about to conduct

Limiting Signal Voltage to a Ring Modulator

To explain the limiting factor clearly, it will be assumed temporarily that the rectifier elements have an infinite reverse resistance and a zero forward slope resistance, but with a forward voltage "threshold" of E, i.e., the elements pass no current with forward voltages of less than E (Figure 1).

A simple form of modulator is shown in Figure 2. The idealised action is that of a commutator switch that reverses the input-output connexions every half-cycle of the carrier or polarising voltage e_c. This switching is produced by the action of the carrier voltage on the four rectifier elements. During one half-cycle the arms AC and BD will conduct, and during the other half-cycle the arms AD and BC.

When e_c is zero, it is apparent that the voltage e_1 across AB cannot exceed $\pm 2E$, as at this voltage current flows round either ABC or ADE, and any excess voltage will be shorted out. By summing e.m.f's round these paths, it can be shown that the same limiting voltage holds for any value of e_c.

In this idealised case, therefore, $\pm 2E$ is the limiting value of the input voltage.

If a bias battery of voltage E_B is now inserted in the correct sense in series with each rectifier element, the voltage required across each arm to make it conduct will be $(E+E_B)$ and the limiting input voltage is raised to $\pm 2\ (E+E_B)$.

With practical rectifier elements, if E is now the voltage at which the elements pass an appreciable current and e_F and e_1 are instantaneous values, by summing e.m.f.s round ACB and ADB, it can be shown that

$$\text{limiting } e_1 = \pm\ (2E_B + E + E_F)$$

e_F can be taken as being always

greater than E, as even when the elements are not conducting, this voltage must be developed before any current can pass, so that a conservative value of the maximum permissible e_i is:

$$e_i \text{ max.} = \pm 2(E_B + E) \quad \ldots\ldots \quad (1)$$

During the time that the carrier voltage is less than $\pm(E_B+E)$ no rectifiers should be conducting, and there is thus a period when the output voltage should be zero: this can be seen clearly in those oscillograms in Figure 4 which are for low input voltages. The effect of the signal on this interval is discussed below as "Distortion without overload." By the use of suitable bias, this interval can be adjusted so that the modulating function contains very little third harmonic.[2]

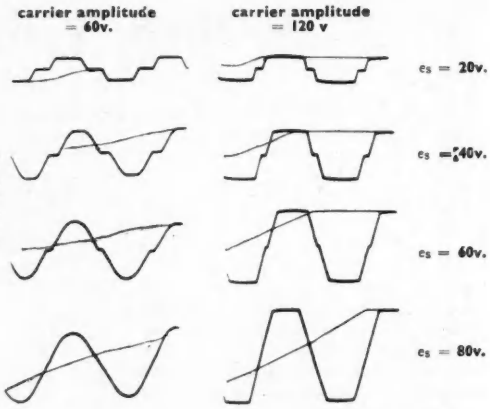

Fig. 4. Oscillograms of the modulation of DC by a battery-biased ring modulator. Bias 30 volts Diodes 6H6 Carrier feed resistors 25K Input resistance 10K. Output direct to C.R.O. deflector plates. Ideally these should be "Square" waveforms

The Effect of Large Biases on Reverse Resistance

The reverse resistance of metal and crystal rectifiers decreases rapidly as the reverse voltage is raised, and the use of large biases will thus reduce the efficiency and stability of the modulator, and owing to the non-linearity of the reverse resistance, large signals may be distorted. It is therefore preferable to use thermionic diodes where possible.

Distortion Without Overload

It has been shown that above a certain voltage some shorting out of the input takes place, and this may be regarded as overload. However, distortion also takes place at smaller input voltages due to the fact that some of the input appears across those rectifier elements which are not conducting, and so alters the point at which conduction commences.

Considering the circuit shown in Fig. 3, where two of the modulator arms have been omitted for clarity, the instantaneous voltages across the rectifier elements when neither is conducting are given by:

$$e_A = e_c - E_B + e_s \; R/(R_S + 2R) \quad \ldots\ldots \quad (2)$$

$$e_B = e_c - E_B - e_s \; R/(R_S + 2R) \quad \ldots\ldots \quad (3)$$

where $e_c = A \sin wt$.

Taking the case when e_s is positive, it is thus apparent that the conduction of AC is in advance of that of BD.

If AC is conducting and BD is not, the current i_A through AC will add another term to the right hand side of equation (3) giving:

$$e_B = e_c - E_B - e_s \; R/(R_S \; 12R) - Ki_A \quad \ldots\ldots \quad (4)$$

where K is a positive factor in terms of the various resistances (*see* (c) below).

Ideally the two rectifiers should commence conduction together at a time unaffected by the signal; the last terms in equations (2) and (3) and the last two terms in equation (4) therefore represent distortion.

During the time when only one rectifier is conducting, the voltage across the output has components from both the signal and the carrier, and this can clearly be seen in the oscillograms of Figure 4. These show the distortion produced on the modulation of a D.C. input using a battery biased ring modulator. Here, as soon as one rectifier starts conducting, the output rises steadily with a portion of the carrier waveform (since the input is steady) until the output voltage reaches the input voltage across the modulator terminals, at which point the second rectifier starts conducting, and the output voltage is derived solely from the input. In the last two oscillograms of the left-hand series, the carrier voltage is never high enough to achieve this latter state, and so the second rectifier never commences conduction.

The influence of various factors on this effect will now be considered.

(a) Carrier voltage ("Polarising voltage"). It is obvious that the most effective means of minimising this distortion is to have a large carrier voltage, as this will shorten the interval during which only one rectifier is conducting.

(b) Bias. There is some advantage in making the bias as small as possible within the limits given by equation (1), so that the time which the distortion occurs is as near as possible to the time at which the carrier voltage passes through zero. The carrier voltage will then be changing most rapidly, and if the signal is an A.C. in phase with the carrier (as in simple phase-conscious rectification), the instantaneous signal voltage will be least.

(c) Input and output impedance. The factor Ki_A in equation (4) can be shown to be given by:

$$Ki_A = \frac{[e_c + e_s/(2+X) - E_B](4+X+Y)}{4+3X+3Y+2XY+Z(2+X)(2+Y)} \quad \ldots\ldots \quad (5)$$

where $X = R_s/R$, $Y = R_L/R$,

and $Z = \dfrac{e_A/ia}{R}$

To obtain some idea of the importance of this effect, it is possible to

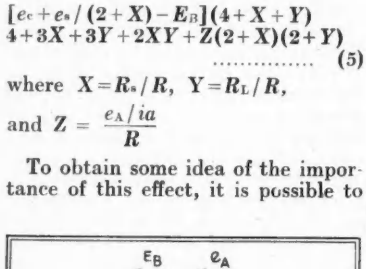

Fig. 5. The circuit is considered when AC and BD are about to conduct

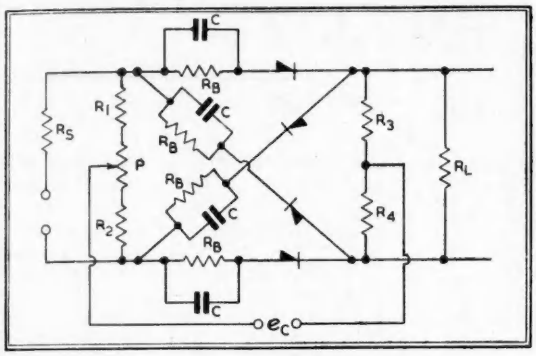

Fig. 6. A method of Auto-Bias.

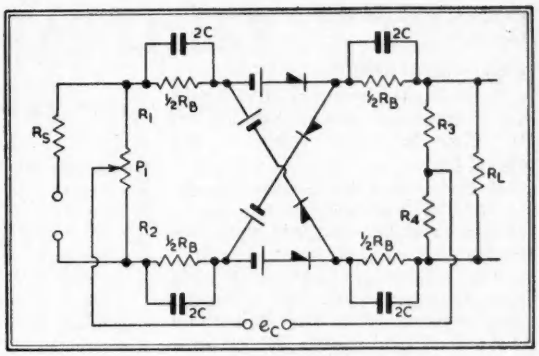

Fig. 7. Circuit equivalent to Fig. 5

calculate the value of e_s which is just sufficient to prevent the second arm conducting at all (this is not quite happening in the oscillogram in Figure 4 where $A=60$ volts, $e_s=40$ volts). To simplify the result it will be assumed that the forward resistance of the rectifier elements is zero and that they start conducting at zero voltage, so that $Z=0$ and the critical $e_B=0$. Then substituting equation (5) in (4) we can obtain the critical signal voltage e_s.

If $X=Y=1$ or $X=0$ and $Y \to \infty$,

Critical $e_s=A-E_B$ where A is the carrier amplitude.

If $X=Y=.5$,

Critical $e_s \approx .65\ (A - E_B)$.

Here e_s refers to the instantaneous value when the carrier voltage is a maximum.

It is thus possible for the effect to be serious when using large biases and signals.

To reduce the value of Ki_A to a minimum, X and Y should be as large as practicable.

In transformer coupled modulators (Fig. 5), it can be shown that the equation equivalent to (4) above is

$$e_B=e_c-E_B-e_s-i_A\ (R_c-R_s-R_L)$$

where it is assumed that the forward voltage across the rectifiers is zero, and that the transformers are perfect with a ratio of 1:2 and 2:1 respectively. Thus, when $R_c=R_s+R_L$, distortion due to the last term vanishes.

Method of Biasing

A convenient method of auto-biasing is shown in Figure 6. The current through the rectifier produces bias voltages in the correct sense across the decoupled resistors R_B. The resistance required give a ratio B of bias voltage to carrier amplitude may be calculated from the following formula:

$$\frac{R_F}{R_B} = \frac{1}{2\pi}\left[\sin^{-1}B+\left(\frac{1}{B^2}-1\right)^{\frac{1}{2}}\right]-.25.$$

$$\approx \frac{1}{2\pi}\left[B+\left(\frac{1}{B^2}-1\right)^{\frac{1}{2}}\right]-.25.$$

Where R_F is the resistance of each carrier feed resistor, and R_B is the resistance of each decoupled bias resistor.

The signal causes the currents through the various arms to alter, and the effect of the decoupled resistors is very similar to that of the circuit shown in Figure 7. Low frequencies, and in particular D.C., in the input or output may thus be considerably attenuated.

If the output feeds into a high impedance circuit—for instance, a valve grid—this effect may be reduced for certain purposes by replacing R_3 and R_4 by capacitors. In the case of phase-conscious rectifiers, it has been found by experiment that this produces non-linearity in the curves of output against the cosine of the phase angle, and of input against output, particularly in the former. The non-linearity decreases as the impedance of the capacitors is increased, and was hardly noticeable on the graphs when the impedance of the capacitors was approximately the same as that of R_1 and R_2. It should be borne in mind that these capacitors

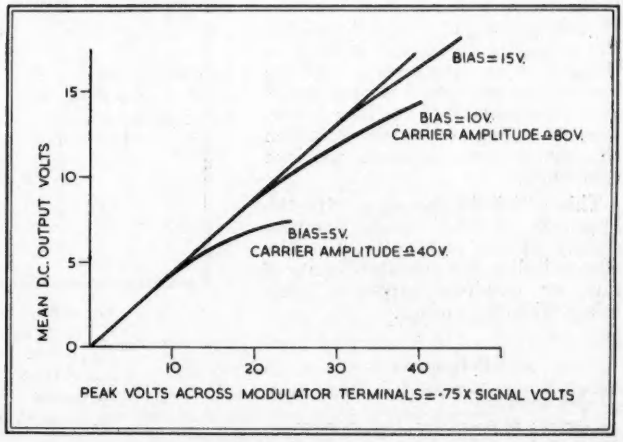

Fig. 8. Curve of output against input for a phase conscious rectifier. Zero Phase-angle

produce a phase shift in the carrier current.

Experimental Results

Experiments were performed with an auto-biased modulator similar to Fig. 6. The resistors had values:

$R_L \gg R_B = R_1 = R_2 = R_3 = R_4 = 3R_9 =$ 30,000 ohms P_1

and the rectifier elements were 6H6 diodes.

The modulator was tested as a phase-conscious rectifier at audio-frequency, so that the input and carrier ("polarising") voltages were of the same frequency.

(1) The curves in Fig. 8 are largely self-explanatory. It will be noted that the output starts falling off when the peak voltage across the modulator terminals is twice the bias voltage.

(2) The curve in Fig. 9 indicates that the modulator efficiency is practically independent of the bias and carrier voltages as long as these are higher than the critical value.

(3) A graph of output against the cosine of the phase angle with an input about two-thirds of the limiting value was also drawn. Though the curve was linear within experimental error, there was some slight consistent indication of the output being smaller than expected for small phase angles. The deviation was less than 2 per cent of the maximum output.

Conclusions

It is concluded that this form of biased ring modulator using diodes provides a satisfactory precision "phase-conscious rectifier" for use at voltages high enough to enable the output to be applied directly to the grid of an output stage, and the author has also found it very useful as a phase-conscious rectifier in certain measuring instruments in which the signal contains large spurious components.

This article is published with the approval of the Lords Commissioners of the Admiralty, but the responsibility for any statements of fact or opinions expressed rests solely with the author.

References

[1] D. G. Tucker: *Electronic Engg.*, 1947, March, August, September.

[2] J. Garlick: *Electronic Engg.*, 1948, February.

[3] D. G. Tucker: "Some Aspects of the Design of Balanced Rectifier Modulators for Precision Applications," *J.I.E.E.* (in press).

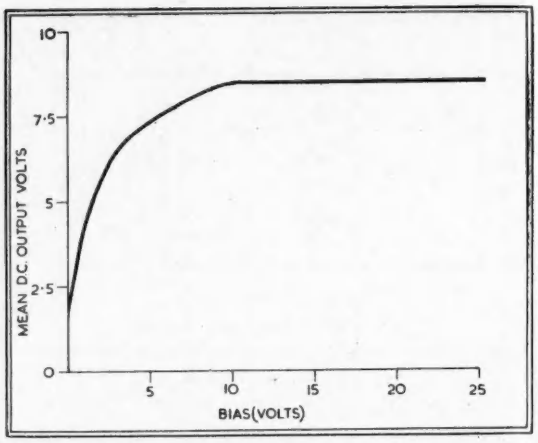

Fig. 9. Curve of output against bias. Input constant at 20 peak volts across modulator terminals

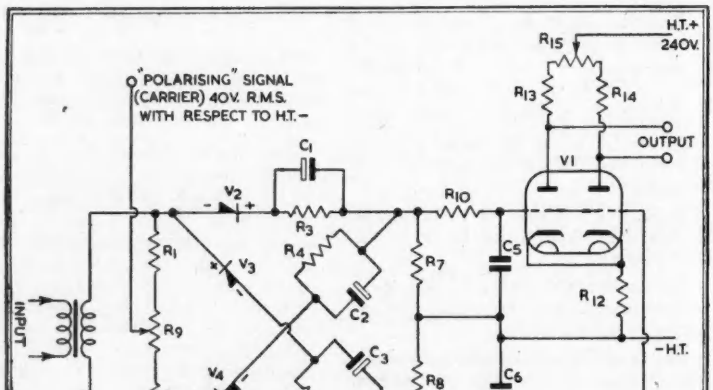

R_{1-3} —50K
R_9 —10K Preset
$R_{10,\ 11}$—470K
R_{12} —220 Ω
$R_{13,\ 14}$—10K
R_{15} —5K Preset

C_{1-4}—1 μF, 25V
C_{5-6}—0.1 μF
V_1 —6SN7
V_{2-5}—SENTERCEL "Uniplate" Rectifiers, Type 6A, or 6H6 Diodes

Fig. 10. A typical "Phase-Conscious Rectifier" circuit for use at Audio-frequencies down to 50 C.P.S. Sensitivity with output shorted is approximately 1.25 ma per volt R.M.S. input

VOLTAGE STABILISERS

—Part III

By F. A. BENSON, M.Eng., A.M.I.E.E.*

Stabilisers Employing Thermionic Valves (*Continued*)

A change of V_o is applied to the grid of V_1 after amplification by V_2 such that the change in the voltage drop across V_1 opposes the change in V_o. The cathode voltage of V_2 is held approximately constant by the neon tube V_3. The grid voltage of V_2 will only be slightly more negative than the cathode so that the grid will receive a fraction v/V_o of the variation in V_o where v is the voltage across V_3. The disadvantage of the circuit is that it cannot produce perfect stabilisation because some change in output is required to give a correction. Certain modifications can be made, however, to obtain better stabilisation. Since variations in V_o are produced principally by changes in input voltage and load current these latter changes can be used to give correction factors. The method of obtaining these corrections is illustrated in Fig. 21. The potentiometer chain is modified and two further resistors R_6 and R_7 are added. If the input voltage changes the change produces a variation in the grid voltage of V_1 by way of R_6, the potentiometer and the amplifier valve V_2. In this way the voltage drop across V_1 changes to oppose the change in input voltage and a variation of output voltage is prevented.

A fine control can be obtained for keeping the output voltage constant if the load current changes by inserting a resistor R_7 as shown. A change in load current produces a change in the voltage drop across R_7 which is applied to the grid of V_1 via the potentiometer and the amplifier valve V_2. In this way the output voltage change is counteracted.

A circuit for providing a stabilised supply of the order of 300 volts at currents from zero to about 160 mA which embodies the above improvements is shown in Fig. 22. Two CV124 valves are employed in parallel as the series element and a CV1091 pentode is used as the amplifier valve. The cathode voltage of the latter is held approximately constant by a CV188 neon tube. If a fault occurs in the circuit resulting in the amplifier valve taking no current (this may easily occur through failure of either the amplifier valve or the neon tube) then the output voltage rises. Since this may damage the equipment to which it is connected a safety precaution is taken by connecting a diode CV1092 directly to the anode of the CV1091. This diode is arranged so that when the anode voltage of the CV1091 exceeds a certain value it passes current and the output voltage is prevented from rising unduly.

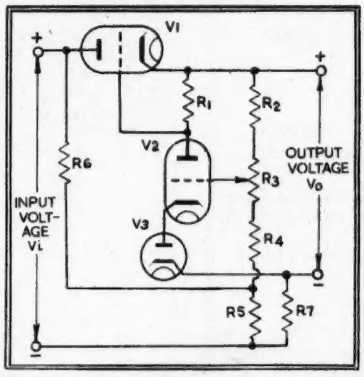

Fig. 21. Series-parallel circuit giving improved stabilisation

The performance of this stabiliser can be summarised as follows: As the load current varies from zero to 160 mA the output voltage only varies by about ±0.15 per cent and a ±10 per cent change in input voltage produces a variation of only about ±0.25 per cent in the output voltage.

The following circuits have been developed to supply a stabilised output voltage of about 1600 volts at a current of the order of 6mA. In each case calculations are made to illustrate the results to be expected. By a suitable choice of valves and other circuit parameters these circuits can be employed to cover wide ranges of current and voltage.

A parallel valve circuit is first considered. In this case a stabilised voltage of 400 volts is available across the neon tubes in addition to and independent of the 1600 volts supply. The circuit consists of a stabilising valve V_1 in series with four neon tubes CV188 across the supply voltage (Fig. 23). The neon tubes in addition to giving the auxiliary voltage also provide the reference voltage. A series resistor R_1 is included.

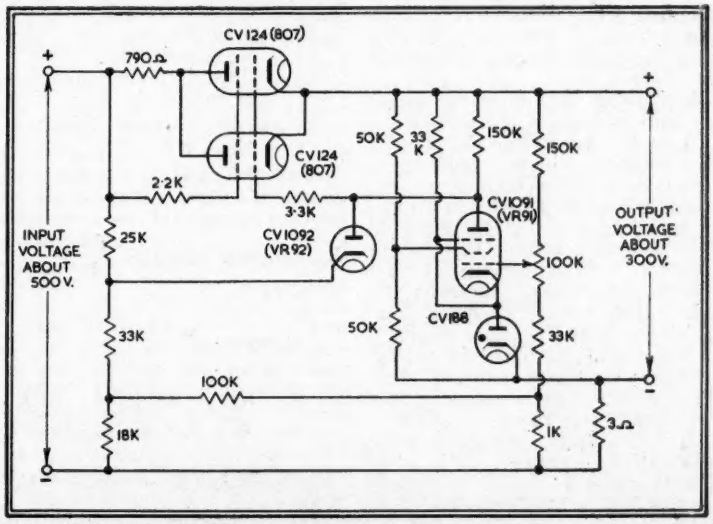

Fig. 22. Stabilised circuit for output voltage of 300 with current variation from zero to 160 mA

* Electrical Engineering Dept., University of Liverpool.

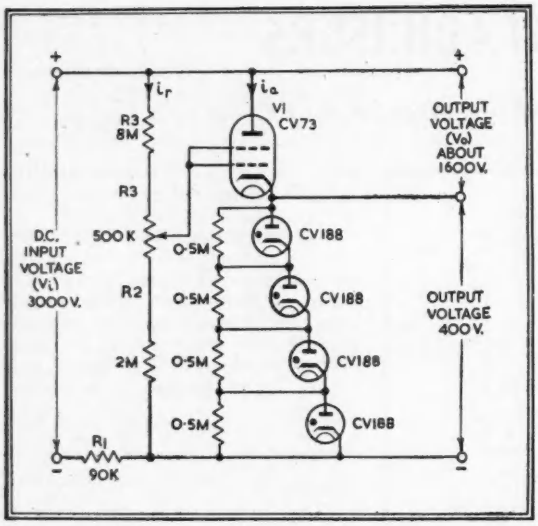

Fig. 23. Stabiliser circuit for output voltage of 1600 using a CV73 beam tetrode

Any high-slope triode is adequate as V_1 but a tetrode or a pentode can also be used. Tetrodes or pentodes may either be connected in the normal manner, supplies for the other grids being obtained from potentiometers across the supply voltage, or used as triodes, all the grids being strapped together. The valve must, of course, be capable of withstanding the input voltage between its anode and cathode and this limits the application of the circuit to voltages of about 3,000 volts or less. A CV73 beam tetrode is used in this case, being connected as a triode, and the output voltage is obtained from between its anode and cathode. Potentiometer R_2R_3 gives the necessary grid voltage for the valve.

Any change in voltage V_1 changes the grid voltage of the CV73 valve (V_3) and thus its anode current. This current change produces a variation in the voltage across the series resistor R_1 which compensates for the change in V_1. For example, if V_1 increases, voltage R_2i_r goes up where i_r is the current through potentiometer R_2R_3. Therefore, the grid voltage of V_1 becomes more positive so that the anode current i_a increases and the drop in voltage across R_1 increases (since i_a flows through R_1). This increase in voltage counteracts the increase in V_1 and the output voltage remains substantially constant. It is advisable to insert a variable resistor in the line R_2R_3 so that small variations can be made in the values of R_2 and R_3 to obtain the best stabilisation.

The performance of this stabiliser will now be calculated. It is shown in the Appendix that the ratio of the percentage change of output voltage to the percentage change of input voltage, i.e., the quantity $\frac{dV_o}{V_o}\cdot\frac{V_1}{dV_1}$ is given by:—

$$\frac{dV_o}{V_o}\cdot\frac{V_1}{dV_1} = \frac{1}{1+\frac{v}{V_1}\left[\frac{R_1\left(\frac{\mu R_3-1}{ra}\right)-1}{R_2+R_3}\right]} \quad \ldots(1)$$

where v is the constant reference voltage, *i.e.*, the voltage across the neon tubes

μ is the amplification factor of the CV73

ra is the anode resistance of the CV73.

Also, the ratio of the percentage change of output voltage to the percentage change of load resistance R_L, i.e., the quantity $\frac{dV_o}{V_o}\cdot\frac{R_L}{dR_L}$ is given by:—

$$\frac{dV_o}{V_o}\cdot\frac{R_L}{dR_L} = \frac{1}{1+\frac{R_L}{ra}+\frac{R_L}{R_1}+\frac{R_L}{R_2+R_3}+\frac{\mu}{r_a}\left(\frac{R_2R_L}{R_2+R_3}\right)} \quad \ldots(2)$$

In this case $R_1 = 90\text{K}\Omega$: $V_1 = 3{,}000$ volts.

Assume for optimum stabilisation $R_2 = 2.1\text{M}\Omega$, $R_3 = 8.4\text{M}\Omega$. The CV73 valve when connected as shown has the characteristics $\mu = 300$, $ra = 100\text{K}\Omega$. The characteristics of the CV188 neon tubes have already been given, thus $v = 400$ volts.

$\therefore$ from (1) $\frac{dV_o}{V_o}\cdot\frac{V_1}{dV_1} = 0.03.$

i.e., a change of input voltage of 10 per cent causes the output voltage to change by 0.3 per cent, *i.e.*, by about 5 volts.

From (2) it can be seen that $\frac{dV_o}{V_o}\cdot\frac{R_L}{dR_L}$ depends on the value of the load resistance R_L.

Assuming that $R_L = 260\text{K}\Omega$

$$\frac{dV_o}{V_o}\cdot\frac{R_L}{dR_L} = = 0.006$$

i.e., a change in load resistance of 10 per cent causes the output voltage to change by 0.06 per cent, *i.e.*, by about 1 volt.

A series-valve circuit will now be considered. Fig. 24 shows one of a number of possible circuit arrangements. The stabilising valve, in this case a CV73 beam tetrode connected as a triode, is in series with the load and a series resistor R_1 is also included. The grid voltage of the CV73 is governed by the potentiometer R_2R_3. The reference voltage (v) is placed in series with R_2R_3 and is obtained from a single neon tube CV188 but in this case an auxiliary supply of the order of 100 volts is required.

Variation of input voltage V_1 changes the grid voltage of the valve. Thus the voltage V_a across

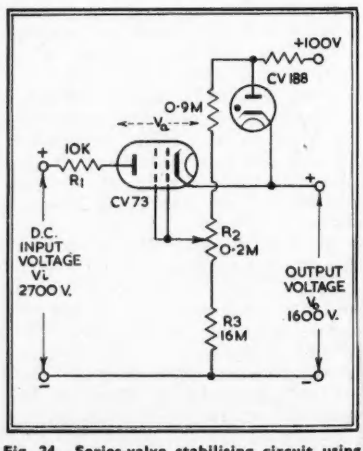

Fig. 24. Series-valve stabilising circuit using a CV73 beam tetrode

the valve varies and compensates for the change in V_1. This method is not particularly good as it is necessary to have a change in output voltage V_o in order to produce a change in grid voltage of the valve. The performance of this stabiliser will be calculated. It is shown in the Appendix that in this case the ratio of the percentage change of output voltage to the percentage change of input voltage is given by:

$$\frac{dV_o}{V_o} \cdot \frac{V_1}{dV_1} = \frac{1}{1 + \frac{v}{V_1}\left[\frac{\mu R_3 - R_1 - r_a}{R_2 + R_3}\right]} \quad \ldots\ldots (3)$$

and the ratio of the percentage change of output voltage to the percentage change of load resistance R_L is given by:—

$$\frac{dV_o}{V_o} \cdot \frac{R_L}{dR_L} = \frac{1}{1 + R_L\left[\frac{R_1 + R_2 + R_3 + r_a + \mu R_3}{(R_1 + r_a)(R_2 + R_3)}\right]} \quad \ldots\ldots (4)$$

It can be seen from (3) that the valve employed should be one having a high "slope."

In this case $R_1 = 10\text{K}\Omega$ $R_2 = 1\text{M}\Omega$ (say) $R_3 = 16\text{M}\Omega$ $V_1 = 2{,}700$ volts $v = 100$ volts $\mu = 300$, $r_a = 100\text{K}\Omega$, Assume $R_L = 260\text{K}\Omega$.

From (3) $\frac{dV_o}{V_o} \cdot \frac{V_1}{dV_1} = 0.087$

i.e., a change in input voltage of 10% causes the output voltage to change by 0.87%, *i.e.*, by about 14 volts.

From (4)

$$\frac{dV_o}{V_o} \cdot \frac{R_L}{dR_L} = 0.022$$

i.e., a change in load resistance of 10% causes the output voltage to change by 0.22%, *i.e.*, by about 3.5 volts.

Many series-parallel valve circuits have been designed, each one is essentially a combination of the two previous arrangements. In these circuits there are several possible positions for the reference voltage, v. Three circuits will be considered in detail. In all of them the control grid of the series valve is connected to the anode circuit of the parallel valve and the latter behaves as a voltage amplifier.

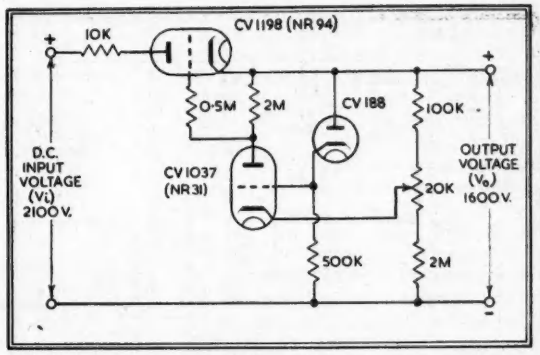

Fig. 25. Series-parallel stabiliser circuit using CV1198 and CV1037 triodes

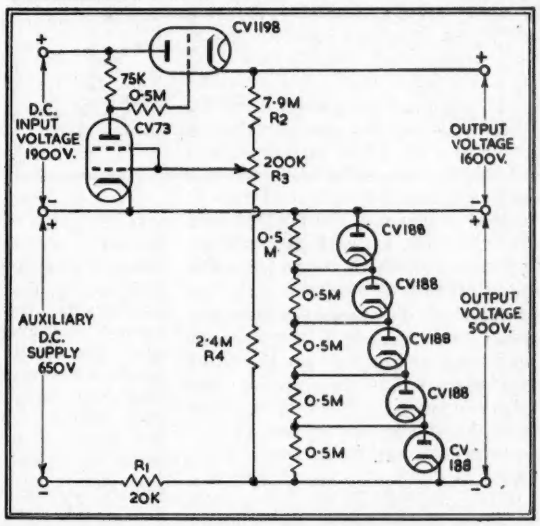

Fig. 26. Series-parallel stabiliser circuit similar to Fig. 25 (above) but using five neon tubes

In the first arrangement considered a CV1198 triode is used as the series valve and a CV1037 triode as the parallel one. The reference voltage obtained from a neon tube CV188 is placed between the cathode of the CV1198 and the grid of the CV1037 as shown in Fig. 25.

Any change in the output voltage changes the voltage of the cathode of the CV1037 with respect to its grid which has a fixed potential with respect to the positive of the output voltage. The change in cathode voltage changes the anode current of the CV1037 and hence the grid voltage of the CV1198. This produces a change in the voltage drop in the CV1198 which counteracts the change in output voltage. Analysing this circuit as in the above cases and remembering that for the CV1198 $\mu = 18$ and $r_a = 2{,}800$ ohms and for the CV1037 $\mu = 25$ and $r_a = 100\text{K}\Omega$ it can be shown that the ratio of the percentage change of output voltage to the percentage change of input voltage is 0.099, *i.e.*, a change of input voltage of 10% causes the output voltage to vary by 0.99%, *i.e.*, by about 16 volts, similarly a change in load resistance of 10% causes the output voltage to change by about 0.064%, *i.e.*, by about 1 volt.

Another satisfactory series-parallel circuit is shown in Fig. 26. Five neon tubes are employed to give the reference voltage v and in this case an auxiliary supply is also required. A stabilised voltage of 500 volts is available across the neon tubes if required. A CV1198 triode is used as the series valve and a CV73 beam tetrode connected as a triode is used as the parallel valve. Here the grid voltage of the CV73 is controlled by part of the sum of the output voltage and the reference voltage. Change in output voltage changes the grid voltage of the CV73 and therefore its anode current. This changes

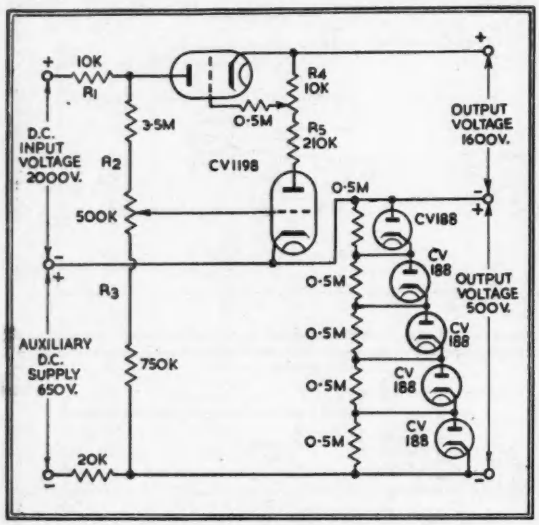

Fig. 27. Series-parallel stabiliser circuit with CV1198 triodes as both series and parallel valves The grid of the parallel valve is controlled by the input voltage

the grid voltage of the CV1198 and hence its current and the voltage drop across it which counteracts the change in output voltage.

Analysing this circuit and remembering that for the CV1198 $\mu=18$ and $r_a=2{,}800$ ohms and for the CV73 valve when triode connected $\mu=300$ and $r_a=100\text{K}\Omega$ it may be shown that the ratio of the percentage change in output voltage to the percentage change in input voltage is 0.024 and in output voltage to the percentage the ratio of the percentage change in load resistance is 0.000019.

As stated earlier these circuits can be used for a wide range of voltages by choosing the components carefully. For example, in this circuit a stabilised output voltage of from 1,900-2,100 volts can be obtained by increasing the input voltage to 2300 volts and making $R_1=25\text{K}\Omega$, $R_2=2.7\text{M}\Omega$, $R_3=50\text{K}\Omega$, $R_4=550\text{K}\Omega$.

A third satisfactory circuit is shown in Fig. 27. In this circuit the grid of the parallel valve is controlled by the input voltage and not the output voltage as in the previous two circuits. CV1198 triodes are used for both series and parallel valves and five neon tubes CV188 together with an auxiliary supply give the required reference voltage. Any change of input voltage changes the grid voltage of the parallel valve and hence its anode current. Since the grid of the series valve is connected to the anode circuit of the parallel valve the grid voltage of the series valve is changed. Hence there is a variation in the voltage drop across the series valve which counteracts the change in input voltage and keeps the output voltage practically constant. The great advantage of this circuit is that the output voltage can be made independent of the input voltage, if as shown in the Appendix, the following condition is satisfied:—

$$R_3\,\mu_p(R_2+\mu_s\,R_4)= (R_2+R_3)\,(R_4+R_5+r_{ap})$$

where:—

r_{as} = anode resistance of the series valve

r_{ap} = " " " " parallel valve

μ_s = amplification factor of series valve

μ_p = amplification factor of parallel valve

and $R_2R_3R_4$ and R_5 are the resistances shown in Fig. 27.

In the case illustrated:—

$$\mu_s=\mu_p=20$$
$$r_{as}=r_{ap}=2{,}800 \text{ ohms.}$$

Assume that $R_2=3.75\text{M}\Omega$, $R_3=1\text{M}\Omega$, $R_4=2.5\text{K}\Omega$. $R_5=217.5\text{K}\Omega$.

Then it will be seen that the above condition is approximately true.

The ratio of the percentage change of output voltage to the percentage change of load resistance for this circuit is of the order of 0.01.

Miscellaneous Circuits

Stabilisers Employing Barretter Tubes

THE barretter tube consists of an element of iron wire enclosed in a glass envelope which contains hydrogen. Over a certain range of voltage across such a tube its resistance increases nearly proportionally with the voltage, *i.e.*, the current through it remains substantially constant. This can be seen by reference to the typical characteristic of a barretter tube shown in Fig. 28. The voltage range and the current are governed by the dimensions of the iron wire. Thus, if a barretter tube is placed in series with a load across a power supply it will absorb fluctuations in the supply voltage. The voltage across the barretter changes to counteract the variations in the supply voltage.

Taylor[25] has described in detail one circuit where the barretter is placed in series with the primary of a transformer (Fig. 29) in order to keep the voltage on the latter constant. In the circuit described, as the input voltage varies over the range 105 to 130 volts, the voltage to the transformer primary remains constant at 88 volts to within ±1 volt. Even when the input voltage varies over the wide range 90 to 140 volts the output only varies by a maximum of 6 volts, *i.e.*, by about 7 per cent.

The characteristics of some available barretter tubes are given in the table below:—

Type	Current (amp.)	Voltage Range (volts)
301	0.3	138—221
302	0.3	112—195
303	0.3	86—129
304 (CV1202)	0.3	95—165
C1	0.2	90—230
C1C (CV1400)	0.2	90—230
C9	0.2	35—100
1927	0.18	60—120
1928	0.18	100—210

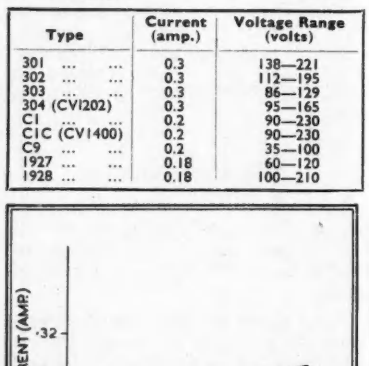

Fig. 28. Typical characteristics of barretter tube

Stabilisers Employing Metrosil

Metrosil (similar products are known under the trade names Atmite and Thyrite) may be employed with success in voltage stabilising circuits. Metrosil[27,28,29] is a solid which contains silicon carbide and has a non-linear volt-ampere characteristic. The current through a Metrosil disk varies as the fourth or fifth power of the voltage across it; *i.e.*, $I = AV^n$ or $V = BI^k$

where $n = 4$ to 5

$k = 1/4$ to $1/5$

I is the current through the disk

V is the voltage across the disk, and

A and B have values which depend on the size and shape of the disk and the material.

B varies from about 60 to 3,000. The material can be adapted to very wide ranges of both current and voltage.

Two common methods are available for employing Metrosil as a voltage stabiliser. In the first the Metrosil unit is connected in series with a resistance R across the supply voltage (Fig. 30). The resistance R is such that the voltage drop across it v is large compared with the output voltage V_o across the Metrosil. Then variations of input voltage V_i produce only small changes in V_o as shown below. Let the current in the circuit be I.

Then $I = AV_o^n$

Also

$$V_i = V_o + v, = V_o + RI = V_o + RAV_o^n$$

Therefore

$$\frac{dV_i}{dV_o} = 1 + RAn\,V_o^{n-1} = 1 + \frac{n(V_i - V_o)}{V_o}$$

i.e.,

$$\frac{dV_o}{V_o} = \frac{dV_i}{nV_i + V_o(1-n)} = \frac{dV_i}{nV_i}$$

approximately.

Thus the percentage change of output voltage is approximately $1/n$th of the percentage change of input voltage. That is, if the input voltage varies by ±10 per cent the output voltage only varies by about ±2 per cent. In the second method of arranging a voltage stabiliser using Metrosil a bridge circuit is employed. Two identical units of Metrosil M_1 and M_2 (Fig. 31) are placed in diagonal arms of the bridge, the other two arms of which contain identical resistances R_1 and R_2. At one particular value of input voltage the bridge balances, *i.e.*, at the point where the input voltage is such that the voltage across a Metrosil unit is equal to the voltage across a resistance. If the input voltage is increased from zero the output voltage starts at zero, rises to a maximum value, and falls again to zero, then increases in the reverse direction as shown in Fig. 32. If the working point of the bridge is arranged to be at the point P on the flat part of the curve, then over a certain range of input voltage (say Q_1Q_2) the output voltage is substantially independent of the input voltage. Ashworth, Needham and Sillars[29] have analysed the circuit and drawn up a table showing the relation between the various currents and voltages and the circuit parameters. The data presented, which includes the conditions for maximum efficiency, is useful when designing such a bridge. These methods of stabilisation are rather inefficient but have several advantages. The circuits are not limited to currents of a few milliamps as are circuits containing valves or neon tubes and are suitable for both direct and alternating current supplies. Further, there is no appreciable deterioration in performance with time as is frequently the case with valve circuits. But any circuit incorporating elements with non-linear volt-ampere characteristics usually provides harmonic voltages when used on A.C. which may be troublesome.

(*To be continued*)

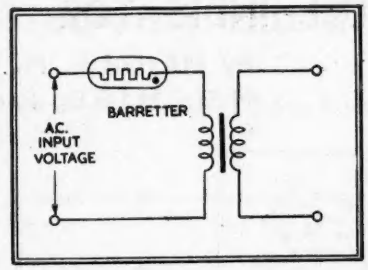

Fig. 29. Stabiliser circuit using barretter tube in series with transformer primary

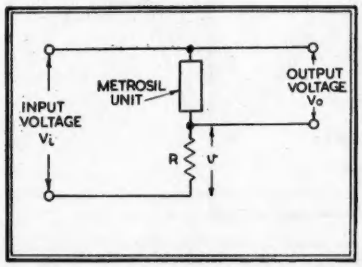

Fig. 30. Stabiliser circuit using a Metrosil unit

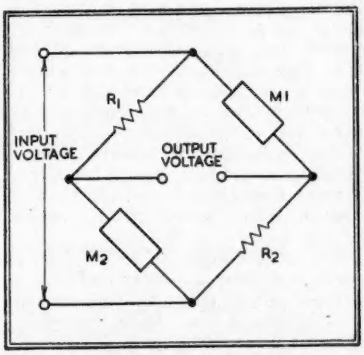

Fig. 31. Stabiliser circuit using Metrosil units in a bridge arrangement

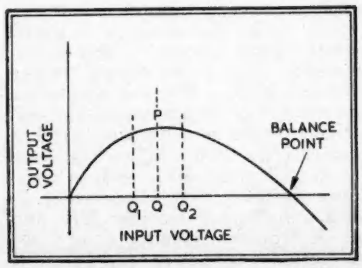

Fig. 32. Voltage characteristics of Metrosils

References

[26] S. G. Taylor: "Ballast Tubes as Automatic Voltage Regulators." *Electronics*, 15, 26. 1942.

[27] "Metrosil. Its Characteristics and Applications Discussed." *The Electrician*, 133, 406. 1944.

[28] R. W. Sillars: "Metrosil." *Met. Vick. Gaz.* July, 1944.

[29] F. Ashworth, W. Needham and R. W. Sillars: "Silicon Carbide Non-Ohmic Resistors." *Journ. I.E.E.*, 93 (Part 1), 385. 1946.

A NEW VISUAL NULL INDICATOR

By MAJOR E. H. W. BANNER,
M.Sc., M.I.E.E., F.Inst.P.,

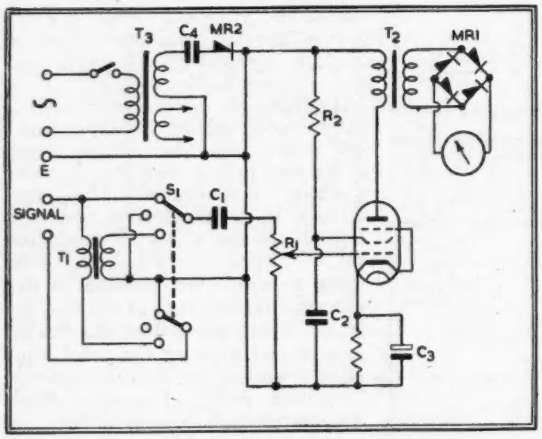

Schematic of the Null Indicator.

THE high sensitivity of telephones to small audio-currents leads to their wide use for A.F. bridges, but there are occasions, such as in noisy rooms, where a visual indication is preferable, especially when increased sensitivity is required by valve amplification. The galvanometer, in some form, is then used. The earliest published use of such a null indicator appears to be in 1932, when the author described* a simple one-valve amplifier with screened input and output transformers feeding a rectifier microammeter as the indicator. Since that date many developments have occurred, mainly in the direction of increased sensitivity and various refinements. There is now a tendency to omit some of the complications while retaining the advantages, and a simple one-valve pentode amplifier has now been developed by Mr. S. J. Wright, B.Sc., A.Inst.P. For wide application two alternative impedances are provided, selected by a switch; these are a high impedance of 1 MΩ with one end earthed, and a low impedance with an input transformer in which the actual impedance varies from about 1 KΩ at 10 Kc/s. to about 100 Ω at 50 c/s. The overall frequency range is 40 c/s. to 20 Kc/s., the maximum sensitivity being in the range 100 c/s.- 2 Kc/s.

The instrument is contained in a small metal screening case carrying a 3½-in. instrument as the indicator, the other components being inside. The zero position of the pointer is to the left of the scale so that any deflexion moves the pointer over the scale. It is intended for 50 c/s. mains, but will also serve 40-100 c/s. Tappings deal with mains voltages of 110, 210, 230 and 250 V.

Controls are on the front of the panel and comprise a central *On-Off* switch, a *sensitivity* control and a three-position input switch for *High, Off* and *Low Impedance*. In the *Off* position the amplifier is short-circuited.

The circuit diagram shows the input transformer T_1, with double-pole switch S_1 serving to select the desired impedance range. A capacitor of 0.1 μF, C_1, passes A.C. and prevents the potential divider R_1 which forms the sensitivity control from being a conducting circuit between the terminals. The valve is a 6J7 pentode with an output transformer T_2 in the anode lead which passes signal current to the microammeter via a 4-element bridge rectifier $MR1$. The microammeter has shaped poles for maximum sensitivity in the zero position. It has a sensitivity of 0.1 in. on the scale for 0.1 μA near zero, with a resistance of 2KΩ. A transformer T_3 with a half-wave rectifier MR_2 and an electrolytic capacitor C_4 of 1,000 μF forms the power supply unit. From this R_2 of 0.1 MΩ and C_2 of 0.25 μF set the screen voltage. The cathode circuit contains the resistor R_3 of 4700 Ω and an electrolytic capacitor of 50 μF. A separate transformer winding T_3 feeds the valve heater.

The overall instrument sensitivity at maximum gain and high impedance is about 1 mV, the higher the frequency the greater the deflexion up to about 5 Kc/s., where it is 0.05 in., falling off above 15 Kc/s., all with an input of 1 mV. At low impedance the sensitivity is 0.01 in. deflexion at 0.03 mV at 50 c/s., and it increases with frequency.

The overload capacity of the instrument is high, as the valve is used insensitively with a low anode voltage, and by virtue of the non-linear instrument characteristic due to the shaped pole-pieces the current through the microammeter does not exceed 1 mA even with 10 V applied to the input terminals.

It will be seen that the instrument comprises a sensitive and robust null indicator of high or low impedance as required, suitable to audio-frequency bridges in general.

Acknowledgment with thanks is made to Baldwin Instrument Co., Ltd., for permission to publish the design details of the instrument.

* *Journ. Sci. Inst.* IX (July 1932), p. 236.

EXPERIMENTAL V.H.F. TRANSMISSIONS

As has already been announced, the B.B.C. intend to make a full-scale trial of A.M. and F.M. as soon as the V.H.F. station now building at Wrotham is ready. In the meantime experimental V.H.F. transmissions with A.M. and F.M. are being made from two transmitters at Alexandra Palace. The carrier frequencies are 90.3 Mc/s. for F.M. and 93.9 Mc/s. for A.M. Both transmitters carry the Third Programme every day from 6 p.m. to midnight, and in addition the F.M. transmitter carries the Light Programme from 11 a.m. to noon and from 2.30 p.m. to 4.30 p.m. on Mondays to Friday inclusive. Vertical polarisation is normally used for both transmissions, but horizontal polarisation may be substituted at any time and the operating schedule may be altered without notice.

Projective Three-dimensional Displays—Part I

By D. M. MacKAY, B.Sc., A.Inst.P.*

A CATHODE-RAY tube as conventionally used gives a two-dimensional display. That is to say, it shows the way in which one variable depends on another, by means of a two-dimensional graph. It is true that, for example in television or radar, the *brightness* of the spot may be used to represent the dependent variable, which can then be shown as a function of *two* independent variables. In one sense this could be described as a "three-dimensional" display, but we shall here use the term to refer to displays in which the *position* of the spot is under the control of three variables.

There is no difficulty in making the position of the spot depend on more than two variables. Probably most of us who use oscilloscopes have at some time connected up X and Y leads, but omitted to make the "earthy" connexion, so that a stray 50 c/s. voltage has superimposed itself on the pattern and displaced it into a "waving carpet" (Fig. 1). More careful users may like to make the experiment deliberately. The simplest way is to insert the secondary winding of a suitable mains transformer in series with the lead which would normally be connected to the earthy terminal of the oscilloscope.

The problem of devising a useful three-dimensional display lies rather in *separating* out the part which each of the three variables has played in producing a given pattern, since with three variables "in control", any one spot-position corresponds to an infinite number of possible combinations of variables.

Now a picture of a three-dimensional subject, on the screen of a C.R. tube, is essentially a projection of the subject, on a plane making certain definite angles with its three axes of reference.

We have thus two problems in this type of display — firstly to secure a reasonably accurate projection of three-dimensional data on the X-Y plane of the C.R. tube, and secondly to remove the ambiguities which exist in any single projection.

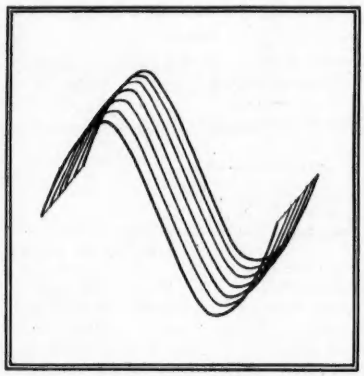

Fig. 1. A "waving" carpet

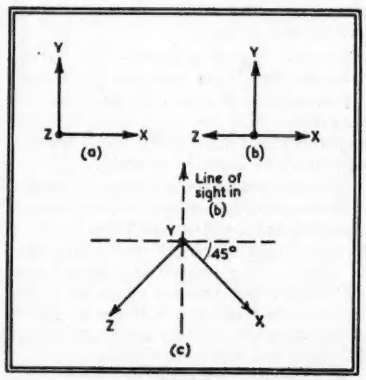

Fig. 2.
(a) View along Z axis
(b) View at 45° to X axis
(c) View of (b) along Y axis

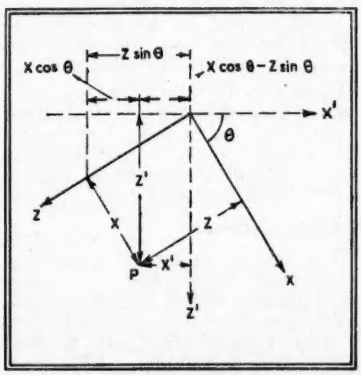

Fig. 3. Rotation of X axis through angle θ

It should be mentioned that this projective method† is not the only way of displaying three dimensions. A comprehensive paper on the display of three-dimensional radar data has appeared recently,[1] and includes an account of optical methods of filling a small *volume* of space with data so as to form a "truly" three-dimensional picture.

Projection

Looking along any *axis*, X say, of a three-dimensional reference system, one has a "plan view" of the other two axes Y and Z. If, however, the line of sight is rotated to a position half-way between X and Z axes in the XZ plane, the view of the Y axis, will be unchanged, but the other direction of the field of view will include "some of X and some of Z." (Fig. 2.).

In mathematical terms what one sees is the projection of X and Z axes on the plane normal to the line of sight. The apparent horizontal co-ordinate x' of any point in the XZ plane will thus be the difference between the projections of its true co-ordinates x and z on the "plane of sight." In general, (Fig. 3), when the X axis has been rotated through an angle θ from the position of Fig. 2(a), i.e., when the Z axis makes an angle θ with the line of sight, the "visible co-ordinate" x' of a point P (x, z) is given by:

$$x' = x\cos\theta - z\cos\theta \quad \ldots\ldots\ldots\ldots \quad (1)$$

The corresponding "invisible" z' co-ordinate is given by:

$$z' = x\cos\theta + z\sin\theta \quad \ldots\ldots\ldots\ldots \quad (2)$$

Now let us assume that we have three voltages, x, y and z, of which y varies with x and z so as to describe a three-dimensional pattern. Clearly all that we have to do to obtain a view along the Z' direct-

* Wheatstone Physics Laboratory, University of London King's College.

† The first published account of projective technique is believed to be the Patent application of Parker et. al.[2]. Mention should also be made of a report by Dumont Laboratories[3], and a paper by Schmitt[4] on similar lines.

tion, is to mix the X and Z voltages in the proportions $\cos\theta$ and $\sin\theta$ before applying the resultant to the X-plates of our C.R. tube. In fact, if we apply a fraction $x\cos\theta$ to one X-plate, and $z\sin\theta$ to the other, the tube will subtract them automatically and give the required X' deflexion to the spot according to Equation (1). The result will be a view of the pattern described by x, y and z, from ground level as it were, and at an angle θ to the Z axis. (Fig. 4, see page 252).

More generally, the line of sight may be at an angle oblique to all three axes. The rule which we have found for the simple case can easily be extended, and in its general form can be stated thus:

To obtain a projection on a plane in which the axis X', Y' are specified by direction cosines ($l_1m_1n_1$) and ($l_2m_2n_2$) relative to the X, Y Z axes, mix the x, y, z voltages in the proportions of the direction cosines of X' and Y'. In other words, make

$$x' = l_1x + m_1y + n_1z \quad \ldots\ldots\ldots\ldots \quad (3)$$

$$y' = l_2x + m_2y + n_2z \quad \ldots\ldots\ldots\ldots \quad (4)$$

and if z' is required,

$$z' = l_3x + m_3y + n_3z \quad \ldots\ldots\ldots\ldots \quad (5)$$

where ($l_3m_3n_3$) are the direction cosines of the line of sight.

Rotation

In everyday life, the two-dimensional projection of the solid world on the retina of the eye is given "depth" in a number of ways. The tension in the focusing muscles, the convergence of the eyes and the different views seen in binocular vision, and, of course, long experience of familiar objects, all help us to distinguish between a small object near at hand and a large one farther away. Sometimes, however, even these are insufficient, and we have to take the trouble to move our point of view to see another aspect of the field, from which the ambiguity is resolved. This important facility of *relative rotation*—so commonly used, for example, in "parallax" methods of optical measurements—is fortunately very simple to secure in our projective displays, and provides the key to the problem which confronted us at the beginning of this article.

There are many ways in which we may choose to rotate our pattern, but one of the most convenient methods is to carry out the selection of aspect in two independent stages.

The first corresponds to the transformation which we considered (Equations 1 and 2), which effectively rotates the pattern about the Y axis. With ganged attenuator-controls to mix continuously-variable proportions of x and z according to Equations 1 and 2, we can select any angle of view (θ) at the turn of a knob.

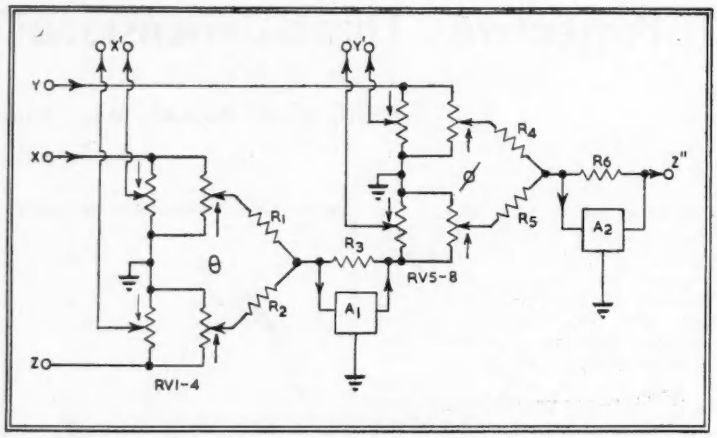

Fig. 5. A resistive resolving circuit

Ganged potentiometers are very suitable for this purpose, though "resolvers" of other kinds, such as magslips,[1] may be used over limited frequency ranges. (We shall return to practical considerations).

The second stage of aspect—selection can conveniently correspond to rotation about the X' axis—choice of the *angle of elevation* of the line of sight. The principle is the same as before, but in this case we must combine y with the voltage z' which is synthesised in the first operation (Equation 2) so as to form:

$$y' = y\cos\theta - z'\sin\theta \quad \ldots\ldots\ldots\ldots \quad (6)$$

and if we wish:

$$z'' = y\sin\theta + z'\cos\theta \quad \ldots\ldots\ldots\ldots \quad (7)$$

Here z'' is the "invisible" co-ordinate normal to the face of the C.R. tube. Its use in providing perspective will be discussed below.

These two facilities can together remove any structural ambiguities present in a given projection, since any surface which is seen "edge-on" under one rotation is "opened out" under the other.

A Practical Circuit

A practical circuit to effect the transformations which we have been considering is shown in Fig. 5. The two stages of rotation, about Y- and X'-axes respectively, can be followed quite separately. $RV_{1\text{-}4}$ and $RV_{5\text{-}8}$ are ganged potentiometers which theoretically should be graded according to sine and cosine laws, but may in practice be linear, with suitable modifications. In the first stage, voltages $x\cos\theta$ and $z\sin\theta$ are derived from RV_1 and RV_3 and passed to the X-plates (preferably through a balancing amplifier). RV_2 and RV_4 are "cross-connected" to RV_1 and RV_3 so that voltages $x\sin\theta$ and $z\cos\theta$ are supplied to the adding circuit $R_{1\text{-}3}$. The latter is one form of the well-known "anode-follower" circuit, in which approximately equal resistances are used in the input and feedback paths of the sign-reversing amplifier A_1. A_1 should have a frequency-response extending at least to the lowest frequency present in x, y or z, but its linearity is of negligible importance owing to the complete negative-feedback. The output is given by the formula:

$$v_o = \frac{a.m}{1+a+2m}\,(x\sin\theta + z\cos\theta) \quad \ldots \quad (8)$$

Where a is the gain of A_1, and m is the ratio R_3/R_1, R_1 and R_2 being equal. Equation (8) represents simple addition if we make $m = \frac{a-2}{a+1}$, and it is clear that, if the gain is large, the value of m required will not differ much from unity, whatever the actual value of a. Changes in gain (or non-linearity) will have correspondingly little effect on v_o, which is then equal to $-z'$. A single valve can provide ample gain for most purposes.

The second stage—a rotation through θ—is identical in principle with the first, but since A_1 changes

the sign of z', the voltage applied to the Y-plates is $y\cos\theta + z'\sin\theta$, while the "perspective" voltage z'' is $-(y\sin\theta - z'\cos\theta)$. Both z' and z'' are developed at low impedance, since feed-back reduces the output impedance of A_1 and A_2 to a few hundred ohms. The output of A_2 can thus be directly connected to the "perspective" circuits, and can be quite heavily loaded without ill effects. z'' can readily be increased by making R_6 approximately $\alpha \times R_4$. One must, however, ensure that A_2 can deliver the correspondingly large peak output voltage.

The design of $RV_{1\text{-}4}$ and $RV_{5\text{-}8}$ is not critical if the measuring techniques adopted are to be of the "scale-free" sort described below.

If accuracy is required, mechanical linkages can be designed to make linear potentiometers follow the required sinusoidal law. For most purposes, however, it is sufficient to obtain "3-point" correction by a device such as that shown in Fig. 6.

If the complete range of RV corresponds to angles from 0° to 90°, the ratio in the half-way position corresponds to an angle of 45°, and should ideally have a value sin 45° or 0.707. This can be arranged by connecting a shunt resistance R_5 as shown, with a value approximately $\frac{5}{8} \times RV$. Where a load resistance such as R_7 is present, R_5 can easily be modified to allow for its effect. In general, for a ratio of 0.7 at 45°,

$$R_5 = 3RV/\ 8 + 14(RV/R_7)$$

It should be mentioned that somewhat expensive continuously-rotating sine-cosine potentiometers exist, with centre-tapped elements and facilities for extracting both sine and cosine fractions of the applied voltage. A push-pull input is required (relative to centre-tap). Using these, one is no longer restricted to one quadrant of view, (though, of course, all other quadrants provide only replicas or mirror images of the first).

Again, if push-pull signals are available, there is no reason why ordinary centre-tapped linear potentiometers should not be used to give 180° rotations if desired. The example described here is merely the simple one which the author has found adequate for electronic computation work and class lectures, and is by no means exhaustive of the possibilities.

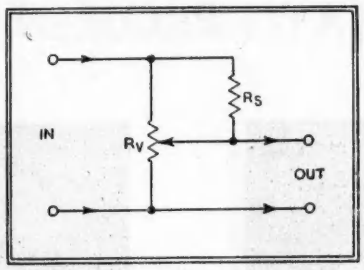

Fig. 6. "3 point" correction circuit

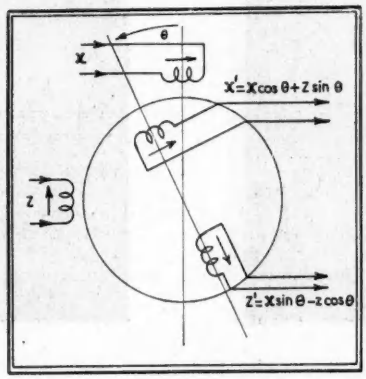

Fig. 7. A magslip resolver

The use of magslip resolvers will only briefly be mentioned, as their frequency-characteristics make them unsuitable for general-purpose work, and in particular they are incapable of resolving steady or low-frequency potentials.

In one form, illustrated in Fig. 7, two windings at right angles produce magnetic fields proportional to x and z. Two rotating coils, also at right angles, have voltages induced in them proportional to $x\cos\theta + z\sin\theta$, and $x\sin\theta - z\cos\theta$, respectively, where θ is the angle shown.

Thus one unit performs all the operations required for a given rotation—a strong point in favour of magslips when the nature of the voltages x, y and z makes it possible to use them. Their sine-cosine law is very accurately followed, and they are, of course, capable of continuous rotation.

Perspective

There is one remaining ambiguity which we have not yet removed—a rather more subtle one. A pattern such as Fig. 8(a) can be pictured in two ways—one with AB nearer to the observer than CD, the other with AB farther away. Both are equally justifiable views. In other words, "turning the pattern inside out" makes no difference. What it lacks is *perspective*, the property by which receding parallel lines appear to converge. Thus, Fig. 8(b) on the other hand leaves us in no doubt that CD is behind AB. What we have to do is to make the *scale* of our picture vary with the *depth*, which is in our case the "unseen" co-ordinate z''.

In practical terms, we must contrive to adjust the deflexion-sensitivity of our display (or, what amounts to the same thing, the gain of our x' and y' amplifiers) in sympathy with z''. Fig. 9 illustrates this. We wish to display a point P which has an X'-co-ordinate x' and is nearer to the observer E (co-ordinate z_e) than the origin O by an amount z''. Since, however, our display is all in one plane $OX'Y'$, the point P is actually represented by a point P', the projection of P from E, on the $X'Y'$ plane. The X'-co-ordinate of P' must therefore be, not x', but:

$$x' \times z_e(z_e - z'')$$

The simplest method of modulating x' in this way is to control the accelerating voltage of the C.R. tube. Since the sensitivity in an electrostatic tube is inversely proportional to the accelerating voltage V, the effect of subtracting a voltage $\alpha \times z''$ from V is exactly what we require, if we make $\alpha = V/z_e$.

For example, if the observer is 3 ft. away, and if the picture-scale is 1 ft. per 1,000 volts, then $\alpha = V/3$ where V is in kilovolts.

Two points of detail may need attention:

The *focus* of an electrostatically focused tube remains unaltered only if the ratio of potentials applied to the gun is kept constant. It is desirable therefore to apply $\alpha.z''$ not merely to the accelerating anode, but to the whole potential-divider feeding the gun, as indicated in Fig. 10(a). C_1 and C_2 are small capacitors chosen to maintain the ratio at high frequences. With electrostatic deflexion, astigmatism may be troublesome, and it is preferable to feed $\alpha.z''$ into the C.R. tube circuit via the last H.T. smoothing capacitor (Fig. 10(b)).

Similar considerations apply to magnetically deflected tubes, but the sensitivity is then inversely proportional to $\sqrt{V}$, so that the law is less exactly followed.

McKAY . PROJECTIVE

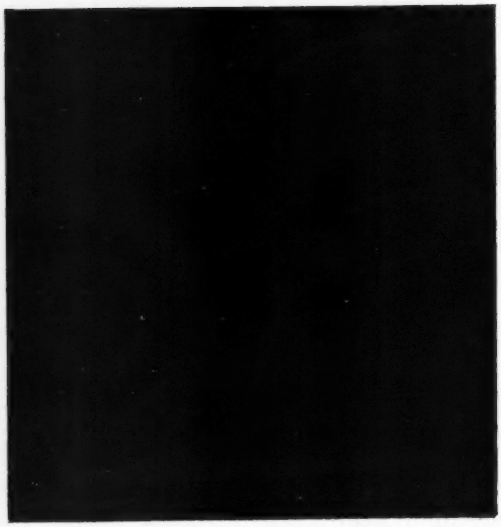

Fig. 4 (a).

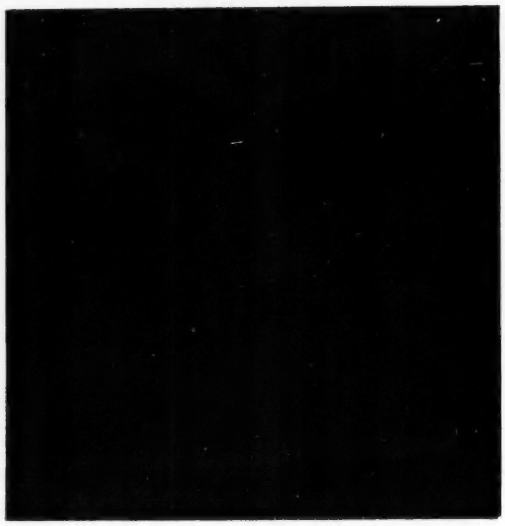

Fig. 4 (b).

Fig. 4. Three elevations of a surface $y=f(x, z)$
(a) Along X-axis
(b) At 45° to X— and Z-axis
(c) Along Z-axis

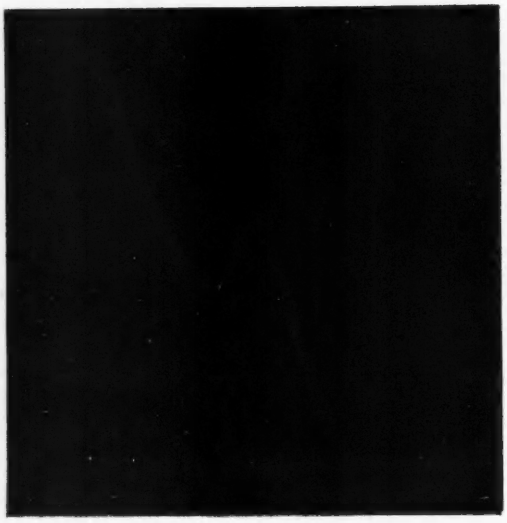

Fig. 4 (c)

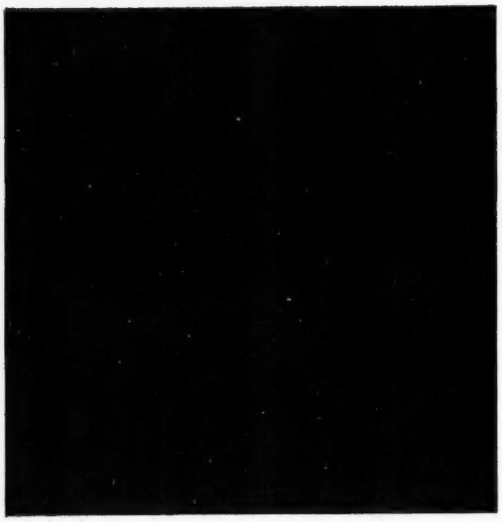

Fig. 19 (a).

THREE-DIMENSIONAL DISPLAYS

Fig. 19 (b).

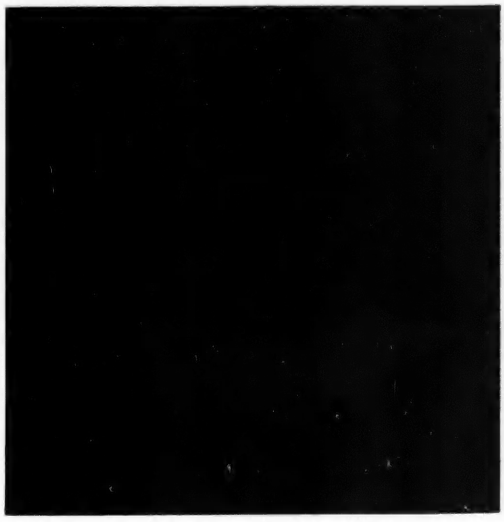

Fig. 19 (c).

Fig. 19. Five stages in the development of a secondary-emission " valley " in the characteristic surface of a tetrode

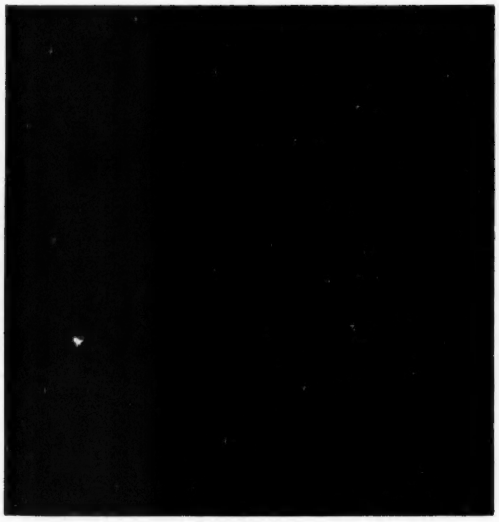

Fig. 19A(d).

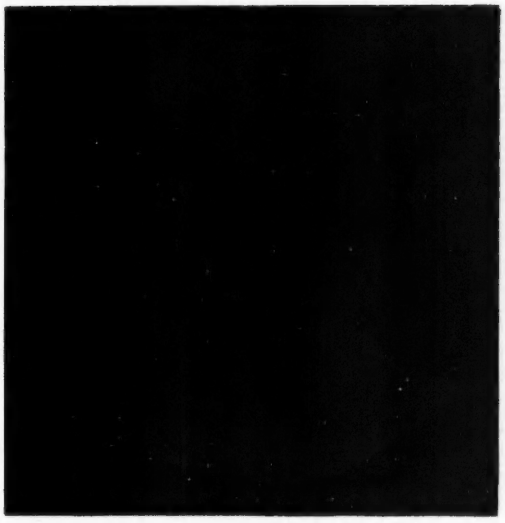

Fig. 19 (e).

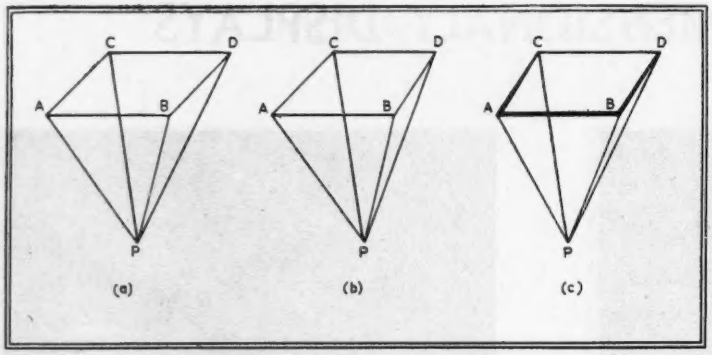

Fig. 8 (a) (b) and (c). The problem of perspective

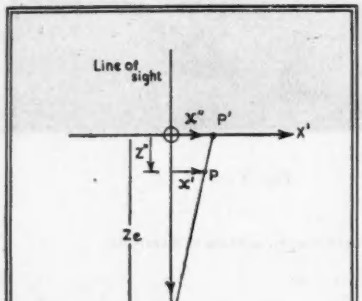

Fig. 9 (above). A point P (x', Z"), is seen by the eye E (O, Ze) as a point P' on the X' axis at a distance $x'' = \left(\frac{Ze}{Ze-Z''}\right) x'$ from O

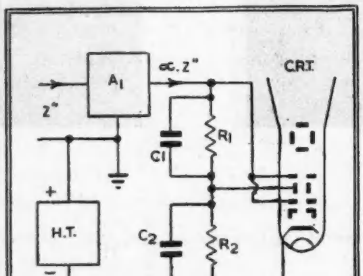

Fig. 10. (a) above and 10 (b) and (c) below. Three methods of obtaining perspective convergence

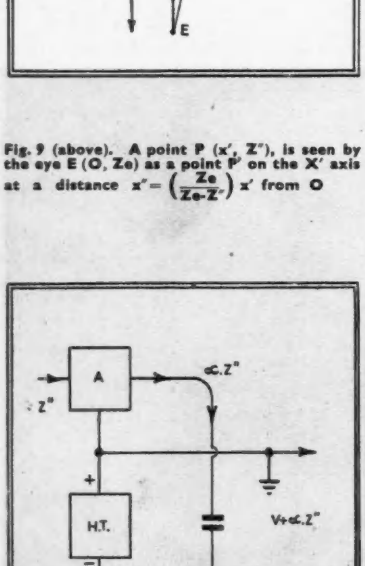

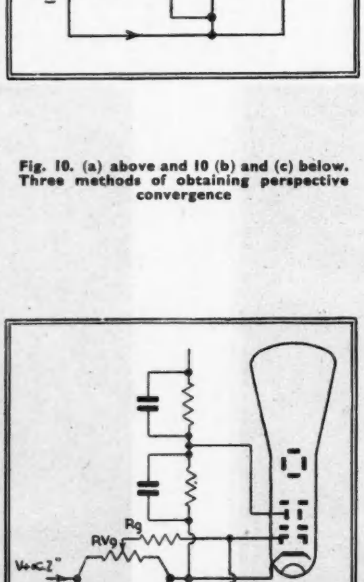

The *brightness* of the trace will tend to increase with accelerating voltage, making the more distant portions of the picture appear brighter. To counteract this it is simplest to feed a fraction of z'' to the grid circuit of the C.R. tube, so as to increase the bias as z'' increases. One way of doing this is shown in Fig. 10(c). Here RV_9 controls the standing grid bias, while RV_{10} controls the fraction of the modulation appearing, via C_g, between grid and cathode.

The last point brings us to a second method of dealing with the ambiguity of Fig. 8(a), which is illustrated in Fig. 8(c). If we can arrange to brighten the parts of the picture which are nearer, the eye seems to be quite deceived. (Fig. 8(c) is identical in structure with Fig. 8(a), but the enhanced brightness of AB leaves us in little doubt that CD is farther away.

In many cases this method alone is sufficient to remove ambiguity, and is considerably simpler to achieve than the first, since grid-modulation can be applied directly, and z'' requires only to be attenuated.

The two methods in combination are, of course, still more effective, and can be applied, for example in Fig. 10(c), simply by "over-compensating" on RV_{10}.

Stereoscopic Displays

We shall not consider here in detail the addition of stereoscopic vision to projective displays, which is rather outside the scope of the present paper. Fundamentally the problem involves the presentation of two projections from slightly different points of view, either alternately on one tube, or on two tubes with their screens optically superposed. Means must then be provided to ensure that the left eye sees only the one (left-hand) view, while the right eye sees only the other.

(To be continued)

REFERENCES

Parker, E. & Wallis, P.R.J., *Inst. Elec. Eng.*
[2] Parker, Wallis & Woroncow, *Brit. Prov. Pat. App.* 9942/46, 30/3/46.
[3] *Dumont Lab. Engg. Report No.* 92, 20/9/46.
[4] Schmitt, O. H., *J. App. Phys.* 18, p. 819, 1947.
[5] See, for example, *I. E.. Radar Convention Papers* 1946.

The Electromagnetic Horn

—Part 1

By W. D. OLIPHANT *

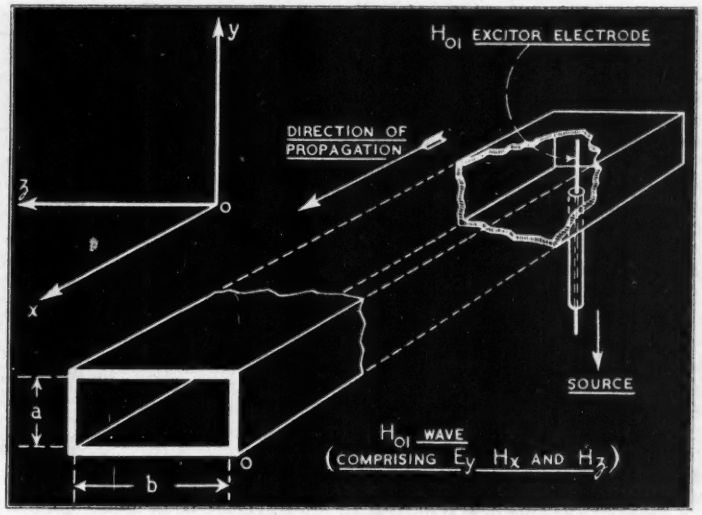

Fig. 1 Rectangular Hollow Tube Wave Guide. (Relevant Dimensions and axes of reference)

EARLY theoretical analyses[1] had indicated the possibility of propagating electromagnetic waves along dielectric wires and through hollow conducting tubes, but only recently has the practical realisation and importance of the subject been demonstrated. This has been made possible by the means for generating frequencies of the order of 300 Mc/s. and upwards, when the physical dimensions of the guide apparatus come within practical laboratory limits.

Transmission phenomena in dielectric wires and through conducting tubes are entirely different in themselves and they also differ from normal free-space wave propagation and from propagation along lines or cables. The properties of hollow-tube wave guides, and in particular those of rectangular and circular section, have received considerable theoretical and practical investigation, and a selection of the published papers is given [2, 3]. Natural extensions of the subject are the cavity resonator and the electromagnetic horn, the former providing a means for utilising the phenomenon of resonance and of replacing the familiar tuned circuit at hyper-frequencies, and the latter providing a means for radiating or absorbing electromagnetic energy in a highly directive manner and thus of replacing the orthodox aerial array and its associated reflector system. The present paper will deal with the theory and practice of the electromagnetic horn primarily as a radiator of energy, but, in accordance with the general theorem of reciprocity, the inverse property of energy absorption is understood everywhere to apply.

Basically, an electromagnetic horn is the open end of a hollow tube wave guide wherefrom the guided waves are launched into free space and the radiation pattern depends on the configuration of the guide end. It will be shown that, by flaring the open end into a horn structure of suitable dimensions, the radiation efficiency and directivity may be considerably increased and secondary lobes and other spurious effects, such as backward radiation, reduced to a negligible amount. By comparison with other highly directive aerial systems at hyper-frequencies, the horn compares very favourably and its inherent simplicity, both constructionally and operationally, indicate considerable advantage in its use.

The action of the flared mouth may be regarded as providing an approximate impedance match between the guide and the external medium, and in this way, subject to considerations associated with the relation between wavelength and physical dimensions, it may be compared with its dynamical analogue, the acoustic horn. The precise horn

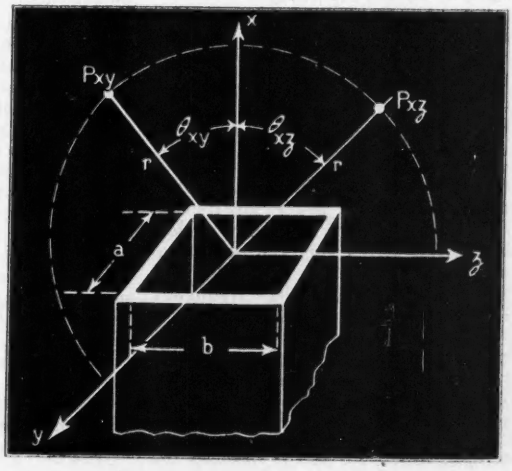

Fig. 2. Rectangular tube guide radiation (co-ordinate system at open end)

* Research Dept. Messrs Ferranti Ltd., Edinburgh

configuration is dependent primarily on the guide section to which it is attached, and, of the rectangle and circle, the former presents the simpler construction and it, at the same time, makes possible the radiation of a true linearly polarised wave. The flare may be produced in two directions to form a pyramidal horn, or in one direction only to form a sectoral horn. The characteristics of such horns will be developed step by step, commencing with the rectangular hollow tube wave guide.

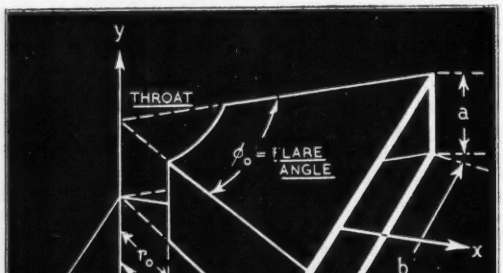

Fig. 3. The sectoral Horn

Part I.—Theoretical Considerations

Guided Waves in Conducting Tubes of Rectangular Section

The guided wave in a non-dissipative twin wire or concentric feeder possesses a field which is wholly normal to the axis of the system; that is to say, the axial components of the E (electric) and H (magnetic) intensities of the wave are zero, and the system will transmit waves of all frequencies with the same phase velocity. In the hollow conducting tube, on the other hand, there must always exist an axial component of either (or sometimes both) the E or H intensities. In accordance with the accepted notation, a tube-guided wave possessing both a longitudinal and transverse component of the E field but only a transverse component of the H field is called an E-wave or transverse magnetic wave (TM-wave). A wave possessing both a longitudinal and transverse component of the H field but only a transverse component of the E field is called an H-wave or transverse electric wave (TE-wave).

In each case there exists a fundamental wave denoted by E_o or H_o, and, in addition, geometric harmonic waves wherein the nth harmonic is denoted by E_n or H_n. Furthermore, the harmonic waves are extended in "order"; thus the nth harmonic wave of mth order is designated E_{nm} or H_{nm}. Each wave, of whatever type, harmonic or order, has its own critical or cut-off frequency below which the waves are rapidly attenuated and above which they are freely transmitted. This critical frequency is governed by the tube dimensions. A tubular wave guide thus exhibits the properties of a high-pass filter, and in the transmission band introduces considerably less loss than do the parallel wire or coaxial cable counterparts.

A typical rectangular hollow tube wave guide with relevant dimensions and axes of reference is shown in Fig. 1, and it is assumed for present purposes that the guide is non-dissipative. The type of guided-wave which possesses the most outstanding properties is the fundamental transverse electric wave of the first order—the H_{01} wave—and attention will therefore be confined to it alone. This type of wave is characterised by an E field intensity which is normal to the direction of propagation (x-axis) and parallel to the side a (y-axis). The intensity distribution along the z-axis is a half-period sinusoid, the maximum value occurring at the centre of the section. When the open-ended tube is employed as a radiator of energy, this intensity distribution produces a displacement current sheet across the mouth whose current elements are all parallel and of equal phase, and which therefore all produce similarly polarised component space waves. The resultant space wave is thus vertically polarised and the radiation characteristic is a single-lobe beam. Other practical advantages of the H_{01} wave include the lowest critical or cut-off frequency for a given section of guide and negligible attenuation which decreases with increase in frequency. Furthermore, its use calls for a minimum of material in the construction of the guide, as will presently be shown.

The excitor electrode is positioned at the closed end of the tube to coincide with a line of electric intensity in the field pattern and the optimum position can best be obtained by making the closed end in the form of a movable piston reflector which maintains a high conductivity joint around its periphery. The length of the excitor electrode should also be capable of adjustment so as to provide a correct impedance match between the guide, excitor and concentric feeder connecting with the source.

For a rectangular hollow tube wave guide, it can be shown that the critical wavelength (λ_o) is given by the simple relation:

$$\lambda_o = 2b \quad \ldots\ldots\ldots\ldots\ldots\ldots \quad (1)$$

and the cut-off frequency (f_o) by

$$f_o = c/2b \quad \ldots\ldots\ldots\ldots\ldots\ldots \quad (2)$$

where c is the free space-wave velocity $= 3 \times 10^{10}$ cm/sec.

In terms of the free space excitation wavelength (λ_e), the wavelength in the tube (λ_t) is given by

$$\lambda_t = \lambda_o / M \quad \ldots\ldots\ldots\ldots\ldots\ldots \quad (3)$$

where

$$M = \left[1 - \left(\frac{\lambda_e}{2b}\right)^2\right]^{\frac{1}{2}} \quad \ldots\ldots \quad (4)$$

The interesting point to note is that the critical wavelength is not dependent on the dimension a which is parallel to the electric vector E_y and so the tube may be made of small cross-sectional area provided only that Equation (1) is satisfied and that adequate space is available for the insertion of a suitable excitor electrode. For a given operational wavelength the H_{01} wave thus requires less material in the guide construction than would be the case for a circular or square section tube required to transmit any of the possible wave types.

From Equation (3) it is evident that $\lambda_t > \lambda_e$ and thus the phase velocity in an air-filled tube is always greater than that in free space. The value of the phase velocity is given by

$$v_p = c/M \quad \ldots\ldots (5)$$

and this approaches the value c when λ_e becomes small compared with $2b$ or λ_c.

In transmission line practice it is customary to express the general property of the line in terms of its characteristic impedance, and appropriate impedance expressions may be derived on a power or a current-voltage basis for a hollow tube wave guide. In problems associated with radiation, where the essential quantity is field intensity, a quantity (Z_o), symbolic of impedance, is given by

$$Z_o = \mu c/M \quad \ldots\ldots (6)$$

where μ is the magnetic permeability of the medium within the tube, and in the case of air this has a value $4\pi \times 10^{-9}$ henry/cm.

For a plane wave in free space the corresponding value is

$Z_o = \mu c = 377$ ohms, and it can be seen that this value is approached in Equation (6) as b becomes considerably greater than the excitation wavelength λ_e. Thus by flaring out the end of the tube in the direction of the z-axis, it is possible to approach an impedance match between the guide and the external medium. The horn structure, apart from directivity considerations, may thus be regarded as a non-uniform hollow tube guide with impedance matching properties in the same manner as the non-uniform transmission line.

Rectangular Tube Guide Radiation

The H_{01} wave launched by the excitor electrode (Fig. 1) will travel along the tube to the open end when the greater part of the wave energy will be radiated into free space: only a small part of the energy will be reflected back along the tube.

The properties of this simple form of radiator have been investigated both theoretically and practically by Barrow and Greene[4] who derive expressions for the horizontal and vertical field characteristics for a fundamental transverse electric wave of any order (H_{om}). The equations here given are simplified in virtue of the fact that only the first order wave is being considered, and the co-ordinate system adopted is shown in Fig. 2.

The relative magnitude of the electric intensity normal to the radius vector r, which is large compared with the excitation wavelength (λ_e) and with the guide dimensions, in terms of the angle θ (referred to the x-axis or direction of propagation) is given by the following two equations:

(a) Vertical characteristic (xy-plane for points P_{xy}).

$$E_{\theta(xy)} = C \left| (\cos\theta + M).\frac{\sin A}{A} \cos\theta \right| \quad \ldots\ldots (7)$$

(b) Horizontal characteristic (xz-plane for points P_{xz}).

$$E_{\theta(xz)} = C \left| (\cos\theta + M).\frac{\cos B}{B^2 - [\frac{1}{2}\pi]^2} \right| \quad \ldots\ldots (8)$$

where

$$\left.\begin{aligned} A &= \pi W_v \sin\theta \\ B &= \pi W_h \sin\theta \\ W_v &= \text{vertical aperture} = a/\lambda_e \\ W_h &= \text{horizontal aperture} = b/\lambda_e \end{aligned}\right\} \quad \ldots\ldots (9)$$

and M is given in Equation (4).

The quantity C is a comprehensive constant taking into account the excitor current and frequency, the size of the tube and the value chosen for the radius vector about which the field intensity is being explored; in short, C does not influence the relative field distribution provided the factors just cited do not vary.

From Equations (7) and (8) the first minima are found to occur when

$$\theta_{xy} = \sin^{-1}\frac{1}{W_v} \text{ and } \theta_{xz} = \sin^{-1}\left(\frac{3}{2W_h}\right)$$

and so the vertical and horizontal beam angles are given by

$$\left.\begin{aligned} \theta_v &= 2\sin^{-1}\frac{1}{W_v} \\ \theta_h &= 2\sin^{-1}\frac{3}{2W_h} \end{aligned}\right\} \quad \ldots\ldots (10)$$

since the field configurations are symmetrical about the x-axis.

For equal apertures the beam will thus always be sharper in the vertical plane than in the horizontal, being in ratio of 2:3. In general, any values of beam angle may be provided for by suitable choice of W_v and W_h, that is to say, of a and b.

In the operational limit when the tube is functioning at its critical wavelength, then $\lambda_e = 2b$, hence $W_h = \frac{1}{2}$ and $B = \frac{1}{2}\pi.\sin\theta$; this Equation (8) reduces to:

$$E_{\theta(xz)} = C \left| \frac{\cos(\frac{1}{2}\pi.\sin\theta)}{\cos\theta} \right| \quad \ldots\ldots (11)$$

which is almost a circle possessing a major axis in the direction of propagation.

Again, when $a \to 0$, then $W_v \to 0$ and so $A \to 0$, giving rise to a limiting value for the vertical characteristic in the form

$$E_{\theta(xy)} = C \mid (\cos\theta + M)\cos\theta \mid \quad (12)$$

and if in addition the critical wavelength is also reached, then $M = 0$, and so in the double limit

$$E_{\theta(xy)} = C.\cos^2\theta \quad \ldots\ldots (13)$$

Such an examination of the basic equations given at (7) and (8) reveals the manner in which the directive radiation pattern is dependent not only on the physical dimensions of the guide orifice but also on the operational wavelength. In general, it may be stated that for a sharp beam in the horizontal plane (the usual practical requirement), the operational wavelength should be considerably less than the cut-off wavelength, which is another way of stating that the horizontal width of the guide orifice should be large compared with the operating wavelength.

In the previous section, impedance match was seen to be approached by flaring the horizontal tube dimension, and in the present section such flaring also indicates a sharpening of the horizontal beam characteristic. It is now necessary to see how these qualities are achieved by the fitting of an actual horn structure to the end of the hollow tube guide or of the use of a finite length of non-uniform hollow tube guide.

The Sectoral Horn

The relevant dimensions of a sectoral horn, together with the axes of reference, are shown in Fig. 3. The material of the horn, like that of its parent tubular guide, is of high conductivity, at any rate as far as the inner surface is concerned.

The horizontal and vertical apertures are defined in terms of the wavelength and mouth dimensions in accordance with Equations (9), but in addition there exists a relative radial "length" (x_r) and cut-off "length" (x_o) defined by the equations.

$$\left.\begin{aligned} x_r &= r_1/\lambda_e \\ x_o &= r_o/\lambda_e \end{aligned}\right\} \quad \ldots\ldots (14)$$

Such a conductive structure may be excited either by attaching a

hollow tube-feed to the throat or by direct excitation when the excitor electrode, backed by an adjustable reflector, is inserted into the throat region. For wavelengths of the order of 20 cm. or less the former method is recommended, while the latter is reserved for the longer wavelengths; in either method of excitation substantially the same radiation field characteristics prevail subject to certain dimensional requirements dependent on horn-wave propagation. For purposes of radiation analysis, the field distribution across the mouth is taken to be the same as that across the appropriate section of a similarly flared horn of infinite radial length when end effects are absent; the ideal mouth distribution is thus the same as that produced by the H_{01} wave in the guide radiator.

In the tubular guide the wavelength (λ_t) was greater than that in free space (λ_o) and, as is to be expected in the case of horn-wave propagation, the wavelength at the throat end is much greater than that at the mouth end, and there thus exists a crowding of the H-lines with attendant high field intensity in the vicinity of the throat. In the throat region the waves suffer a high degree of attenuation, while further along the horn they encounter little or no attenuation, and it is customary to think in terms of an attenuation region and a transmission region through which the waves must pass. The horn, in effect, acts as a specialised form of guide for electromagnetic energy, allowing it to spread out in such a manner as to create a transverse wave across the relatively large boundary surface at the mouth.

In the attenuation region (small r), the phase constant β is very small compared with its free space value of $2\pi/\lambda_o$, while in the transmission region (large r) β is practically equal to the free space value.

For a fundamental transverse electric wave of any order (H_{0m}) the attenuation constant (α) and the phase constant (β) for the attenuation region are given approximately by [5]

$$\left.\begin{aligned} \alpha &= \frac{m\pi}{\phi_o r} \\ \beta &= \frac{2\pi}{\lambda_o}\left\{\pi\left[\left(\frac{m\pi}{\phi_o}-1\right)!\right]\right\}^{-\frac{2}{\left(\frac{\pi r}{\lambda_o}\right)^{2\pi m/\phi_o - 1}}} \end{aligned}\right\} \quad \ldots\ldots (15)$$

where r is the radial distance measured from the apex or origin in the xz-plane.

Similarly, for the transmission region the approximate relations are:

$$\left.\begin{aligned} \alpha &= 1/2r \\ \beta &= 2\pi/\lambda_o \end{aligned}\right\} \quad \ldots\ldots (16)$$

The line of demarcation between the attenuation and transmission regions is not well defined, but it is evident from the first of Equations (15) that the radial distance to which the attenuation region extends increases with wave order and with decrease in flare angle. For a given flare angle the horn therefore presents the properties of a wave-order filter tending to suppress the higher order in favour of the lower order waves.

The phase velocity (v_p) and wavelength (λ_h) within the horn are given by

$$\left.\begin{aligned} v_p &= \omega/\beta \\ \lambda_h &= 2\pi/\beta \end{aligned}\right\} \quad \ldots\ldots (17)$$

The group velocity (v_g) in the case of any wave propagation in air or vacuo is given in terms of the phase velocity in accordance with the equation

$$v_g = c^2/v_p \quad \ldots\ldots (18)$$

Thus, since the phase velocity in the throat is larger than c it follows that the throat group velocity is less than c. As the horn wave progresses radially, the phase velocity decreases, while the group velocity increases, until at the mouth they are both equal to the free space wave velocity c.

The above theory applies generally to a horn which extends radially to infinity, but in practice it may also be taken to apply to a horn of finite length. For purposes of radiation, the mouth is taken to be several wavelengths beyond the attenuation region, thus calling for an overall relative "length" (x_r) of the order of about 8 to 10; in addition the flare angle is limited to a maximum value of 90°.

In calculating the field distribution, the radiation is taken to originate from the displacement current sheet across the mouth in precisely the same manner as was done in the case of the guide radiator. As far as the vertical characteristic (xy-plane) is concerned, the radiation conforms with the configuration given in Equation (7), being independent of the flare angle. The rigorous mathematical analysis for the horizontal characteristic (xz-plane) is distinctly involved and can be found elsewhere,[5] but for flare angles not greater than 50° the expression already given in Equation (8) may be employed to a high degree of practical accuracy provided the horizontal aperture is of the order of 3. For flare angles greater than 50° the experimentally observed lobes are broader than those obtained theoretically by the use of Equation (8) and the discrepancy increases rapidly with increase in flare angle. Thus within the 50° limit, the beam angle (θ_h) may also be computed as for a tube radiator.

In assessing the behaviour of a horn as a radiator, apart from its directive qualities, the relative power gain is taken as a measure of its effectiveness. By relative power gain is meant the ratio of the power radiated by a simple dipole to that radiated by the horn to produce the same E-field strength at a fixed point on the principal axis (x-axis) distant many wavelengths from the origin. The power gain is found to be dependent on the flare angle for a given fixed radial length and is also proportional to the vertical aperture (W_v) and relative radial "length" (x_r).

(To be continued)

References

[1] Heaviside, "Electric Papers," p. 443 (1892).
"Electromagnetic Theory," vol. 1, p. 399 (1893)
Rayleigh, "On the Passage of Electromagnetic Waves through Tubes or the Vibrations of Dielectric Cylinders," *Phil. Mag.*, *43*, 125 (1897).
"Scientific Papers," vol. 4, p. 227 (Oxford 1897)
Thomson, "Recent Researches in Electricity and Magnetism," p. 344 (Oxford, 1893).

[2] Adams & Page, "Electromagnetic Waves in Conducting Tubes," *Phys. Rev.*, *52*, 647 (1937).
Barrow, "Transmission of Electromagnetic Waves in Hollow Tubes of Metal," *Proc.I.R.E.*, *24*, 1298 (1936).
Carson, Mead & Schelkunoff, "Hyper-frequency Wave Guides—Mathematical Theory," *B.S.T.J.*, *15*, 310 (1936).
Clavier, "Theory of Cylindrical Dielectric Wave Guides and Coaxial Cables," *Bull. Soc. des Elec.*, *8*, 255, (1938).
Southworth, "Hyper-frequency Wave Guides—General Considerations and Experimental Results." *B.S.T.J.*, *15*, 284 (1936)..
"Some Fundamental Experiments with Wave Guides," *Proc. I.R.E.*, *25*, 807 (1937).
"New Experimental Methods Applicable to Ultra-Short Waves," *Jour. App. Phys.*, *8*, 660 1937).

[3] Barrow & Chu, "Electromagnetic Waves in Hollow Metal Tubes of Rectangular Cross-section." *Proc. I.R.E.*, *26*, 1520 (1938).

[4] Barrow & Greene, "Rectangular Hollow Pipe Radiators," *Proc.I.R.E.* *26*, 1498 (1938).

[5] Barrow & Chu, "Theory of the Electromagnetic Horn," *Proc. I.R.E.*, *27*, 51 (1939).

Panoramic Display — Design Considerations *

By DONALD W. THOMASSON †

"PANORAMIC Display" is the general name covering a very useful type of oscilloscope. Whereas, in the ordinary way, one of the dimensions of the diagram produced is in a scale of time, in a panoramic display, the corresponding dimension is in a scale of frequency. The variation of the second variable may therefore be observed over a wide range of frequency, as in a "panorama" of the range.

Without the use of panoramic technique, the observation would entail a large number of separate measurements at different frequencies, the results being plotted as a graph. This is, at best, a laborious process, and has other disadvantages.

In the panoramic display, the frequency of measurement is swept continually through the required range, and the motion of the spot on the C.R. Tube screen in one axis is related to the variation of frequency. Each point on that axis is therefore corresponding to a certain frequency.

The second variable is made to control the motion of the spot in the other axis, so that the graph obtained by the "static" technique, mentioned above, is continuously visible on the screen.

Types of Display

There are two basic types of display. In the passive type (Fig. 1), the second variable is an externally generated signal, or signals, and the voltage and frequency of the various components are displayed as vertical lines whose position indicates frequency, and whose height indicates voltage. Examples of the passive type include the panoramic receiver and harmonic analyser.

The active type (Fig. 2), generates the observed signal itself, and displays the effect of an external circuit on the signal. This produces a "response curve" of the circuit, as in the "Wobulator" type of alignment generator.

Essential Features

The essential features of the apparatus required for producing a panoramic display are: the oscilloscope unit, the variable frequency oscillator and a circuit having a finite acceptance band.

In the passive display, the "circuit with a finite acceptance band" is generally in the form of an I.F. amplifier. In the active display, it is the circuit under test, with special reference to any peaks in the response of that circuit.

Whatever the circuit is, the frequency of the input signal fed to it will sweep across the acceptance band. It is this fact that gives rise to the inherent limitations of the technique.

Limitations

General Basis.

"If the frequency of the input to a circuit having a finite pass band is varied across that pass band, distortion of the output will occur if the time taken to cross the pass band is less than the reciprocal of half the band-width."

This is fundamental, and no proof will be given here. The basis of the rule can be seen if the response is assumed to cause amplitude modulation of the applied signal. In practice, the results are in close agreement with the rule.

It may be expressed:

$$w = \sqrt{\tfrac{1}{2}\frac{df}{dt}} \quad \ldots\ldots\ldots\ldots\ldots\ldots (1)$$

Where the width of the acceptance band is $2w$ c/s., and $\frac{df}{dt}$ is the rate of change of frequency.

Linear Scale.

If the motion of the spot in the frequency axis follows the usual saw-tooth form, with negligible fly-back time, and the change of frequency within a given time is proportional to the movement of the spot, a linear frequency scale will be produced.

If the sweep repetition frequency is s c/s., and the band swept is b c/s. wide, $\frac{df}{dt} = sb$, and:

$$w = \sqrt{\frac{sb}{2}} \quad \ldots\ldots\ldots\ldots\ldots\ldots (2)$$

Resolution.

The "electrical resolution" (r) of the display is defined as $2w/b$, and is a measure of the degree of accuracy (see Fig. 3). A small resolution indicates high accuracy. Values between 0.03 and 0.003 are satisfactory for most purposes. Substitution of the definition in

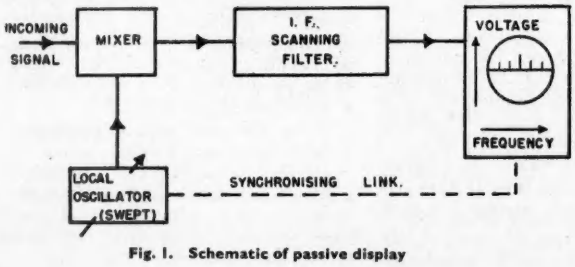

Fig. 1. Schematic of passive display

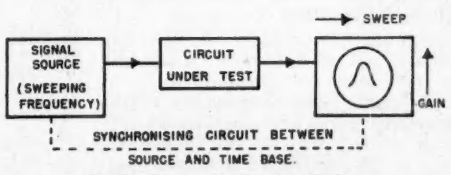

Fig. 2. Schematic of active display

* Based a paper presented before the Brit.I.R.E. (*J.Brit.I.R.E.* May-June 1948).

† E.A.R.L. Services, Exeter.

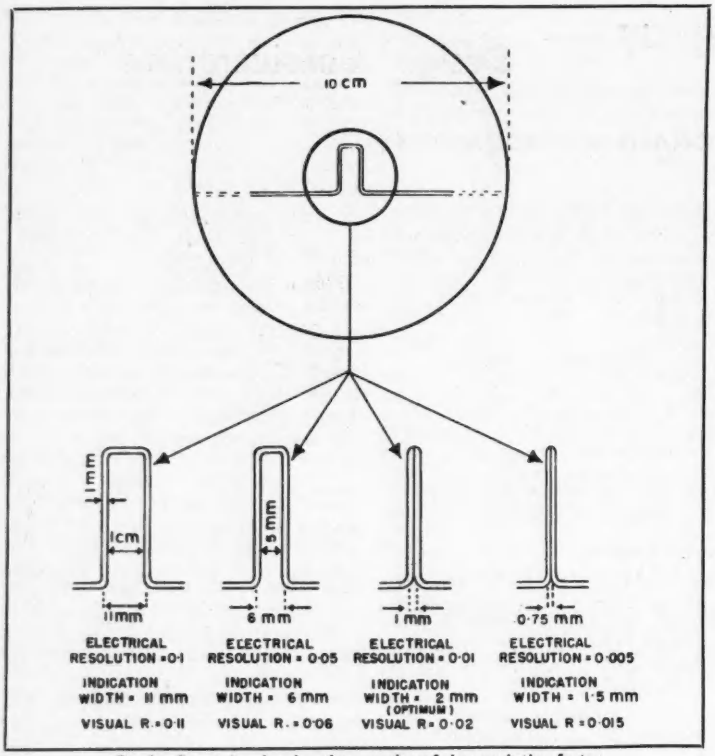

Fig. 3. Examples showing the meaning of the resolution factor

Equation 2 gives:

$$r = \sqrt{\frac{2s}{b}} \quad \ldots\ldots\ldots\ldots\ldots\ldots \quad (3)$$

An improvement in resolution therefore implies a reduction of sweep frequency or an increase in the swept band.

Selectivity.

The "selectivity factor" (n) is defined as $2w/f$, and is a measure of the degree of accuracy in respect of frequency. From Equation 2:

$$n = \frac{\sqrt{2sb}}{f} \quad \ldots\ldots\ldots\ldots\ldots\ldots \quad (4)$$

This implies a maximum swept band limit, whereas Equation 3 implied a minimum limit. Together, they imply a minimum frequency limit to the sweep:

$$f_o = \frac{2s}{nr} \quad \ldots\ldots\ldots\ldots\ldots\ldots \quad (5)$$

This should be compared with the following form of Equation 3:

$$b = \frac{2s}{r^2} \quad \ldots\ldots\ldots\ldots\ldots\ldots \quad (3a)$$

Practice.

In practice, s is limited by the nature of the screen. With an ordinary high-speed screen, s must not be less than 25 c/s., or flicker will appear. With after-glow screens, s may be reduced to 0.2 c/s.

It has been stated that r should normally lie between 0.03 and 0.003, and similar values are desirable for n. Combining these requirements with those for s, it is seen that the minimum bandwidth and the minimum frequency of the sweep are both 55.5 Kc/s. With the after-glow screen, both may be reduced to 450 c/s.

These, however, apply only when the worst usable values of r and n are employed. A resolution of 0.03 corresponds to the reading accuracy obtainable with a C.R. Tube having a screen 3 cm. in diameter and a spot 1 mm. in diameter. It should be noted that 0.03 is the electrical resolution, and that the visual resolution would be 0.06 if this size of tube were used, giving a 2 mm. indication width.

With a more useful resolution $r = 0.01$ (10 cm. screen, 1 mm. spot) the limit frequencies increase to 500 Kc/s. and 4 Kc/s.

Evading the Limitations.

These inherent limitations cannot be avoided, but they can be evaded. One possible solution for low frequency sweeps, or where very good resolution is required, is the use of logarithmic frequency sweep. In this, the rate of change of frequency is proportional to frequency, and the optimum value of w varies with frequency.

In the case of the passive type of display, where w is the width of the pass band of a tuned circuit, it is difficult to obtain the full advantage of logarithmic sweep. A recent American design actually varies the bandwidth of the circuit by a control voltage during the sweep, but this is a complex and difficult procedure.

For the passive display, however, another method is available. This involves "shifting" the observed band to a less restricted region by hetrodyning. The technique has been applied with success in recent experiments on vibration analysis.

Frequency Relating Circuits

The heart of any panoramic apparatus is the circuit used to relate the C.R. Tube deflexion voltage and the observation frequency. Some possible circuits will be described.

Reactance Valve.

The most familiar circuit for relating voltage and frequency is the reactance valve (Fig. 4). In this, the signal across the oscillator coil is applied across the anode and cathode of a valve, while a voltage which is 90° out of phase with this signal is fed to the grid. The anode-cathode impedance is thus substantially reactive, the magnitude of the reactance, and hence the oscillator frequency, being controlled by altering the standing bias of the valve.

The reactance valve has a limited sweep range, and the relation between voltage and frequency tends to become non-linear when large sweeps are used. It is, nevertheless, a very useful circuit.

It can be used with advantage in a beat-frequency circuit, when the controlled oscillator can operate at a frequency much higher than that required at the output. In this case, an automatic drift correcting circuit is desirable.

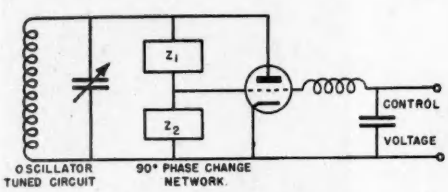

Fig. 4. Reactance valve circuit

A typical production model

For very wide sweeps, two klystrons have been used in such a circuit, the sweep being obtained by variation of the reflector voltage of one of the valves.

Resistance Valve.

Both the input and output impedance of a cathode follower depend on the mutual conductance of the valve, and can be used to control the frequency of an *R-C* tuned oscillator. It is usual to employ the output impedance, but the input resistance can be made to give a wider sweep.

The negative input resistance condition of a cathode follower can be used to couple a reactance vale to the oscillator. This avoids the resistive loading which is mainly responsible for the limitation of reactance valve performance.

Mechanical Sweep.

It is possible to control the sweep by mechanical means, such as a motor-driven tuning capacitor, but there are several disadvantages, and the method should only be used as a last resort.

If mechanical sweep is used, it is necessary to derive the deflexion sweep voltage from the frequency variation. This can be done by use of circuits of the "cycle counting" type, or by using filters with a varying attenuation over the sweep range, so that the output voltage varies with frequency.

When difficulty is experienced in obtaining a linear sweep with ordinary methods the technique of making the voltage dependent on the frequency can be used to advantage in conjunction with the reactance valve and other circuits.

Auxiliary Circuits

Marker Circuits.

Like all forms of oscilloscopes, panoramic display apparatus is best used for comparison rather than measurement. The provision of marking points on the display are valuable for comparison purposes.

In general, the marker circuits should be independent from the main display circuit, and marks in the form of bright spots are then possible. A system which has been found very useful is the provision of a number of crystal controlled spot frequencies, and a variable frequency for interpolation.

Constant Output Circuits.

The variable frequency oscillator is required to give a constant output over the whole sweep. Some form of constant output device is therefore desirable. Many circuits used for this in the normal way cannot be applied here, owing to the rapidity of the frequency variation.

The circuit which has been found of greatest use is that in which a control signal derived from the output voltage is made to control the oscillator amplitude. The selection of time constants requires considerable care.

Video Amplifier.

If amplification is used after the detector, it must respond to all frequencies between s and w c/s. In cases where this gives rise to difficulty, it is possible to avoid post-detector amplification by using a high-level detector feeding the C.R. tube directly.

Applications

Passive Types.

The panoramic receiver is fairly well known, and has especial advantages when it is necessary to monitor the signals present within a given frequency band. It is also of value for frequency comparison work.

The audio frequency equivalent is the panoramic analyser. This displays the harmonic components of the input signal, and permits very rapid assessment of amplifier performance in terms of the distortion of a square wave input. It has also been used to analyse musical notes.

Active Types.

The use of active displays for aligning band-pass tuned circuits is well known, and this technique has also been applied to the alignment of peaked circuits with success. The method is of especial value in aligning television receivers, and a variation used in this connection is to sweep the video modulation frequency of a 45 Mc/s. carrier, so that the overall video response is observed. This is the only method of aligning television receivers that does not necessitate subsequent adjustment for good picture quality.

In the audio-frequency field, active displays have been used to measure the frequency response of amplifiers, rooms, loudspeakers, microphones, etc.

Conclusion

This brief, and necessary incomplete, survey has shown something of the virtues and vices of the panoramic technique. If the design is carried out in a proper manner, panoramic display apparatus can be of great value in many branches of electronic work.

Unfortunately, many commercial products in this field are badly designed, and their failures and shortcomings are blamed on the basic technique. It is hoped that those responsible will see the error of their ways, and modify their designs to function correctly.

Grateful acknowledgments are due to the Brit.I.R.E. for permission to publish this summary of "The Principles and Practice of Panoramic Display," and for the drawings and circuits, which have been supplied by them.

Dr. J. T. Randall, Wheatstone Professor of Physics, King's College, London

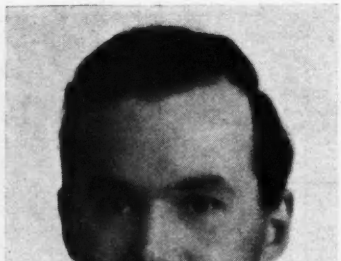

Dr. J. Sayers, Professor of Electron Physics, Birmingham University

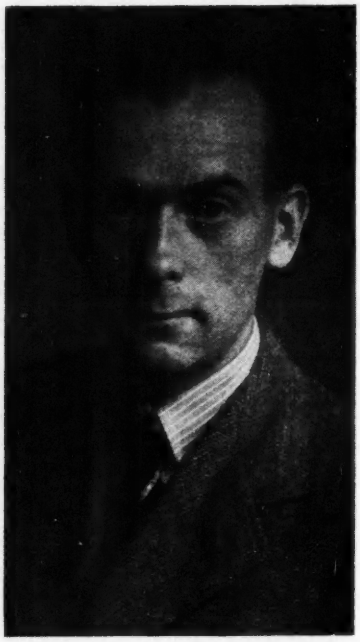

Dr. H. R. H. Boot won conducting further magnetron research for the Ministry of Supply

Magnetron Awards

READERS of this Journal will have seen with satisfaction the announcement in the Press of May 20 that the Royal Commission on Awards to Inventors has awarded £36,000 to Professor J. T. Randall, Dr. H. A. H. Boot and Professor J. Sayers, the inventors of the cavity magnetron.

Dr. Randall and Dr. Boot were members of a team under the inspiring leadership of Professor M. L. Oliphant at Birmingham University, where the original development work on the magnetron was carried out; and Dr. Sayers, also at Birmingham, initiated the strapping of the magnetron anodes.

Dr. Randall is now Wheatstone Professor of Physics at King's College, London, Dr. Boot is with a Government Research Laboratory engaged on further magnetron work, and Dr. Sayers is now Professor of Electron Physics at Birmingham University.

It is not an overstatement to say that no single contribution to the war effort changed the fortunes so profoundly as did the invention of the magnetron in the early days of 1940. At that time, the Battle of the Atlantic was at its bleakest, and shipping losses were mounting, the Germans having developed suitable counter measures to our radio detecting methods.

Almost overnight, however, the tide turned, and from then on Britain maintained a commanding lead in the detection of enemy ships and aircraft by the now familiar Radar technique. From the early magnetron-equipped radar apparatus came the host of other devices such as Gee, H_2S, Oboe and Rebecca, which conquered the submarine menace and provided the wonderful navigational devices for the R.A.F.

In these days £36,000 tax free is a lot of money, but the award is still not over generous. We join with Mrs. Randall, who is reported to have said "The award is not a surprise. We have been waiting nine years for it."

So have we! H.G.F.

NOTES FROM THE INDUSTRY

"British Trade Week" in Manitoba and Saskatchewan

The United Kingdom Trade Commissioner at Winnipeg (Mr. W. G. Coventry) has reported that the Provincial Legislatures of Manitoba and Saskatchewan have both passed resolutions calling upon the Lieutenant-Governor of each province to proclaim the week of September 26 to October 1, 1949, to be designated "British Trade Week," and requesting all traders to feature and further the sale of British goods during that week.

These actions and similar arrangements from time to time in other parts of Canada constitute most favourable conditions for United Kingdom exporters, particularly (in these instances) for consumer goods of all kinds likely to be saleable to the population of predominantly agricultural areas.

For United Kingdom firms who wish to test the market for specified products, the department will be pleased to supply the names of Canadian buyers of similar goods on application. The names of recommended agents can also be supplied (as a longer term undertaking) after consultation with the Trade Commissioners in the areas concerned.

BBC Engineering Division Changes

After 25 years service, of which the last 13 years have been spent as Head of Overseas and Engineering Information Department, Mr. L. W. Hayes, O.B.E., M.I.E.E., F.I.R.E., has resigned from the Corporation to take up the post of Vice-Director of the Comité Consultatif International des Radiocommunications in Geneva. Mr. Hayes will be chiefly concerned with the activities of the C.C.I.R. in the broadcasting and allied fields. During his service Mr. Hayes has represented the B.B.C. at nearly a hundred International Radio Conferences in all parts of the world.

The following changes in the Engineering Division of the Corporation have been made as a result.—

The Overseas and Engineering Information Department, the Engineering Secretariat and the Engineering Training Department have been formed into the Engineering Services Group. Mr. F. C. McLean, M.B.E., B.Sc., M.I.E.E., S.M.I.R.E. and Mr. E. L. E. Pawley, M.Sc., M.I.E.E., have been appointed Head and Assistant Head respectively of this Group. Mr. H. Wilkinson, B.Sc., becomes Head of Overseas and Engineering Information Department, and Mr. F. Williams, B.Sc., M.I.E.E., Head of Engineering Secretariat. Dr. K. R. Sturley, M.I.E.E., continues as Head of the Engineering Training Department.

Change of Address

Solartron Laboratory Instruments, Ltd., have removed to larger and more convenient premises at 22 High Street, Kingston-on-Thames, where they are concentrating on the research, design and manufacture of electronic instruments and test gear for research Laboratory use.

Opening of Branch Office

Air Control Installation, Ltd., announce that they are opening a branch office in Manchester and have appointed Mr. F. Wright, A.M.I.E.E., A.M.I.H.V.E., as Branch Manager. Inquiries should for the present be addressed to Mr. Wright at 1 Vale Drive, Prestwich, Manchester. Telephone: Prestwich 1653.

Cinema-Television—Dawe Instruments

The Electronics Centre, a combined showroom for Cinema-Television and Dawe Instruments, was opened on June 1. Instruments on show include atomic equipment, measuring instruments, stroboscopes, industrial counters, oscilloscopes, communications equipment, metal detectors photographic flash units, photo-electric cells and cathode-ray tubes.

Visitors will be welcome between the hours of 9 a.m. to 12.30 p.m. and 1.30 p.m. to 5.30 p.m. Monday to Friday.

The address of the Electronics Centre is 83 Piccadilly, London, W.1.

British Standard for Capacitors for Intrinsically-safe Circuits (B.S. 1551 : 1949.)

In response to a request by the Ministry of Fuel and Power, the British Standards Institution has just issued a British Standard for the construction of capacitors primarily intended for incorporation in intrinsically-safe circuits.

At the time that the Ministry of Fuel and Power's request was made, small capacitors were chiefly used as a means of spark suppression in remote control circuits which were designed to be intrinsically safe in accordance with the definition of that term given in B.S. 1259, Intrinsically-safe Electrical Apparatus and Circuits.

As an outcome of recent research, however, alternative methods of spark suppression have been found for such circuits, but there are other applications such as the coupling of an intrinsically-safe telephone circuit to the G.P.O. system. The capacitors for such a use are covered by this new standard, which deals with the dimensions of the containers and gives full details of tests.

Copies of this standard may be obtained from the British Standards Institution, Sales Department, 24 Victoria Street, S.W.1, price 2s.

Publications Received

Mullard Instruments for Research and Industry.

A list of instruments for the electrical laboratory and electrochemical and industrial equipment.

Obtainable from *Mullard Electronic Products, Ltd., Aboyne Works, Aboyne Road, London, S.W.*17.

*Redifon 5-7½ KW Transmitter Type G.*41.

Full particulars of a medium power short wave transmitter for telephony, telegraphy or broadcast services. Booklet available from *Rediffusion, Ltd., Broomhill Road, Wandsworth, London, S.W.*18.

The Ether Conqueror Radiogramophone.

Description of the series of radiograms and accessories manufactured by *Dynatron Radio, Ltd., Raylea Road, Maidenhead, Berks.*

Electrical Connectors.

A leaflet describing their products, distributed by *Films and Equipment, Ltd.*, 138 *Wardour Street, London, W.*1.

Electronic Co-ax Cables (Publication No. 27).

A brochure describing air-spaced articulated co-axial cables for radio frequencies has been received from *Messrs. Transradio, Ltd.*, 138*a Cromwell Road, London, S.W.*7.

Siemens' Engineering Bulletins No. 237 *and* 238/9.

A description of the Lisbon-Vila Franka trunk telephone cable, and power cable short circuit data respectively. Received from *Messrs. Siemens Bros. and Co., Ltd., Woolwich, London, S.E.*18.

The Twenty-ninth Annual Report of the Board, 1948.

Published by the *Institute of Physics,* 47 *Belgrave Square, London, S.W.*1.

Latest catalogue of Silvered Mica Capacitors manufactured by: Stability Radio Components, Ltd., 14 Norman's Buildings, Central Street, London, E.C.1.

"PERA and Your Production."

A 44 page brochure, well illustrated, giving information on the objects and achievements of the *Production Engineering Research Association of Great Britain, Staveley Lodge, Melton Mowbray.*

Acru Electric Tool Manufacturers, Co., Ltd., 123 *Hyde Road, Ardwick, Manchester,* 12.—A leaflet describing their new "ACRU 24" electric soldering iron.

Electronic

A monthly record of British electronic apparatus, components and accessories, compiled from information supplied by the manufacturers.

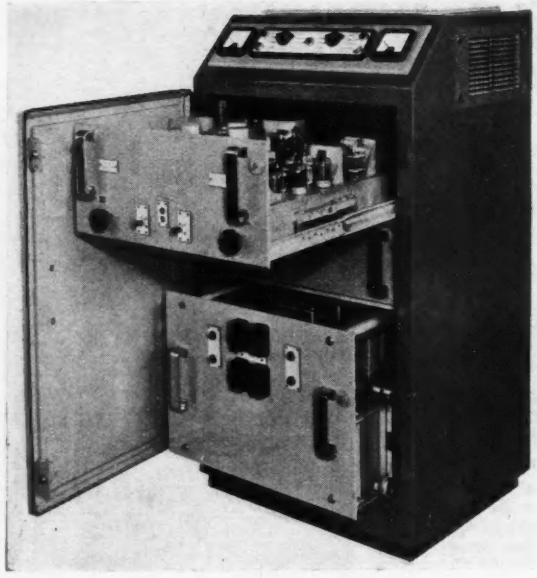

A New 50-watt V.H.F. Transmitter

(Photo above)

STANDARD Telephones and Cables Limited have produced a 50-watt V.H.F. transmitter especially suited for ground-to-air communication. The frequency range of the first models is 115-135 Mc/s., but since many other uses are envisaged for this transmitter, provision has been made to supply models to operate on a number of bands within the range of 70-150 Mc/s.

It was found that one of the features required at airports was the ability to speak through the same microphone to aircraft listening on two different frequencies, and arrangements have therefore been made whereby the operator can select at will transmission on either one or both of two frequencies. To make this possible the R.F. equipment is duplicated and the power supply equipment and modulator are designed so that they can drive both R.F. units at once. A V.O.G.A.D. (Voice-operated Gain Adjustment Device), incorporated in the speech amplifier ensures a substantially constant depth of modulation, irrespective of wide variations of input level.

The transmitter is housed in a single cabinet as shown in the photograph. It measures 3 ft. 8 in. by 2 ft. by 1 ft. 9 in., and weighs 350 lb. The equipment incorporates a meter panel which gives indications of the operating conditions and enables meter readings to be taken without the necessity for access to any of the units. Changing frequency has been made extremely simple, involving only changing a crystal and adjusting one control.

Standard Telephones & Cables, Ltd.
Connaught House, Aldwych, London, W.C.2.

Ekcovision Table Model TS105

(Photo below)

THE lowest-priced combined television and broadcast receiver has just been marketed by E. K. Cole, Ltd. It is the Model TS105, of which the Midlands version (TS1105) will shortly be available. The makers claim high sensitivity and efficient interference suppression for the television receiver, which uses a 9-inch diameter tube.

The radio section is a superhet circuit with four pre-set station positions, the selected station being shown on one of the four illuminated indicators on the front of the cabinet. The total weight is less than 45 lb.

Price : 45 gns., plus £10 15s. 0 tax.

E. K. Cole, Ltd.,
Southend-on-Sea, Essex.

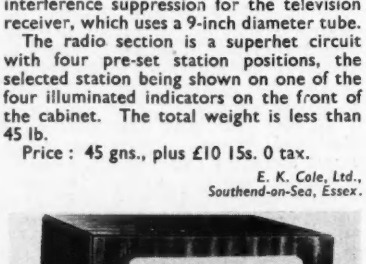

Moisture-in-Timber Meter

(Photo above)

ALTHOUGH it is well recognised that the drying-oven method is the only way of obtaining precise measurements of the moisture content of timber, there has long been a need for an instrument that would give the moisture content to a reasonable degree of accuracy within minutes instead of the hours required by a drying-oven test. Such an instrument can be of immense value in the quick examination of timber, in the forest, in the yard or during kilning.

The new Moisture-in-Timber Meter, developed by The General Electric Co., Ltd., provides exactly what is needed for unskilled personnel to carry out rapid tests on timber. All that is necessary is for the instrument to be "set" from a built-in standard and it is then ready for indicating the percentage moisture directly in terms of the dry weight, merely by pushing a small electrode fitted with four prods into the sample.

One thermionic valve is incorporated, of a type that is widely stocked by radio dealers, and the calibration of the instrument is unaffected by its replacement, should the existing one be damaged.

The tester weighs 13 lb. and is operated from self-contained dry batteries of a type that can be purchased at all large electrical dealers.

General Electric Co., Ltd.
Magnet House, Kingsway, London, W.C.2.

Equipment

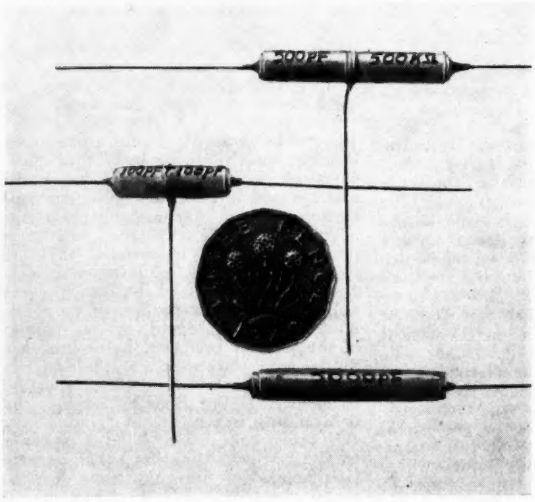

Erie Capacitor-Resistor Units

(Photo above)

THESE are combinations of capacitor and resistor elements arranged in compact mechanical form and which have various electrical combinations frequently used in modern radio and television circuits. They have the advantages of saving in chassis space, and assembly time, and the improved screening which is possible when the resistor element is enclosed by the "earthy" capacitor electrode. In addition, the concentric method of construction makes it possible to keep the inductance associated with the capacitor elements to very small values so that efficient by-passing is obtained at high frequencies.

Diode Filter

This comprises two capacitors and a resistor arranged in the form of a π filter, and has its chief function as an R.F. filter in diode demodulator circuits, and similar applications.

Values available are: 33Ω to 10MΩ and up to 100pF+100pF.

Anode and Grid Decoupler

This is an L-type filter intended for use in decoupling anode or screen-grid circuits at H.F. It may also be used as a combined coupling capacitor and grid leak by the choice of suitable values, in which case it may be advisable for the designer to consider the question of temperature co-efficient where frequency stability of the circuit is important.

Values available are: 33Ω to 10MΩ and up to 5000 pF.

Cathode Decoupler

A parallel combination of capacitor and resistor which has obvious applications as a combined cathode resistor and by-passing capacitor in the H.F. applications.

Values available are: 33Ω to 10MΩ and up to 5000pF.

Erie Resistor Ltd.,
Millora Works, South Denes, Gt. Yarmouth.

Mains Connector

(Photo below)

A NEW 2-pole 5-amp. rated mains connector is announced by A. F. Bulgin & Co., Ltd. Having the list number F.461, it may be used at 10 amps. on 6-12 volts, or 1 amp. on 500 volts. 3-pole and 6-pole varieties can also be supplied. The plug is non-reversible.

A. F. Bulgin & Co., Ltd.
Bye Pass Road, Barking, Essex.

The B.T.H. Leak Detector—Type H

(Photo above)

THE Leak Detector, Type H, detects the presence of vapours of halogen compounds (those containing chlorine, bromine, iodine and fluorine) and is applied in locating small leaks in pressure or vacuum systems. It can detect freon issuing from a container through a leak at the rate of 1/10 to 1/20 ounces per year.

This instrument is suitable for the production testing of refrigerators, freezers and air-conditioning equipment, where the apparatus under test contains a halogen-bearing compound. It is applicable also for the pressure testing of tanks, pipes, joints and welds, etc.

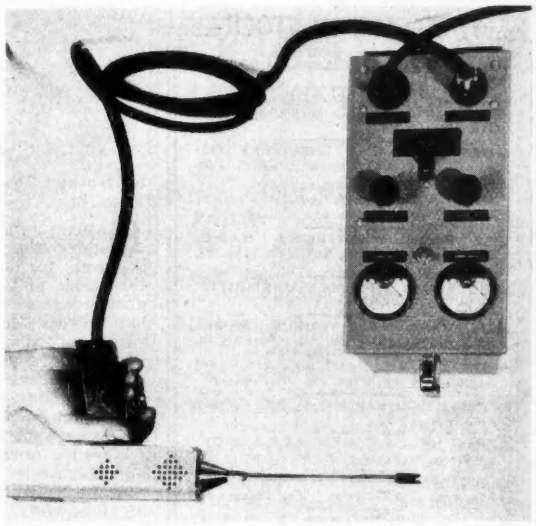

The Type H Leak Detector consists of the detector unit, control unit and the necessary leads. The detector unit is a hand-held probe with a convenient grip and a metal nozzle with plastic tip. It contains an element which is sensitive to halogen compound vapours and a blower which draws air into the detector unit.

Built into the detector is a small loud-speaker which emits a succession of clicks, of which a change in the frequency is an indication of the presence of halogen compound within the detector head. A length of cable is supplied to connect the detector unit to the control unit.

The control unit is a self-contained portable unit containing the power supply, amplifier, voltage stabilising transformer, indicating instrument and other necessary controls. A 20 ft. lead is supplied for connecting a 190 to 260 volt A.C. power supply to the control unit.

B.T.H. Research Laboratory,
Rugby.

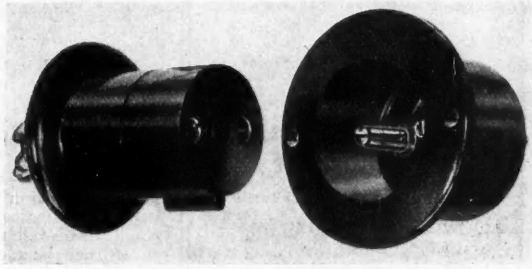

THESE ARE IN STOCK

ULTRASONICS, by Benson Carlin. 30s. Postage 9d

OUTLINE OF RADIO—Covering the Principles of Radio, Television and Radar. 21s. Postage 9d.

QUESTIONS AND ANSWERS ON ELECTRONICS, by E. Molloy. 5s. Postage 4d.

RADIO VALVE DATA—Compiled by Wireless World. 3s. 6d. Postage 3d.

THE RADIO AMATEUR'S HANDBOOK, by A. R. R. L., 1949. 15s. 6d. Postage 1s.

ELECTRONIC TIME MEASUREMENTS, by M. I. T. 42s. Postage 9d.

INTERNATIONAL WORLD RADIO STATION LIST. 1s. 6d. Postage 2d.

RADIO TUBE VADE-MECUM, 1946 edition by P. H. Brans. 5s. Postage 6d.

RADIO ENGINEERING, by F. E. Terman. 42s. Postage 9d.

RADIO LABORATORY HANDBOOK, by M. G. Scroggie. 12s. 6d. Postage 5d.

ELECTRONICS IN THE FACTORY, Edit. Professor Trewman. 20s. Postage 9d.

APPLIED ELECTRONICS, by M. I. T. 39s. Postage 1s.

We have the finest selection of British and American radio books. Complete list on application.

THE MODERN BOOK COMPANY
(Dept. E.7)
19-23, Praed Street, LONDON, W.2

ELECTRON TUBES.
Volumes I and II

RCA Review has just published two additional volumes of its Technical Book Series :

ELECTRON TUBES
Volumes I and II (1935-48)

consisting of 40 full-length papers, 52 papers in summary form and 2 appendices.

All papers are written by RCA engineers and have appeared in leading scientific journals.

Construction, operational and theoretical considerations of Vacuum Tubes are presented in four sections :
General, Transmitting, Receiving and Special.

Price per volume (cloth-bound) 15/-

Write to :
RCA PHOTOPHONE LIMITED,
(An Associate Company of the Radio Corporation of America),
43, BERKELEY SQUARE, LONDON, W.1.

BOOK

Cybernetics

by Norbert Wiener. John Wiley, 1948. Price 18s.

IN many ways this is a book to gladden the heart of an electronic engineer, for it pursues variations on the theme of feedback through all the great range of subjects for which "one has always felt" that a unifying treatment was possible. The somewhat inharmonious title of the new field is derived from the Greek for "helmsman," and will alone doubtless guarantee the work a mixed reception, particularly from those to whom its forms of thought are new and of uncertain value.[1] But the more courageous will find that the elegance of Professor Wiener's mathematical approach compensates both for the title and the highly condensed form in which it is presented. Essentially his thesis is that "the study of sensitive automata, whether in the metal or in the flesh, is a branch of communication engineering," for which the appropriate methods are those of statistical mechanics and group theory.

What gives *direction* to the arrow of time? Wiener answers that in the "Bergsonian" time of statistical mechanics there is a unidirectional flux of *information*. This quantity is defined, apart from sign, in the same way as thermodynamic entropy, and the association of the two is not new. What the author has done, however, is to set forth its fundamental role in widely-differing cybernetic processes.

Chapters III and IV come perhaps nearest to the home ground of the electronic engineer. They include the fruit of some years of war work on filter design and prediction, but make difficult reading for the non-specialist. Particularly important contributions are made to the central practical problem of identifying the "degrees of freedom" of a time series—of reducing it to canonical form. Quantal aspects of information do not, however, receive much explicit notice.[2] Some familiarity with recent papers such as Shannon's on Communication Theory[3] may be found an aid to the digestion of this important section.

In Chapter V, "Computing Machines and the Nervous System," the author outlines the principles on which numerical and logical data can be manipulated by automata. The problems of simulating behaviouristic aspects of logical reasoning, memory, conditioned reflexes and learning, and so on, can be met in principle by the joint application of mathematical logic and feedback to the organisation of machines operating on a binary scale, and including retentive and other devices familiar in the field of electronic computation. It is explicitly and wisely denied that anything more than *possible* models of physiological mechanisms are being described. The argument that a mechanistic account of cerebral activity would prove that thought was "nothing but" a physico-chemical process, would be too naïve when stated in that form to carry conviction; but in various guises it has never lacked its devotees, and it is perhaps relevant to remark that no fundamentally new philosophical issue appears to be raised by the present volume. The construction of an autonomous artefact would, in the opinion of the present reviewer, be of immense value and interest, to philosophers among others; but the result would be to clarify, rather than to resolve, the outstanding issues.

In this connection it also appears to the reviewer that the behaviouristic significance of internal noise (artificially induced or otherwise) would repay further study. In the main logical "mill" of such a device it would merely predispose to vulgar errors. But in controlled amounts at other points its effects would tend to increase the resemblances between human characteristics and those of the machine in much more interesting ways. In conjunction with analogue techniques, a number of concepts such as *probability*, *preference*, *prejudice* and so on could find especially simple analogues.

It would be churlish to accuse a professedly introductory volume of naïveté, but one wonders whether some of the space devoted to a long and chatty introduction could not have been saved for more detail in exposition. As one example of a communication channel, this, of all books, ought in its structure to be statistically matched to its intended public; and one wonders whether in its present form it represents an optimum design. Its task is made harder by the lack of an index, and the presence of numerous misprints in this first edition.

Less than justice has here been done to the scope and significance of Professor Wiener's subject, bearing as it

References

[1] *Book of Acts*, 17: 32.

[2] *Gabor D.*, J. Inst. Elec. Engrs., 93, III, 429-458, 1946.

[3] *Shannon C. E.*, Bell System Tech. Journal, Vol. XXVII, July and Oct., 1948.

REVIEWS

does on almost every branch of knowledge. In many respects the book will invite and perhaps deserve criticism; but it is important that it, and much more on the same subject, should become widely read.

D. M. MacKay

The Theory and Use of Complex Variable

by S. L. Green, M.Sc. Pitman 2nd Edition 1948. 12s. 6d.

THIS small book on the theory of the complex variable has already proved a valuable and readable introduction to the subject. To the engineer it is valuable, since it includes in the text many details of manipulation which can hardly be called mathematical methods, yet are useful time and time again. Moreover, the examples are printed in large type and seem to be chosen with possible applications in mind.

The last two chapters (8 and 9) discuss briefly applications in potential theory and alternating current theory. The electrical engineer may regret that they are not much longer, but in such a short all-round introduction any intensive investigation in one field is not possible. A more serious criticism is that the discussion of the integration of complex variables in Chapter 4 is very short. Far more examples could well be included in view of the importance of this method of dealing with complicated integrals in radio work or elasticity, and in Laplace transforms.

In Chapters 1 and 2 complex numbers are introduced in a consistent way using the Argand diagram, and the important theorem of De Moivre is discussed and applied to integration and series summation. Chapter 3, on series, is entirely concerned with the exponential function and has many useful formulæ. Chapter 4 deals with complex functions and methods of examining them and plotting them, besides integration and Cauchy's theorem. Chapter 5 on conformal transformations is very long for this book, but is especially relevant to applications of complex variables, as it contains a detailed discussion of some important transformations. The Schwartz-Christoffel transform which transforms a polygon into a half-plane, is dealt with separately in Chapter 7.

There is no mention in the preface of any changes from or additions to the first edition.

G. J. Kynch

New Advances on Printed Circuits

United States Department of Commerce. National Bureau of Standards. Miscellaneous Publication 192, 73 pages, 43 illustrations 6 tables. Price 40 cents.

LIKE all publications by the National Bureau of Standards, Washington, this booklet is well set out with clear and relevant illustrations, and full of interesting subject matter. It has often been said that British industry must look to America for a lead as far as production methods are concerned. This booklet certainly deserves close attention from designers, engineers and management in the radio and electronic industry.

The Editor is Dr. Cledo Brunetti whose publication on the same subject in 1947 was widely read in this country and caused unusual interest. This publication shows that American industry has taken full advantage of the information published then and has forged ahead not only in the development of new methods and collection of data but also in turning this technique to a useful purpose in construction and production.

The book contains 22 papers read by representatives of American industry and Government Laboratories at a Convention on the subject in November, 1948. Dr. Brunetti himself starts by surveying the existing methods impartially and giving some useful hints on design to users, as well as a list of available components and details of performance. Methods of depositing printed wiring on high temperature material and in particular ceramics are presented by representatives of the Centralab Division of Globe Union, Du Pont de Nemours and Continental Carbon. Methods on low temperature materials are described by representatives of Metaplast, Altair Machinery Corporation, Spraywire Laboratories, Franklin Airloop and Kenyon Instrument Co. All these companies give their methods in detail with useful figures on performance. Thus it is claimed that silkscreen printed conductors 1 in. long by 0.08 in. wide have a resistance of 0.1 ohm, a surprisingly high figure which can be bettered in this country.

Stress is put on the value of subassemblies and composite components.

Much, however, depends on the availability of high K ceramics in the construction of these. Messrs. Centralab's article ends with an interesting comparison of cost between ordinary wiring and a printed assembly. It is not surprising that this company which has so well understood the value of this

H. K. LEWIS & Co. Ltd.

LENDING LIBRARY

Scientific and Technical
Annual Subscription from
ONE GUINEA

Prospectus post free on request

New Scientific and Technical Books and new editions are always available

Bi-monthly list of new books and new editions sent post free to subscribers on request.

THE LIBRARY CATALOGUE
Revised to December, 1943
containing Classified Index of Authors and Subjects. Demy 8vo pp. viii+928
To Subscribers - - 12s. 6d. net
To Non-subscribers - - 25s. net
(Postage 9d.)
Supplement, 1944 to December, 1946
To Subscribers - - 2s. 6d. net
To Non-subscribers - - 5s. net
(Postage 4d.)

LONDON: H. K. LEWIS & Co. Ltd.
136 GOWER STREET, W.C.1
Telephone : EUSton 4282
Business hours:-9 a.m.-5 p.m. Saturdays-1 p.m.

NEW BOOKS

INDUSTRIAL ELECTRONICS AND CONTROL

By R. G. KLOEFFLER
Head of Department of Electrical Engineering, Kansas State College
9 × 6 478 pages 422 figures 33s. net

MICROWAVES AND RADAR ELECTRONICS

By E. C. POLLARD
Assoc. Professor of Physics,
and J. H. STURTEVANT
Assoc. Professor of Chemistry.
(both of Yale University).
Demy 8vo 426 pages 193 figures 30s. net

CHAPMAN & HALL, LTD.
37-39 Essex Street, London, W.C.2.

BOOK REVIEWS *(continued)*

technique stands supreme in the market.

Messrs. Du Pont's defence of the silk screen method and of subsequent plating, especially on plastics, is one with which few experts in this country will agree. The list of applications and details of economics are, however, worth studying.

The low temperature techniques show only disadvantages over methods developed in this country and most lecturers are very frank about these. Apart from the method given by the Franklin Airloop Co. which includes valuable data particularly on heavy duty wiring, there is little new in this section. Perhaps the most valuable part of the booklet is the descriptions of components either manufactured by these methods or specially suitable for incorporation in printed circuits. These are by representatives of International Resistance Co., who have thoroughly studied the question of laminated resistors, bulk produced, and adjusted by area, and Remington Arms Co., who give full details of the vitreous enamel capacitor about which we have heard so much recently.

Other interesting contributions on the subject are made by Corning Glass Co., *et al.* An outstanding contribution comes from Balco Researcn Laboratories, who give a particularly interesting description of resistors and coils. The latter are printed on quartz or glass ready for insertion. Also discussed are capacitors on plastic film and high K ceramics. An interesting paragraph on assembly technique is a valuable contribution.

The papers most worthy of note to British readers are those given by users of printed circuits describing articles already on the market and those planned. Outstanding is a contribu tion by B. V. Blom, of the Signal Corps, describing how printed circuits help in design of constructions used for military purposes, particularly as regards miniaturisation; unitised construction; increased frequency coverage; number of pre-set channels and reliability; lower operating voltage: operation at higher frequencies, and over extreme climatic conditions. Lastly, it promises increased mass production capabilities. Representatives of various companies describe their printed products which may be summarised in the words of Al Gross, of the Citizens Radio Co. "Printed circuit techniques are here to stay, for they are a boon to the radio and electronic industry." A paper on fundamentals by L. Marton, of the N.B.S., is further worthy of mention.

The booklet ends with a summary on a questionnaire filled in by 527 representatives of American industry which represents a testimony of faith in the method and a vote of confidence in the future of printed circuit technique in general. Of special interest is a list of equipment to which the technique can be applied giving the percentage of those present who are interested in the particular application. It is remarkable that Home Receiving Equipment (AM and FM) top the poll with 35 per cent. Aircraft equipment and television receivers are next. Altogether 20 subjects are listed.

It is regretted that this book, unlike its predecessor, contains no bibliography, and it is even more to be regretted that like its predecessor it will not be readily available to all engineers in this country who might profit by its study.

P. P. HOPF.

Theorie et Applications des Tubes Electroniques

D. G. Fink, Dunod. Paris, 1948.

THIS is a French translation of Mr. D. G. Fink's well-known book in the McGraw-Hill series, and the anonymous translator has done his work well. The problems at the end of each chapter have been included, and an appendix gives definitions of the A.I.E.E. electronic terms. The best summary of the book is given in the phrase on the cover band, which is far more expressive in the original French: "Sans mathématiques supérieures ni vulgarisation élémentaire."

G. PARR

Proceedings of B.T.H. Summer School in Electronic Engineering

Published privately by the B.T.H. Co. Ltd., Rugby.

IN the summer of 1948 the British Thomson-Houston Company held a unique meeting for professors of electrical engineering at their Rugby works, at which the company's staff gave lectures and demonstrations of some of the latest developments in electrical and allied science. These lectures have been issued in book form for private circulation, and should prove of great value to all engaged in teaching the advanced aspects of the subject. A limited number of copies are obtainable by executive engineers and senior officials on application to the Publicity Department at Rugby.

Basic Technical Electricity Cleaver-Hume Electrical Series

No. 1 by H. Cotton, M.B.E., D.Sc., M.I.E.E. Cleaver-Hume Press, Ltd., 238 pages, 74 figs Price 8s. 6d. net.

PROFESSOR COTTON has a wide reputation as an author of electrical engineering textbooks. He is the general editor of a new series of nine volumes, the Cleaver-Hume Electrical Series, but it is not clear whether or not he is to write them himself. His avowed intention is to provide electrical knowledge for daily work or pastime, and in the preface he claims that this volume contains the minimum of theory as well as such fundamentals as will be required in reading the later volumes. While he mentions electronics in the preface, he does not introduce the subject in this volume. We must therefore assume that the later volumes will not be concerned with applications of thermionics.

Writers of books on technical electricity have in the past evaded the purely scientific issue, and adopted the attitude that if the reader does not already know the fundamental physics of the subject it is no part of that particular writer to remedy the omission. The fields of theoretical physics and applied electrical science overlap to such an extent that the overlap cannot be ignored and employing the electronic theory from the beginning, as this book does, is most helpful.

The presentation is that normally used, the production of an electric current, followed by the effects of current, that difficult subject "Work Power and Energy", then magnetism and electromagnetism and lastly units and measurements. The reviewer would have been pleased if Professor Cotton had adopted the optimistic conception of a conductor and used conductance and mhos straightaway on p. 26, where we are introduced to resistance but perhaps it was venturesome enough to mention it on p. 34 for future employment.

The numerical examples in the text are a great help in understanding quantities, especially electrical units, and the test questions at the end are valuable to the reader who wishes to check his grasp of the subject.

The plates of large power plant are somewhat premature and though they are interesting to the beginner their place is more properly the later volumes.

H. CLARKE

Made in America

Being a selection of American electronic equipment and products, with notes compiled from the manufacturers' data.

New 5-KW FM Transmitter

A NEW R.C.A. 5-KW FM transmitter designed for broadcasters who require up to 60 KW effective radiated power has been announced by the R.C.A. Engineering Products Department. High efficiency and low tube and operating costs are claimed for the new Model BTF-5A transmitter. It is particularly adapted for use with a four-section Pylon antenna with a gain of six to obtain 20 KW radiated power.

This transmitter, combining the "Direct FM" circuits common to previous R.C.A. transmitters with the power saving grounded grid circuit, is capable of furnishing power output of from 1,000 to 5,000 watts to the transmission line, and when used with the R.C.A. high-gain Pylon antenna, can provide radiated power up to 60 kilowatts.

Structurally, the 5 KW FM transmitter consists of three standard transmitter cabinets. The exciter (and a spare, if used) and its power supply are located in the centre cabinet. The R.F. amplifier circuits are housed in the left-hand cabinet, and the high-voltage power supply and control circuits in the right-hand cabinet. Cabinet styling and appearance are the same as that of all unit enclosures of other R.C.A. FM transmitters of both lower and higher power.

A variety of R.C.A. Pylon antennas may be used with the new transmitter including the standard and heavy duty types. By adding from one to eight sections, radiated power of from 7.5 kilowatts to 60 kilowatts is possible.

RCA 5794 Triode *(Photo on left)*

THE 5794 is a fixed-tuned U.H.F. oscillator triode with two integral resonators for use in radiosonde transmitters operating at 1,680 megacycles. One of the resonators is fixed-tuned and is attached between grid and cathode; the other is tunable over a narrow range about 1,680 megacycles and is attached between grid and plate. The latter resonator is loop-coupled to a coaxial R.F.-output terminal. The 5794 has a useful power output in the order of 500 milliwatts.

Features contributing to the usefulness of this valve in radiosonde service include its compact metal construction, low battery drain and small frequency drift.

R.C.A. Photophone, Ltd., 43 Berkeley Square, London, W.1.

Rahm Medical Equipment

THE following electro-medical equipment is described in brochures issued by Rahm Instruments Inc.

All-mains electro-encephalograph gives smudge-proof, inkless recording "Duratape." The amplified uses miniature valves to give a maximum gain of ten million (1 mm. deflexion per microvolt).

A fixed- and a variable-frequency stimulator. For neurosurgical use in determining Motor-Cortex areas and locating sensory pathways.

Two electro-shock monitors; a comprehensive model with variable shock voltage and duration (from 0.1 to 1 second), and a smaller and lighter type with only the essential features of the more expensive model incorporated. Both monitors, however, are fully safeguarded.

Rahm Instruments Inc., 12 West Broadway, New York 7.

THE Fourth National Instrument Exhibition is to be held in the St. Louis Municipal Auditorium from September 12 to 16, 1949. It is anticipated that upwards of 10,000 people will inspect the exhibits, which will include scientific and industrial instruments and devices for measurement, inspection, testing and control.

Technical sessions of the Instrument Society of America, American Institute of Physics, Industrial Instruments and Regulators Division of the American Society of Mechanical Engineers, and the Instruments and Measurements Committee of the American Institute of Electrical Engineers, the Institute of Radio Engineers, the American the National Telemetering Forum, will be held in the Auditorium while the exhibition is in progress.

United Kingdom firms wishing to participate should apply to the Executive Secretary of the Instrument Society of America, 1117 Wolfendale Street, Pittsburgh, 12, Pa.

Inquiries about this exhibition should be addressed to the Department's Exhibitions and Fairs Division, Horseferry House, Thorney Street, London, S.W.1. (Telephone: Victoria 6800 Ext. 253).

Data Recorder *(See below)*

A NEW addition to the standard line of data recorder mechanisms produced by Cook Laboratories has been announced. This unit is designated Type MR-4 and is designed for use with suitable coupling equipment and sensing instruments as a complete recording system. It is fully capable of withstanding high shock accelerations up to 75 G.

The Type MR-4 recording mechanism is a miniature 13-channel unit weighing 24 ounces. It includes one reference frequency oscillator plus 12 information channels and has a recording time of 2½ minutes. Its small size of 8 × 3⅜ × 2¼ in. and light weight make it suitable for applications requiring the measurement of such factors as accelerations, stresses, temperatures, pressures, vibrations, etc., in airborne equipment, flight testing and guided missile work.

This new unit, like other Cook recorders, uses magnetic tape to store variable or transient data under conditions of severe shock acceleration for later analysis.

Cook Research Laboratories, 1457 Diversey Parkway, Chicago 14, Illinois.

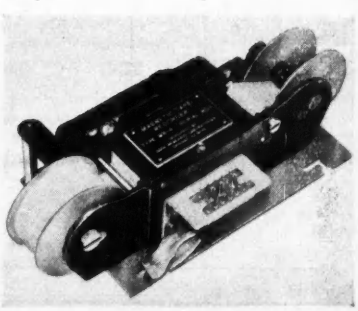

CORRESPONDENCE

R–C Oscillators

DEAR SIR,—In Mr. F. Butler's article "Variable Frequency *R-C* Oscillators,"[1] there are inaccuracies in the table giving attenuation ratio and operating frequency for various stages of the *R-C* uniform ladder, which is used as the feedback network. From a cursory inspection of the literature on the subject, it appears that no one has yet published a carefully checked list of attenuation and frequency coefficients for the *R-C* and *C-R* uniform ladder networks of n steps (Fig. 1). In fact, there seems to have been errors in several of the early articles. As examples, (*a*) Ginzton and Hollingsworth[2] give a wrong expression for the attenuation of a non-uniform 4-step *C-R* ladder, and a wrong attenuation coefficient for a 3-step uniform *R-C* ladder; (*b*) Whitehead,[3] for a 3-step uniform *R-C* ladder gives a quite erroneous table of attenuation and frequency coefficients, (these having been deduced by neglecting the shunting effects of subsequent steps on any one section, thus he gives an attenuation factor of 8, which should be 29): and finally (*c*) Bacon,[4] who makes the same simplification as Whitehead.

Table 1 herewith has therefore been produced to meet this need; the number of steps is probably beyond the range of practical interest, although it may serve to show the surprising result that less amplification is required, the larger the number of steps used.

Comparing this Table 1 with the table given by Butler, it will be seen that for the *R-C* uniform ladder, the two attenuation coefficients he gives for 5- and 6-steps, namely 16.15 and 13.72, should be 15.43 and 14.12 respectively. A more serious error occurs in the frequency coefficients which he gives; they are all about twice the correct values. Consequently the range of 250-5,000 c/s., which he states for the 4-step *R-C* oscillator of his Fig. 3, should I think, be 125-2,500 c/s.

Regarding the more detailed 25-17,000 c/s. *R-C* oscillator given in his Fig. 4 and the table referring to the frequency range on each of its six positions, from the description and figure it is difficult to decide if the feedback *R-C* ladder has 3, 4 or 5 steps. Assuming the oscillator to have a 4-step *R-C* ladder, the variable capacitor to change between the values 100-500 pF, and neglecting the phase shift occasioned by the 0.1 μF coupling capacitor and the 1-MΩ shunt, then Table 2 herewith gives the theoretical frequency ranges which would be obtained. It can be seen that these are, very roughly, about twice those given by Butler. This difference could not be occasioned by the coupling, the effect of which would be negligible at the top of the range, and at the bottom would cause the frequencies stated to be about 25 per cent too low. It would be very informative to know if the figures given by Mr. Butler are experimental or theoretical, and if experimental, how he would account for such large differences.

References

[1] F. Butler, "Variable Frequency *R-C* Oscillators," *Electronic Engineering*, Vol. 21, No. 254, pp. 140-142, April, 1949.

[2] E. L. Ginzton and L. M. Hollingsworth, "Phase Shift Oscillators," *Proc. I.R.E.*, Vol. 29, pp. 43-49, February, 1941.

[3] R. C. Whitehead "Resistance-Capacity Oscillator," *Wireless World*, Vol. 48, pp. 278-281, December, 1942.

[4] W. Bacon, "A simple *R-C* Oscillator," *Electronic Engineering*, Vol. 14, p. 707, April, 1942.

Table 1

Attenuation and Frequency Coefficients for *R-C* and *C-R* Uniform-Ladder Networks of n Steps

Steps n	Attenuation Coefficient α for both *R-C* and *C-R* ladders	Frequency Coefficient β *R-C*	Frequency Coefficient β *C-R*
3	—29	0.390	0.0650
4	—18.39	0.1905	0.1332
5	—15.43	0.1178	0.2155
6	—14.12	0.0812	0.3135
7	—13.43	0.0593	0.427
8	—12.97	0.0457	0.556
9	—12.66	0.0363	0.702
10	—12.58	0.0296	0.858
∞	—11.57	0	∞

Table 2

Range	Frequency c/s
1	34.5— 54.5
2	47.7— 95.5
3	76.2— 381
4	381 — 1905
5	1905 — 9520
6	7620 —38100

JOHN E. PARTON,
Electrical Engineering Dept.,
Glasgow University.

DEAR SIR,—The contribution about "Variable Frequency *R-C* Oscillators" by F. Butler in the April issue, 1949, of ELECTRONIC ENGINEERING contains on page 140 a table giving the attenuation of an operating frequency by different *R-C* ladder networks according to Fig. 2. The operating frequencies given in the table, do not agree with my calculations nor with the data published by Ginston and Hollingsworth in the February issue, 1941, of the *Proc. I.R.E.* The data for f, given by Butler, are about twice too high. Accordingly the frequency ranges given for the oscillators shown in Fig. 3 and Fig. 4 do not seem to be correct.

In order to give Mr. Butler opportunity to check my calculations and eventually to point out the fault in my calculation, I give you an extract of the way I tackled the problem.

In the figure below, I pictured a general ladder-network of series-impedances Z_1 and shunt-impedances Z_2. Applying Kirchoff's laws we can write down the following equations:

$$i_1(Z_1 + Z_2) - i_2Z_2 = E_1$$
$$-i_1Z_2 + i_2(Z_1 + 2Z_2) - i_3Z_2 = 0$$
$$-i_2Z_2 + i_3(Z_1 + 2Z_2) - i_4Z_2 = 0$$
$$\cdots\cdots\cdots\cdots\cdots\cdots\cdots$$
$$-i_{n-2}Z_2 + i_{n-1}(Z_1 + 2Z_2) - i_nZ_2 = 0$$
$$-i_{n-1}Z_2 + i_n(Z_1 + 2Z_2) = 0$$
$$i_n = E_0/Z_2.$$

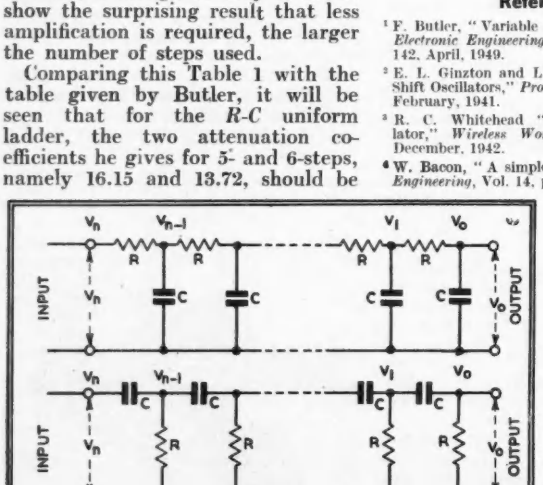

R-C and C-R uniform ladder networks
(See letter, above, from J. Parton)

From these equations we can find the relation E_i/E_o by eliminating $i_1, i_2 \ldots i_{n-1}, i_n$. This I have done in the following way. Putting $Z_1/Z_2 = a$ we can rewrite the equations as follows:

$$\begin{aligned} i_1(1+a) - i_2 &= E_i/Z_2 \\ -i_1 + i_2(2+a) - i_3 &= 0 \\ -i_2 + i_3(2+a) - i_4 &= 0 \\ \hline -i_{n-2} + i_{n-1}(2+a) - i_n &= 0 \\ -i_{n-1} + i_n(2+a) &= 0 \end{aligned}$$

$$i_n = \frac{E_o}{Z_2}$$

From these we find:

$$i_n = \frac{E_o}{Z_2}, \quad i_{n-1} = i_n(2+a),$$

$$i_{n-2} = i_n(2+a)^2 - i_n$$

$$i_{n-3} = i_n(2+a)^3 - 2i_n(2+a),$$

$$i_{n-4} = i_n(2+a)^4 - 3i_n(2+a)^2 + i_n$$

$$i_{n-5} = i_n(2+a)^5 - 4i_n(2+a)^3 + 3i_n(2+a), \text{ etc., etc.}$$

For $n = 3$ we find therefore:

$$i_3 = \frac{E_o}{Z_2}; \; i_2 = (2+a)\frac{E_o}{Z_2};$$

$$i_1 = (2+a)^2\frac{E_o}{Z_2} - \frac{E_o}{Z_2}$$

and finally:

$$\frac{E_o}{Z_2}\left\{(1+a)(2+a)^2 - (1+a) - (2+a)\right\} = \frac{E_i}{Z_2}$$

giving:

$$\frac{E_i}{E_o} = (1+a)(2+a)^2 - (3+2a)$$

In the case under consideration

$$Z_1 = R; \; Z_2 = \frac{1}{j\omega C}; \quad \frac{Z_1}{Z_2} = j\omega RC = ja$$

yielding:

$$\frac{E_i}{E_o} = 1 - 5a^2 + j(6a - a^3)$$

For a phase difference of 180° between E_o and E_i, the imaginary part must equal zero. This gives $6 - a^2 = 0$; $a^2 = 6$. The real part of the expression for E_i/E_o then works out to $E_i/E_o = 1 - 30 = -29$, showing that the phase difference is really 180° and the attenuation ratio is 29. The operating frequency works out to

$$f = \frac{a}{2\pi RC} = \frac{\sqrt{6}}{2\pi RC} = \frac{0.391}{CR}$$

For $n = 4$ and working along the same lines, I find:

$$\frac{E_i}{E_o} = 1 + 10a + 15a^2 + 7a^3 + a^4,$$

giving

$$\frac{E_i}{E_o} = 1 - 15a^2 + a^4 + j(10a - 7a^3)$$

This yields for 180° phase difference between E_i and E_o: $a^2 = 10/7$,

$$\frac{E_i}{E_o} = -18.4, \; f = \frac{a}{2\pi RC} = \frac{\sqrt{(10/7)}}{2\pi RC} = \frac{0.191}{CR}$$

$n = 5$ gives:

$$\frac{E_i}{E_o} = -15.83; \; f = \frac{0.118}{CR}$$

and $n = 6$ gives:

$$\frac{E_i}{E_o} = -14.09; \; f = \frac{0.081}{CR}$$

If my calculations are correct, it seems to me in the interest of the readers of ELECTRONIC ENGINEERING to have the data published by Mr. Butler corrected. If there might be a hidden fault in my reasoning, I should be glad to be corrected by Mr. Butler.

J. ROORDA.

Hofwyckstraat 57, Voorburg, Holland.

Sealed Transformers

DEAR SIR,—In reference to the article "Hermetically Sealed Transformers" in the June issue we submit the following elementary comments on the principles of manufacture.

The testing o fcontainers for leaks

Under-water tests with some 20/30 lb. of internal pressure is of little value, however frequently repeated, for revealing the extremely small holes through which oil may escape. The surface tension of water is too great for this purpose and sets a limit on the size of the hole it is possible to detect. Still more important, a hole will most certainly be obstructed by the resin flux used when soldering. There is also the dangerous possibility that the cold water may be at a lower temperature than the transformer as it arrives from the preceding hot soldering process and water may be sucked through by air contraction before the pressure is applied. Again the very presence of water at any stage during manufacture is in complete disregard to the condition so strictly enforced in transformer or capacitor production of absolute dryness of surroundings.

The pressure process of testing containers for leaks is normally made under oil of low surface tension raised to a sufficient temperature to soften adequately any obstructing resin deposit. Ultra-violet light tests are often defeated by the presence of trichlorethylene used for degreasing.

Steel or tin plate containers v. copper or brass

Both iron and tin plate offer rustable edges. All iron pieces need to be resin dipped soon after shaping and in consequence become inconvenient to handle and difficult to fit tightly together. The meagre degree of magnetic screening that thin iron may provide is a doubtful merit. Iron is less costly than copper, but the latter metal is always clean and unrustable and will not corrode under paint when in use. The consideration that iron is less heavy is insignificant, a typical transformer consisting of a $1\frac{1}{2}$ in. stack of No. 4 stampings being only $\frac{3}{4}$ per cent heavier with copper container..

Terminal sealing by R.F. heating

This often suggested process is not favoured. The small metallised ring around many a bush may suffer immediate destruction, resting as it does on an insulating surface of resin flux and the metal terminal heads all become overheated. Nothing is easier, if electrical heating is intended, than the passing of a current, regulated by foot switch control, across the terminal carrying section of the box, from copper or carbon faced clamps, particularly as the current density increases around the holes. Ceramic bushes so fixed can be smashed off on the face of an anvil, but the silver to copper seal, carrying a coating of sharp ceramic particles, will always remain.

Metal flanged glass bushes

These are far more easily damaged by heat, transit and use than those of hard ceramic. The

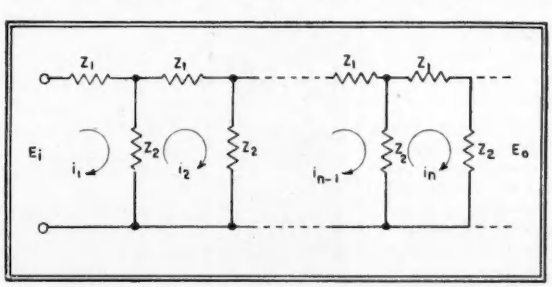

Series- and shunt-impedance network
(See letter from J. Roorda)

CORRESPONDENCE (*continued*)

centre conductor is usually sharp ended and inadequate, while the seals themselves take up too much space.

Filling Materials

Reference is made to the difficulty of injecting petroleum jelly or other media into the container. The commonly used methods of vacuum impregnation by which all canned devices are filled presents no problem. In any event the filling fluid is best kept adequately heated and under vacuum to ensure dryness, and any air subsequently admitted must be drawn through a drying source. The adoption of such special insulating fillings as have been recently introduced in respect of small high voltage capacitors offers enormous advantages.

The first transformers built to this general principle of total sealing in lapped seam copper containers and fitted with soldered-in insulating terminal bushings were developed by ourselves. The system was later taken up by a number of contemporary producers to meet the war demands of the services. We have made no substantial change from the original productions using horizontal core stack so as to afford flexibility of can size with the fixing centres standardised on lamination corner holes, features that are appreciated by your contributor.

Small canned transformers are undoubtedly useful in certain applications, but respect may be paid in design to the lack of ventilation. Specific heat and the latent heat of melting of the filling give some measure of cooling in intermittent use. The canned unit is no more costly to produce than the overall dipped open type, where the general construction can be seen and judged. The open type is to be preferred for many purposes and insulation weaknesses so often criticised usually arise from inferior terminal plate design.

HUGH F. HAYNES
Haynes Radio, Ltd.

Mr. Jones replies:

I appreciate that there are several methods of manufacturing hermetically sealed transformers, and the method each individual manufacturer chooses is no doubt to some extent dictated by the equipment available. The points raised by Mr. Haynes seem to suggest only a different method of arriving at a similar result. I wish to emphasise that the ultimate test of sealing is the final heat run of four hours at +110° C. mentioned in my article, the immersion of the container in a fluid after inflation being only a preliminary eliminating test.

I make no claims that mounting the laminations horizontally is unique, as this construction seems only logical if some measure of standardisation is to be achieved within the industry. I cannot agree, however, that with the present materials available the hermetically sealed transformer need be more costly than its open counterpart. The total cost of material per transformer is considerably greater, and more time is involved in the prolonged additional tests necessary to check the efficacy of the sealing, as unless this is complete the transformer may well be inferior to the open type.

Combined Current and Voltage Feedback

DEAR SIR,—The amplifier described in Dr. Sturley's article in your May issue is a simple case of a multiple-path feedback amplifier. It is true that the local feedback occurring in the input stage of an amplifier can usually be neglected, but considerable use can be made of such feedback mainly to improve the stability margin of the amplifier. An example where the local feedback has been deliberately employed can be found in an article "A Miniature Audio-frequency Amplifier" in the *Post Office Electrical Engineer's Journal* 41 p. 228, January '49.

The use of multiple-feedback paths in amplifiers is described in a paper entitled "Some Consideration in the Design of Negative Feedback Amplifiers," early copies of which are available from the Institution of Electrical Engineers.

W. T. DUERDOTH,
B.Sc., A.M.I.E.E.

Microwave Radio Link for Television Outside Broadcasts

B.B.C. engineers are investigating the possibilities of microwave radio links for transmitting television pictures from outside broadcast points to Alexandra Palace.

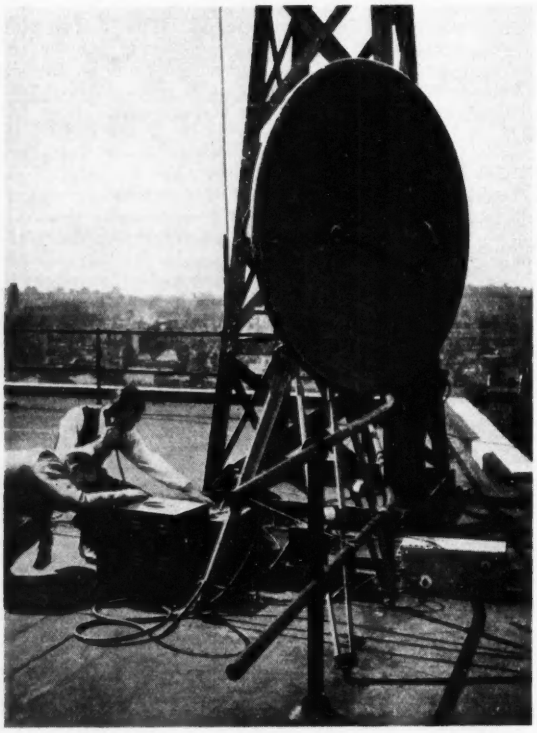

The transmitting equipment being used in these tests consists of a klystron oscillator operating on a wavelength of 4.5 cm., which is frequency modulated by the vision signals, and a 4-ft. diameter paraboloid reflector with waveguide feed. The transmitter power is about 100 mW and the aerial gain is 5,000. A similar aerial system is used at the receiving end. The transmitter and the receiver are built into the back of the paraboloid reflectors, and the rest is constructed in "suitcase" form.

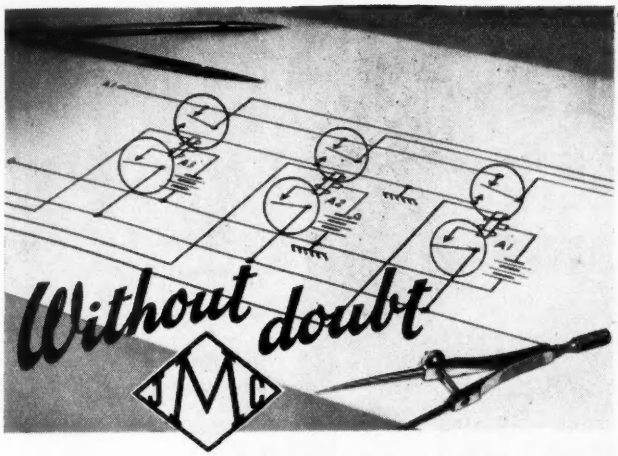

You will be in no doubt of the basic excellence of your design. It is the result of many hours of detailed planning and experimental work, and you will have left nothing to chance. The operation of the equipment when it leaves your hands will be faultless. But—will it continue to be so?

Shortening of useful life due to mechanical or electrical wear of contacts, fluctuations in circuit characteristics through surface tarnishing—these are ever-present possibilities when the contacts you have fitted are not suited to their work.

RELAY CONTACTS & SPRINGS

Specialised products of

Johnson Matthey
MALLORY

If you have experienced such problems, or others more subtle, remember that we maintain at your command a range of contact materials we know to be without equal and an advisory service always ready to assist you impartially in obtaining the maximum working life from your equipment

JOHNSON, MATTHEY & CO., LIMITED, HATTON GARDEN, LONDON, E.C.1
Controlling Mallory Metallurgical Products Ltd.

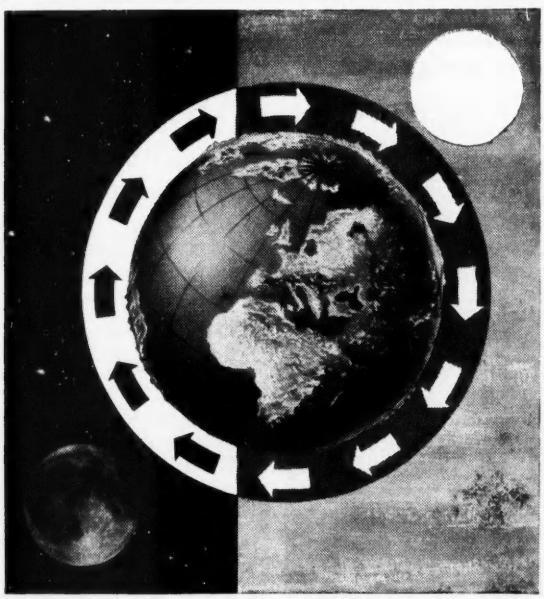

Continuously in Service, Day and Night

Noon over Nanking. Dawn over the Atlantic. Blackness over the Andes. In all parts of the world, at all times of the day and night, Marconi built stations are in operation, broadcasting or sending telegraph messages and giving unrivalled service. Wherever ships and aircraft are plying, you will find Marconi apparatus guiding them, every hour of the day, every day of the week. Pioneers in Wireless Communication fifty years ago, Marconi's still maintain their leadership. Behind every new development there will be Marconi's accumulated experience. Behind every new piece of Marconi equipment there will be the honoured name as an assurance of maximum efficiency.

Marconi THE GREATEST NAME IN WIRELESS

MARCONI'S WIRELESS TELEGRAPH COMPANY LTD., MARCONI HOUSE, CHELMSFORD, ESSEX

ONE OF THE BALDWIN INSTRUMENTS

ELECTROMETER — VOLTMETER

A sensitive
ELECTROMETER

The input resistance is 10^{16} ohms and the capacitance less than 1 pF

MEASURES
Electrostatic potentials
Very small currents
Very high resistances

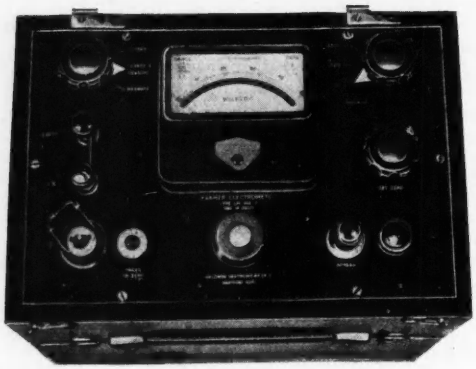

A first-grade D.C.
VOLTMETER

Ranges:
0 — 50 — 100 — 500 V

WIDE APPLICATIONS
in electronic engineering, including ionization measurements

USES AN ELECTROMETER-VALVE
in the Farmer Cathode-follower circuit.

BALDWIN INSTRUMENT CO. LTD., DARTFORD, KENT
Telephone : DARTFORD 2989

MINIRACK

COMPLETE CATHODE - RAY OSCILLOGRAPH EQUIPMENTS

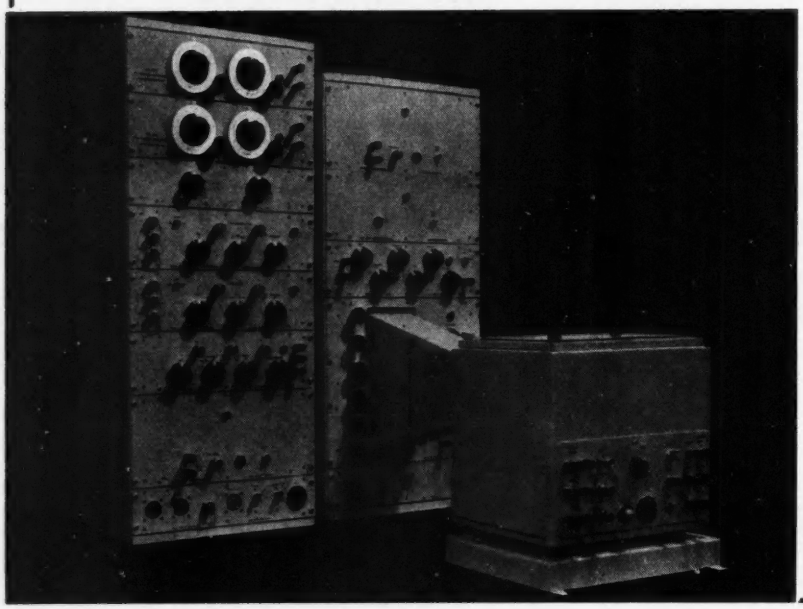

- Single and Multi-channel
- F.M. Amplifiers
- A.C. and D.C. Amplifiers
- Time-Bases
- Time-Markers
- Recording Cameras
- Pressure and Vibration pick-ups

We make a wide range of standard equipments to suit all purposes.
PLEASE WRITE FOR DETAILS

Special equipments made to meet users' requirements

SOUTHERN INSTRUMENTS
LIMITED
FERNHILL, HAWLEY
CAMBERLEY, SURREY
Phone: Camberley 1741

"COLVERN" HIGH ACCURACY PRECISION POTENTIOMETERS

For Electronic Computing, Radar, Communications and Laboratory apparatus.—Incorporating the unique COLVERN CAM-CORRECTION DEVICE—the finest and most accurate potentiometers in the world.

A guaranteed law accuracy of better than ± 0.1% is maintained in all standard COLVERN CAM-CORRECTED POTENTIOMETERS, whilst in the type CLR. 9101 illustrated the law tolerance can be held as low as 0.04% and even lower dependent on resistance value.

There is a "COLVERN" Potentiometer to suit every circuit an Electronic Engineer is likely to devise.—Write for illustrated brochures to :—

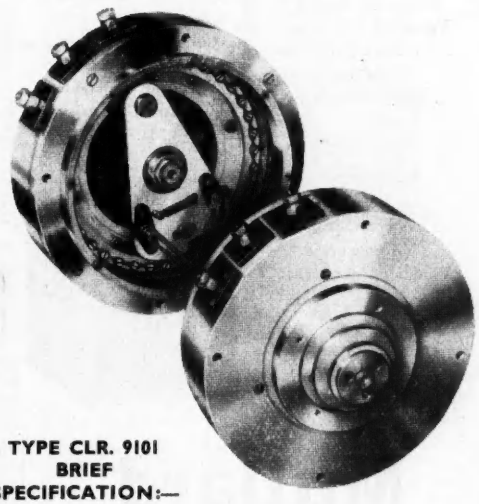

TYPE CLR. 9101
BRIEF SPECIFICATION:—

Rating	... ...	10 watts
Resistance values	... ...	1000Ω to 150,000 Ω
Law accuracy	... ...	± 0.04%
Working voltage (between spindle and track)	... ...	1000 V D.C.
Effective angle of resistance	...	315° plus 0.25°—0°
Angle of spindle rotation	...	360°

COLVERN LIMITED

MAWNEYS ROAD
ROMFORD · ESSEX
Telephone : ROMFORD 2020, 4880, 4881

INDUSTRY

is catching up with

SCIENCE

INEVITABLY, Science is always a step ahead of industry, but it is Mullard's endeavour to close this gap. Mullard are in the unique position of being both electronic experts and industrial consultants — they are, in fact, industrial scientists. Thus, they are able to utilise scientific discoveries in the design of better equipment for practically every sphere of industrial activity.

MULLARD EQUIPMENT FOR RESEARCH AND INDUSTRY INCLUDES THE FOLLOWING :—

Instruments for the Electrical Laboratory

Cathode Ray Oscillographs
Beat Frequency Oscillators
Measuring Bridges
Valve Volt Ohmeters
V.H.F. Valve Voltmeters
High Voltage Power Supply
F.M. Signal Generators

Electrochemical Equipment

Potentiometric Titration Apparatus
Karl Fischer Equipment
Electronic Polarimeters
Conductivity Bridges
Conductivity Controllers
Ultrasonic Generators
Ultrasonic Consistency Meters

Industrial Equipment

Valve Relay Units
Frequency Meters
Viscometers
Vibration Equipment

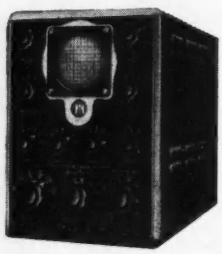

MULLARD OSCILLOGRAPH
Type E.800/1
Information and advice on this and any other equipment may be obtained from

Mullard

ELECTRONIC PRODUCTS LTD.,

Electronic Equipment Division

ABOYNE WORKS, ABOYNE ROAD, LONDON, S.W.17

(MI.2781)

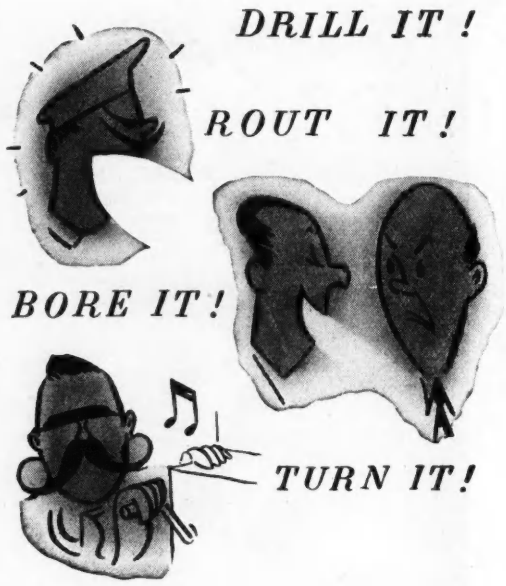

Delaron might have been made for machinists —it's such a tractable material. Mechanically it is strong, tough and remarkably durable. It can replace rawhide in gears and, on the other hand can be formed into quite small clock pinions provided a suitable grade is chosen. It also readily lends itself to fabrication saving patterns and foundry work. On the electrical side it has very desirable di-electric characteristics—for terminal strips, coil formers, bobbins, panels and even instrument cases. Made by treating paper and Fabric to processes of immersion in synthetic resin and plasticising the built up sheets under heat and pressure. Paper grades from 0.2 mm. thickness. Fabric grades from 0.28 mm. *Please write for full details.*

DELARON

laminated plastic

THOMAS DE LA RUE & CO. LTD.—PLASTICS DIVISION
Imperial House, 84/86 Regent Street, W.1. Tel.: REGent 2901

IND/I/49

Of Interest

TO ALL ELECTRICAL AND WIRELESS ENGINEERS

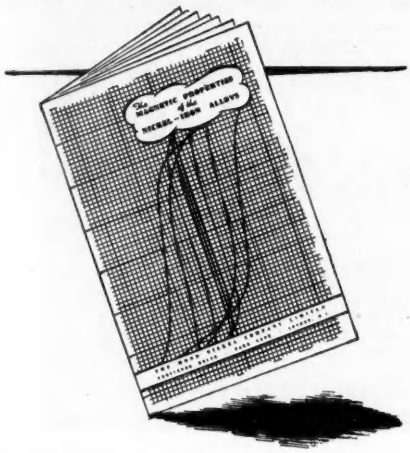

THIS BOOK dealing with the magnetic properties of the nickel-iron alloys will be sent free on request. It contains information on:

1. NON-MAGNETIC AND WEAKLY-MAGNETIC ALLOYS
Non-magnetic ferrous engineering materials—Temperature compensation alloys.

2. HIGH PERMEABILITY NICKEL-IRON ALLOYS
General and historical—Early uses: cable loading—Further development: transformers, screens, dust-cores, etc., radar, specialized alloys.

3. MAGNETOSTRICTION
General—Echo sounding—Frequency control.

4. PERMANENT MAGNETS
Development: Alni, Alnico, Alcomax—Properties—Sintered magnets—Applications—Ductile alloys.

Application should be made to:

THE MOND NICKEL COMPANY LIMITED

Sunderland House, Curzon Street, London, W.1 12/QA/3

Precision with a Pedigree

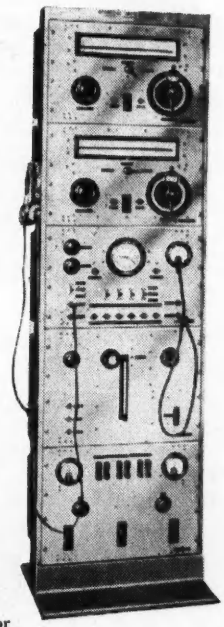

FREQUENCY MEASURING EQUIPMENT

Type TME 1

Years ago, the frequency measuring equipments made by Marconi's were for their own use — because nowhere else could sufficiently accurate instruments be obtained. The present equipment therefore, Type TME 1, boasts a long and distinguished pedigree and, like its predecessors, is precision-built to an exacting specification. Anywhere in the world it can be rapidly installed and its rated stability of 1 part in 10^6 maintained indefinitely. In price too, it commends itself as the ideal laboratory standard. Please ask for further details. Type TME 1 Frequency Measuring Equipment is available for early delivery.

Marconi Instruments Ltd

ST. ALBANS, HERTS. Telephone: St. Albans 6161/5

Northern Office: 30 Albion Street, Hull. Western Office: 10 Portview Road, Avonmouth. Southern Office & Showrooms: 109 Eaton Square, London, S.W.1. Midland Office: 19 The Parade, Leamington Spa.

FROM BBC STUDIOS TO
HOME REPRODUCERS
it's
The same skill and quality that is demanded for B.B.C. FADERS goes into the construction of all Painton products.
Wherever trouble-free, noiseless variation of level is required, either by fading or attenuation to pre-determined settings, you can, with confidence, rely upon
control by PAINTON
PHOTOGRAPHS BY KIND PERMISSION OF THE B.B.C.
PAINTON & CO LTD · KINGSTHORPE · NORTHAMPTON

THE OSCILLOSCOPE FOR EVERY INDUSTRIAL PURPOSE.

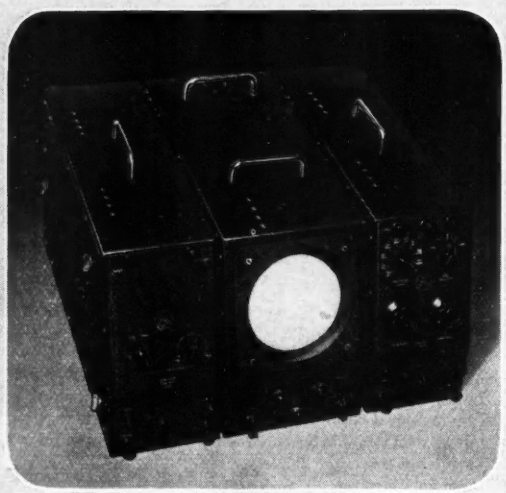

LAL UNIT *Oscilloscope*

10 Mc/S. · 20 Secs: · 4 μ Secs: · D.C.

EVERY Oscilloscope requirement for Industrial Research or Production can be satisfied by the comprehensive range of UNIT Amplifiers and Time Bases. All instruments are immediately interchangeable without loose wires or the use of tools and many can be used independently of the Oscilloscope. Full details will be sent by return of post.

Also available: —
D.C. Amplifiers, medium and high gain. Extra low frequency time base. Circular or spiral heptode time base. Voltage calibrator.

LAL *Lydiate Ash* LABORATORIES
LYDIATE ASH · NEAR BROMSGROVE · WORCS.

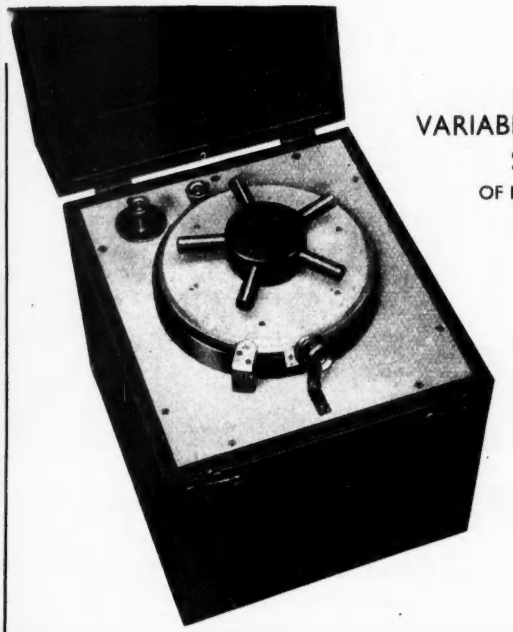

Electrical Standards for Research and Industry

Testing and Measuring Apparatus FOR COMMUNICATION ENGINEERING

VARIABLE AIR CONDENSER STANDARDS

OF HIGH PERFORMANCE

TEMPERATURE COEFFICIENT : 5×10^{-6} per deg. C.
LINEARITY OF LAW : Sufficiently good to ensure a **SCALE SETTING** of 1 part in 30,000.
POWER FACTOR : (10^3 to 10^5 c/s)
$<0{\cdot}00001$ at all settings.
(not seriously impaired at 5 Mc/s)
RESIDUAL INDUCTANCE : $0{\cdot}03\mu$H.

The standard illustrated is fitted with a direct reading scale in addition to the finely divided degree scale and magnifier. The dividing of the latter is much too fine for reproduction in the illustration.

H. W. SULLIVAN LIMITED

LONDON, S.E.15

Telephone : New Cross 3225 (P.B.X.)

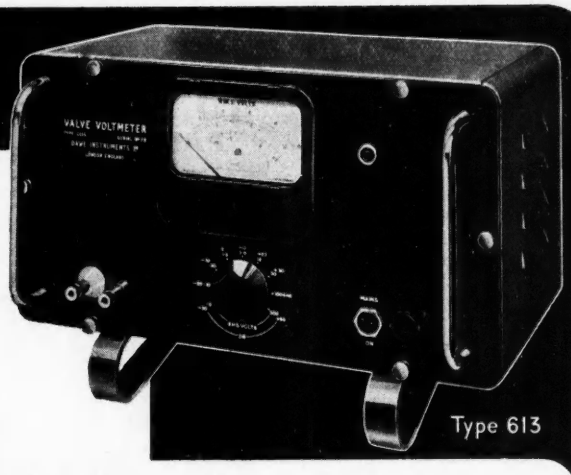

DAWE

VALVE VOLTMETER

Type 613

Sets a new standard of performance for voltage measurements in the audio, supersonic and radio frequency ranges

- WIDE RANGE — 1 mV. to 300 V.
- WIDE FREQUENCY COVERAGE 10 c/s to 1.5 Mc/s.
- DIRECT READING dB SCALE.
- NO ZERO SETTING.

DAWE INSTRUMENTS LTD

130 UXBRIDGE ROAD, HANWELL, LONDON, W.7. EALING 6215

AN ANNOUNCEMENT OF EXCEPTIONAL INTEREST . . . .

The FOX HELICAL POTENTIOMETER type PXF 5/H 10 is now available for general release to the Electronic Industry

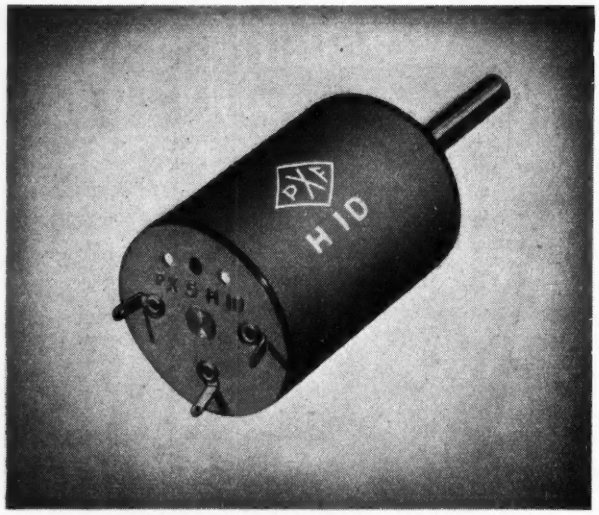

BRIEF SPECIFICATION

Resistance range, 20 ohms to 50 K. ohms.
Helical turns 10.
Rotation, 3,600°.
Number of wire turns, 2,000 to 12,000.
Wattage, 5.

Write for full details to :—

P. X. FOX LIMITED
TOROIDAL POTENTIOMETER SPECIALISTS
HORSFORTH, YORKSHIRE, ENGLAND.
Telephone : Horsforth 2831/2. - *Telegrams :* "Toroidal, Leeds."

n.d.h.

TELE-RADIO (1943) LTD.

177, EDGWARE ROAD, PADDINGTON, W.2.

NOW IS THE TIME TO BUILD THE E.E. TELEVISION RECEIVER

	Each £ s. d.
VARLEY MAINS Transformer	4 10 0
Varley EHT 4 KV Transformer	3 7 6
Scanco 4 KV EHT Transformer	2 8 0
Scanco Scanning coils	1 5 6
Scanco Focus coils	1 10 0
Scanco Line Output Transformer	1 5 6
Vortexion Mains Transformer	2 19 6
Vortexion 4 KV EHT Transformer	2 10 0
Walpole Norman Line Output Transformer	1 16 0
Walpole Norman Focus coil	1 16 0
Haynes Focus coil	1 16 0
Haynes R.F. Oscillator. Unit totally screened EHT as required—5-8 KV	5 8 0
Complete set of coils with heater chokes, etc.	15 0
Non Magnetic bracket for focus coil, etc. (made from duralumin)	13 6
CATHODE RAY TUBES	
15 in. EMI type 3/6ASZ	18 18 0
Scanning coil for above	3 3 0
Focus coil for above	1 16 0
Line output transformer for above	1 13 6
C.R. Tube socket	6 6
12 in. Mazda CRM121	15 2 5
12 in. Ferranti (flat face)	15 2 5
9 in. G.E.C. 6501	11 6 9
9 in. Mazda CRM92	11 6 9
All specified Resistors for Sound receiver, including VC	14 6
All specified Resistors for Vision receiver including Contrast Con.	1 2 10

	£ s. d.
All specified Resistors for Time Base, etc.	17 10
All specified Resistors for Power Pack and Sound Output	17 5
All specified Capacitors for Sound Receiver	1 18 3
All specified Capacitors for Vision Receiver	2 10 0
All specified Capacitors for Time Base	2 18 7
All specified Capacitors for Power Pack	2 10 8
Colvern W.W. Pot. 10K each	5 6
,, ,, ,, 100K each	6 7
,, ,, ,, 2K each	5 6
Valves (10) ex WD EF50 (tested) each	5 0
,, (2) ex WD EA50 each	5 0
,, (1) EBC33 Mullard each	11 7
,, (2) T41 Mazda each	12 10
,, (1) Pen 46 Mazda each	18 3
,, (1) Pen 45 Mazda each	12 10
,, (1) HVR2A Mullard each	1 4 4
,, (1) UU8 Mazda each	18 3
,, (1) EL33 Mullard each	12 10
Complete chassis assembly with all large holes already punched	2 17 6
Complete chassis assembly with all valve holders and sockets fitted	4 13 6

Send for complete price list of all components
Also (1949) Catalogue **9d.** post free.
When ordering please include sufficient for postage and packing.
Shop Hours : Monday-Saturday, 9 a.m. to 5.30 p.m.
Thursday, 9 a.m. to 1 p.m.

'Phone : AMB 5393
PAD 6116
PAD 5606

The type JCF/200 unit illustrated above is representative of the wide range of vacuum type unit available for low and medium frequencies.

FOR FREQUENCY SUB-STANDARDS

Type JCF/200, 100 KC/S

Available from stock adjusted to ± 0·01%. Higher accuracies supplied to special order.

FEATURES

Low temperature co-efficient — less than 2 in 10^6 per °C.

Patented nodal suspension.

Mounted in vacuum: performance independent of climatic conditions.

Exceptionally high Q value.

High stability.

Small size, 3" × ⅞" overall excluding pins.

Fits standard miniature deaf aid valve socket.

Price £2-15-0

SALFORD ELECTRICAL INSTRUMENTS LTD.

PEEL WORKS, SALFORD 3, LANCS. *Telephone BLAckfriars 6688 (6 lines)* *Telegrams and Cables SPARKLESS Manchester*

Proprietors: THE GENERAL ELECTRIC Co. Ltd., of England

Maximum sensitivity with uniform frequency response from a more compact speaker, appreciably reduced in weight—that is what Rola technicians have achieved with the new G.12. Special features include dust-proof suspension completely protecting coil and magnet gap and the powerful Alcomax II magnet. Write for details and also for particulars of Rola 3" and 4" P.M. models, dust-proofed and equipped with Alcomax II magnets.

best of the BIG speakers

BRITISH ROLA LTD., FERRY WORKS, SUMMER RD., THAMES DITTON, SURREY

Telephone: EMBerbrook 3402 (5 lines)

TELCON'S LATEST MAGNETIC DEVELOPMENT

H.C.R. ALLOY

is now available in commercial quantities

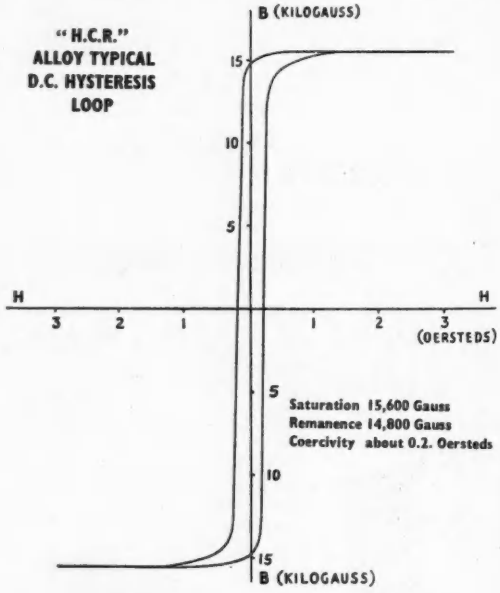

The magnetic properties of this alloy make it suitable for mechanical rectifiers, magnetic amplifiers and special forms of reactors.

Founded TELCON 1864

Full technical details on request from

THE TELEGRAPH CONSTRUCTION & MAINTENANCE CO. LTD.
Founded 1864
Head Office: 22 OLD BROAD ST., LONDON, E.C.2. Tel: LONdon Wall 3141
Enquiries to TELCON WORKS, GREENWICH, S.E.10. Tel: Greenwich 3291

100 Kc/s - 100 Mc/s

HF OSCILLATOR UNIT - HO7 - 100

COMPLETE — FOR IMMEDIATE INCORPORATION IN A SIGNAL GENERATOR — CIRCUIT COMPLETE INSTRUMENT SUPPLIED WITH UNIT

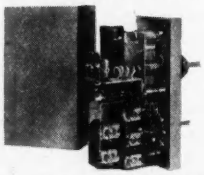

59/6 LESS 6J5 VALVE

LARGE DIRECTLY CALIBRATED SCALE - 9" × 5". TOTAL LENGTH - 50" - ACCURACY - 1% AND ALL OTHER PARTS AVAILABLE.

R. E. D. Co., MORETONHAMPSTEAD, DEVON

the 'TOPS' in TELEVISION
Aerialite Television Aerials are being installed as fast as they can be produced. Of good technical design, robust construction, and easy to get, every Aerialite aerial will give clear, sharp, steady pictures, with never a "ghost." Send for illustrated booklet giving full details.
Sell
AERIALITE
TELEVISION AERIALS
and EQUIPMENT
for the Pictures at Home

Made by: AERIALITE LTD. STALYBRIDGE, CHESHIRE

AMBITIOUS ENGINEERS

HAVE YOU HAD *YOUR* COPY OF "ENGINEERING OPPORTUNITIES"?

Whatever your age or experience—you must read this highly informative guide to the best paid engineering posts. The handbook contains particulars of A.M.I.C.E., A.M.I.Mech.E., A.M.I.E.E., A.M.I.M.I., A.M.Brit.I.R.E., and other important Engineering Examinations, and outlines home-study courses in all branches of Civil, Mechanical, Electrical, Automobile, Radio and Aeronautical Engineering, Government Employment, Draughtsmanship, Building and Plastics, Matriculation, etc.

We Guarantee

"NO PASS — NO FEE"

If you are earning less than £10 a week you cannot afford to miss reading "Engineering Opportunities." It tells you everything you want to know to secure your future. Write for this enlightening guide to well paid posts NOW—FREE and without obligation.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY
337a, Shakespeare House, 17 18 Stratford Place, London, W.1.

BIET

SURELY TESTED

with the

MICOVAC

ELECTRONIC TESTMETER

22 RANGES
VOLTS
D.C., A.C., R.F.
CURRENT
From few micro-amps to 1.5 Amps. D.C.
RESISTANCES
Up to 100 MΩ

A versatile valve voltmeter for laboratory or test bench. Being battery operated, it is instantly ready for use. Probe for V.H.F. measurements.

ELECTRONIC INSTRUMENTS LTD
17 PARADISE ROAD • RICHMOND • SURREY

The Greatest **Advance** *yet!*
100 Kc/s to 100 Mc/s
ON FUNDAMENTALS

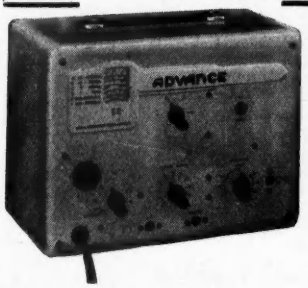

Range: 100 Kc/s.—100 Mc/s. *in 6 bands.*
Frequency: *Guaranteed within* ±1%.
Output: *Approx. volt unattenuated and variable from 1 μV to 100 mV into a 75 ohm load through a matched transmission line.*
Stray Field: *Less than 3μV at 100 Mc/s.*
Illuminated Dial: *Total scale length,* 30 in.
Power Supply: 110 — 210 — 230 — 250 volts. 40-100 c/s.
Dimension: 9½ *in. high* × 13 *in. wide* × 8 *in. deep.*
Weight: 15 *lb.*

The new Advance Signal Generator, Type E.2, has all the advantages of the popular Model 1 plus a greatly extended range to cover the Birmingham Television frequencies. The wider range, 100 Kc/s. to 100 Mc/s., gives greater scope for advanced experimental work than ever before.

In common with the earlier model, the new generator offers an instrument of laboratory standard at a price within the reach of moderate purses. The remarkable high frequency accuracy of ±1% extends over the whole range.

end for fully descriptive leaflet.

Advance TYPE E2 SIGNAL GENERATOR

ADVANCE COMPONENTS LTD.,
Back Road, Shernhall Street, Walthamstow, London, E.17
Tel.: LARkswood 4366/7/8

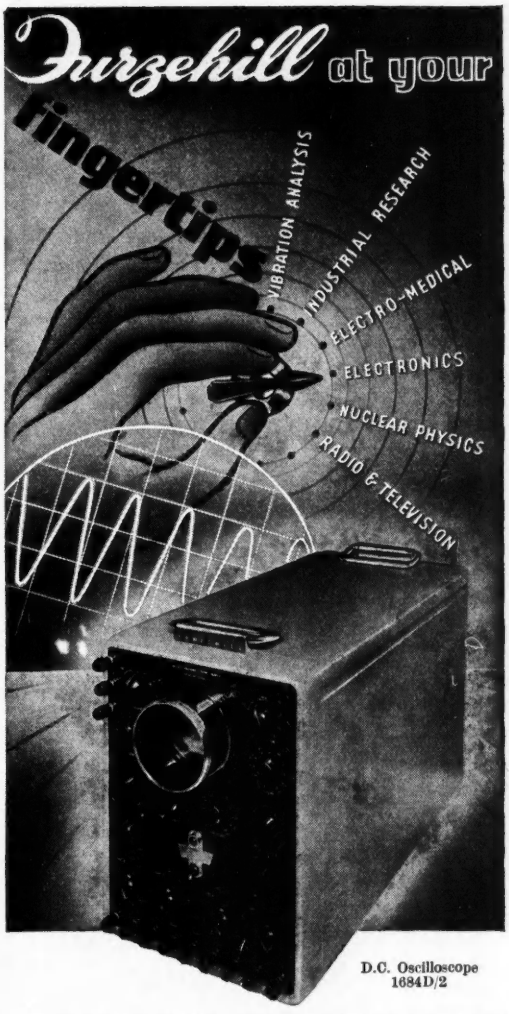

D.C. Oscilloscope 1684D/2

AN EXAMPLE from the Furzehill range of fine instruments is this high-grade oscilloscope for industrial radio and television applications. Both axes have identical d.c. coupled high sensitivity amplifiers with symmetrical inputs and a level frequency characteristic from Zero to 3 Mc/s. Particularly valuable features are the instantaneous action of the shift controls, expansion of the time-base scan from ½ to 5 screen diameters, negligible phase shift in the amplifiers and automatic amplitude-limited synchronisation.

For full details of this, and other instruments in the Furzehill range, write for our new illustrated catalogue.

Furzehill

FURZEHILL LABORATORIES LTD.,
BOREHAM WOOD, HERTS. ELStree 1137

THIS IS REOSOUND REG. TRADE MARK

19" PANEL RACKS: Four Poster Construction, 12" deep.
3½" panel space £2 10 0
5' 3" panel space £3 10 0
Drilled and tapped O.B.A. Finished in black.

CHASSIS:

	s.	d.		s.	d.
17" × 6" × 2½" 18G. Steel	7	0	16G. Aluminium	8	0
17" × 8" × 2½" ,,	8	0	,,	9	3
17" × 10" × 2½" ,,	9	6	,,	10	6
17" × 12" × 2½" ,,	11	0	,,	12	0

TELEVISION CHASSIS: In tinned steel to order.
ANGLE BRACKETS: Steel from 2s. 6d. pair. Aluminium from 2s. 9d. pair.
19" RACK PANELS: Sizes from 1¾"—12¼" 14G. Steel, 2s. 9d. to 8s. 9d. Sizes from 1¾" × 12¼" 16G. Aluminium, 3s. to 9s. 9d. With turned long edges to give additional strength.
STANDARD FINISHES: Steel in Black and Grey Stoved Enamel. Aluminium self-coloured. Black and coloured Wrinkle Enamels to order.
SMALL INSTRUMENT CASES: 18 Gauge Mild Steel Box with 16 Gauge Aluminium Front Panel secured by four screws. Finished in Black Wrinkle Enamel. 6" × 4" × 4"—8s. 6d. 8" × 6" × 4", 10s. 6d. 12" × 8" × 4", 12s. 6d.
CARRIAGE: Paid on Orders over £2.
DELIVERY: The above ex stock. Quick delivery can be made of special products to specification.

REOSOUND ENGINEERING AND ELECTRICAL COMPANY,
"Reosound Works," Coleshill Road, SUTTON COLDFIELD.
Tel.-SUT. 4685 Grams-Reosound SUTTON COLDFIELD.

RELAYS AND SWITCH KEYS
LARGE EX-GOVT. STOCKS IMMEDIATE DELIVERY
Relays: Types P.O. 600 and 3000. – Also High Speed

LIGHT WEIGHT HAND SET
FOUR WAY CORD
ROTARY SELECTOR SWITCHES
CARBON HAND MICROPHONES
TELEPHONE PLUGS - JACKS - CORDS

JACK DAVIS
Dept. E.E.
30 PERCY STREET, LONDON, W.1
Telephone: MUSeum 7960

LAMINATIONS
FOR
ALL RADIO AND ELECTRICAL USES.
IN SILICON, DYNAMO, INTERMEDIATE AND TRANSFORMER QUALITIES.
PERMALLOY, MUMETAL, RADIOMETAL.
SCREENS FOR ALL ELECTRICAL USES.
TRANSFORMER SHROUDS FOR 35 AND 74 LAMS.
GENERAL PRECISION ENGINEERS.
SHERARDISING TO THE TRADE.
ELECTRICAL SOUND & TELEVISION PATENTS LTD.
12 PEMBROKE STREET, LONDON, N.1. — TERminus 4355
2/4 MANOR WAY, BOREHAM WOOD, HERTS. – ELStree 2138

AN ADVANCE IN MEASUREMENT!
CALIBRATED WIDE RANGE cathode ray oscilloscope with simple controls and large screen, combined with the measuring facilities of a valve voltmeter.

THE NAGARD
UNIT CONSTRUCTION in one case provides alternative time bases or amplifiers and improvements at minimum cost. Adequate power supply for all requirements in separate easily portable case.

TYPE 103
STANDARD UNITS include :—D.C. AMPLIFIER of high sensitivity—less than 1 mV per cm. with linear response 0-2.5 Mc/s. TIME BASE with calibrated velocity from 10 c/s to 1 Mc/s, automatic synchronisation and free from effects of mains variations.

OSCILLOSCOPE & OSCILLOMETER
INPUT SIGNAL VOLTAGES measurable by directly calibrated Y shift control, independently of amplifier gain.
THE ONLY PORTABLE instrument combining all the above for the purposes of enabling you to
SEE WHAT YOU MEASURE
MEASURE WHAT YOU SEE
AT HIGH OR LOW FREQUENCIES AND D.C.

NAGARD LTD
245 Brixton Road London, S.W.9.
Phone: BRIxton 3550. Grams: Intertel, Claproad, London.

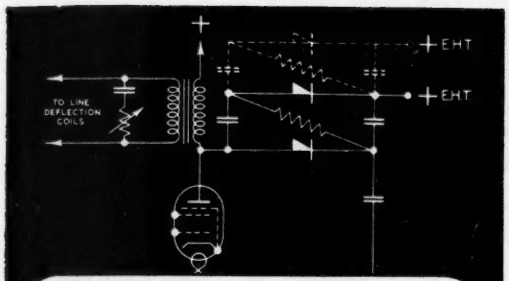

E.H.T. simplicity

E.H.T. from standard line scanning output transformers without any alteration !

Simply add three type 36EHT rectifiers in a tripler circuit. Simple . . . efficient . . . reliable . . . suitable for all sizes of tube.

Three type 36EHT35 rectifiers, each 2⅛ in. long by ⅞ in. dia., give an output of about 6KV at 100μA from a peak pulse input of approximately 2,500 V.

Write for D.S.60 to Dept. E.E.7.

WESTINGHOUSE

WESTALITE

36EHT METAL RECTIFIERS

WESTINGHOUSE BRAKE & SIGNAL CO., LTD.
82, York Way, London, N.1.

MODERN SERVICING METHOD

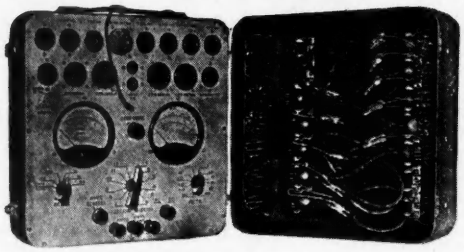

The "L.S.L." Servicing Method is a combined fault analyser and circuit tester; simultaneously capable of indicating all voltage, current and resistance on each valve electrode without removing the chassis from the cabinet. Readings can be taken whilst the set is under actual operating conditions. The "L.S.L." Analyser is a combination of multi-range instrument and valve tester.

PRICE : £18 . 18 . 0 Subject.

THE "LSL" PORTABLE ANALYSER

★ *Saves time and trouble.* ★ *Greatly increases Profit in the Service Department.* ★ *Is portable, can be used on the bench or in the home.* ★ *Is simple to operate.*

Send for further particulars from the sole distributors:

Kerry's (GREAT BRITAIN) *Limited*

WARTON ROAD, STRATFORD, LONDON, E.15,
Telephone: Maryland 6611 *AND BRANCHES*
Export Address: 23-26 St. DUNSTANS HILL E.C.3

TELCON

TELEVISION AERIAL DOWNLEADS

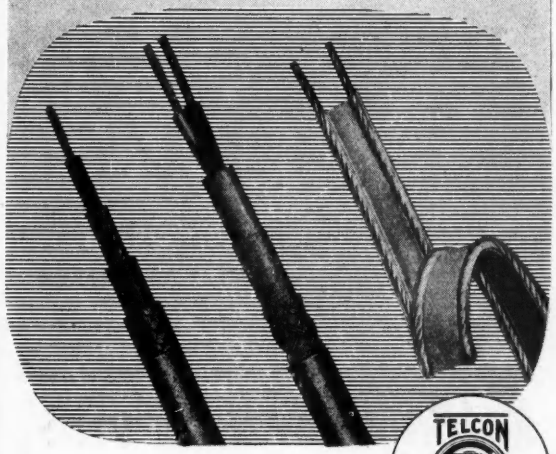

TELCON YOUR GUARANTEE

ALL TELCON CABLES are scientifically *designed*. EVERY COIL is TESTED to ensure that the Impedance and Attenuation characteristics are uniformly maintained within close limits. This background of technical knowledge and care in manufacture is a *guarantee* that Aerial Installations using TELCON TELEVISION CABLES are a source of *maximum signal* and *satisfaction*. There is a TELCON CABLE designed for every Receiver and for all reception areas—PT1M Co-axial for high signal strength and AS 60M Co-axial for "fringe" areas are two examples.

The TELEGRAPH CONSTRUCTION & MAINTENANCE Co. Ltd

Founded 1864

Head Office : 22 OLD BROAD ST., LONDON, E.C.2
Telephone : LONdon Wall 3141
Enquiries to: TELCON WORKS, GREENWICH, S.E.10
Telephone : GREenwich 3291

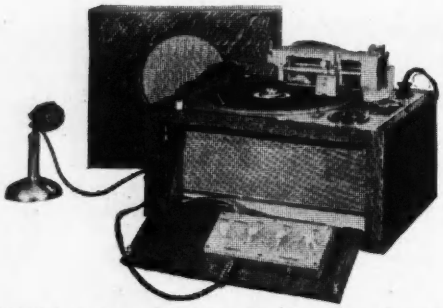

BROWN - E.R.D. 13 inch Portable Disc Recorder

An important S. G. Brown product

Brown - E.R.D.

DISC RECORDER

Incorporating the latest advances in Sound-on-Disc Recording

Write for interesting brochures presenting full technical details of this latest development in Sound-on-Disc recording. Also 17 inch models for the Professional user.

S. G. BROWN, LTD., *Shakespeare St.,* **WATFORD**

Established in Electro Acoustics and high precision Engineering for over 40 years. Manufacturers of the world-famous 'BROWN' Gyro Compass.

Telephone: WATFORD 7241.

"UNO"

PEN STENCILS

ASK West's advice on:

Drawing Office Equipment

Sensitized Papers

Blue Prints and Dye Line Prints

True-to-scale Prints

Surveying Equipment

We can help you from start to finish

A. WEST & PARTNERS LTD.

36 BROADWAY, WESTMINSTER, S.W.1

Portable Test Sets

Robust moving iron Instruments. Suitable for the Electrical Contractor or Automobile Electrical Engineer.

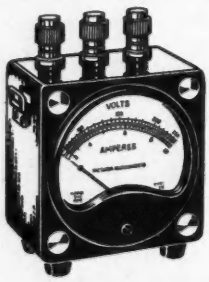

Size: 3¼" × 3¼" × 2½" overall. Complete with carrying strap.

Write for illustrated folder and price list of complete range

These combined instruments are made in many standard ranges. Combination examples:

260 V A.C. or D.C.
15 A A.C. or D.C.

25 V A.C. or D.C.
25 A A.C. or D.C.

Other combinations to order

Victoria Instruments are made uncommonly well

VICTORIA INSTRUMENTS
Prop. V.I.C. (Bournemouth) Ltd.
MIDLAND TERRACE · LONDON · N.W.10

Telephone: ELGAR 7871/2

THE "FLUXITE QUINS" AT WORK

"Come on m'lads!
On your toes!
This aerial's fixed.
Up she goes!
Thank FLUXITE, old clown,
It'll never fall down".
Bawled OI "I shall!
On my nose".

For all SOLDERING work—you need FLUXITE—the paste flux—with which even dirty metals are soldered and "tinned." For the jointing of lead—without solder and the "running" of white metal bearings—without "tinning" the bearing.

It is suitable for ALL METALS—excepting ALUMINIUM—and can be used with safety on ELECTRICAL and other sensitive apparatus.

With Fluxite Joints can be "wiped" successfully, that are impossible by any other method

Used for over 40 years in Government Works, and by leading Engineers and Manufacturers. OF ALL IRONMONGERS—IN TINS—10d., 1/6 and 3/-.

The "Fluxite Gun" puts Fluxite where you want it by a simple pressure. Price 2/6, or filled 3/6.

ALL MECHANICS WILL HAVE

FLUXITE

IT SIMPLIFIES ALL SOLDERING

Write for Leaflets on CASE HARDENING STEEL and TEMPERING TOOLS with FLUXITE also on "WIPED JOINTS." Price 1d. each.

FLUXITE LTD. (Dept. T.V.) Bermondsey St., London, S.E.1

Costs less to maintain!

Because —

Made principally of steel

Steel - preserving electrolyte

Fully enclosed active materials

Practically free from self-discharge

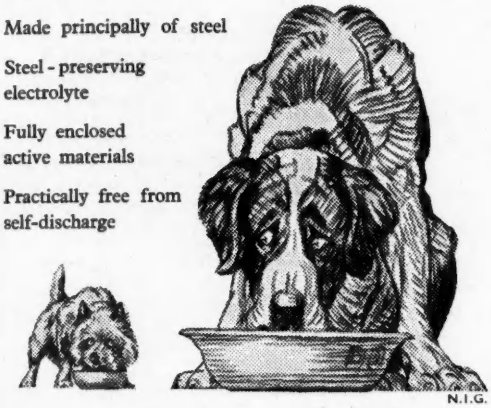

N.I.G.

NIFE **STEEL BATTERIES**

(N.B. Nife Batteries are not yet available for private cars or domestic radio)

NIFE BATTERIES · REDDITCH · WORCESTERSHIRE

Only with CO-AX R.F. CABLES

AIR-SPACED ARTICULATED

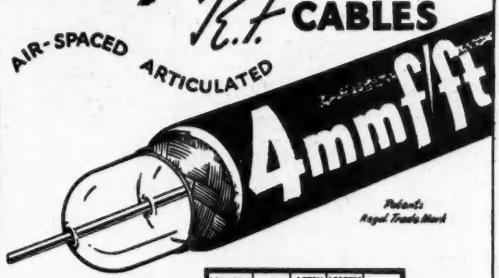

THE LOWEST EVER CAPACITANCE OR ATTENUATION

IMMEDIATE DELIVERIES FOR HOME & EXPORT

Write or cable for data sheets or deliveries to the Engineers of Nearest our spaced H.T. Cables.

TRANSRADIO LTD
CONTRACTORS TO H.M. GOVERNMENT
138A CROMWELL ROAD LONDON SW7
TRANSRAD LONDON

LOW ATTEN. TYPES.	IMPED. OHMS	ATTEN. DECIBELS per 100 ft. at 100 Mc/s.	LOADING Mc.	O.D."	
A 1	74	1.7	0.11	0.36	
A 2	74	1.3	0.26	0.44	
A34	73	0.6	1.5	0.88	HIGH POWER FLEXIBLE
LOW CAPAC. TYPES.	**CAPAC. mmf/ft**	**IMPED. OHMS**	**ATTEN. DECIBELS per 100 ft. at 100 Mc/s.**	**O.D."**	
C 1	7.3	150	2.5	0.36	
P.C.1	10.2	132	3.1	0.36	PHOTOCELL CABLE
C 11	6.3	173	3.2	0.36	
C 2	6.3	171	2.15	0.44	
C22	5.5	184	2.8	0.44	
C 3	5.4	197	1.9	0.64	
C33	4.8	220	2.4	0.64	VERY LOW CAPACITANCE
C44	4.1	252	2.1	1.03	

CONSISTENTLY *Accurate*

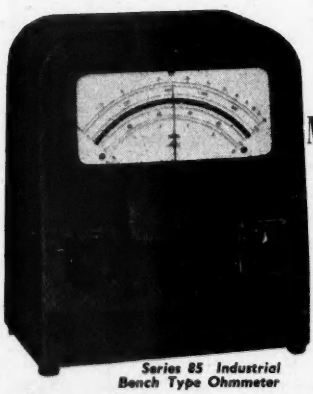

Series 85 Industrial Bench Type Ohmmeter

PULLIN

INDUSTRIAL MEASUREMENT

A Linear Scale Bridge-type Ohmmeter, with press key, designed for routine production testing of all resistive components. For battery or A.C. mains operation. (A.C. mains operated instruments are compensated for voltage variations up to — 15%.) Designed and constructed to withstand severe industrial use. Available as single or multi-range.

Address all enquiries to

MEASURING INSTRUMENTS (PULLIN) LTD
Electrin Works, Winchester St, London, W.3
Telephone: ACOrn 4651/3 & 4995

MIP

SOLONS FOR YOUR SOLDERING JOBS!

Types available:
65 watt oval tapered bit.
65 watt round pencil bit.
125 watt oval tapered bit.
125 watt round pencil bit.
240 watt oval tapered bit.

These five models will satisfy practically every soldering demand whether for the occasional household job or continuous soldering under workshop or factory conditions. With the Solon the heat is in the bit itself . . . continuously . . . hour after hour; all connections housed at end of handle away from heat. Each model complete with 6 feet Henley 3-core flexible. Now available from stock. Write for folder Y.10.

W. T. HENLEY'S TELEGRAPH WORKS CO. LTD.
51-53 Hatton Garden, London, E.C. 1

OF INTEREST TO

NORTHERN READERS

Messrs.

Cinema-Television
Electronic Instruments
Baldwin Instruments
Furzehill Laboratories
Airmec Laboratories
Evans Electroselenium
Wayne Kerr Laboratories

are now represented for demonstration, supplies and services by

F. C. ROBINSON & PARTNERS, LTD.

Equipment Division
308, DEANSGATE, MANCHESTER, 3.
Showrooms and Service
BLAckfriars 1550.

Electronic ACCESSORIES & COMPONENTS

HH

For Research Depts., Laboratories, Colleges, etc. *Send for List.*

HOLIDAY & HEMMERDINGER LTD
74-78, HARDMAN ST., DEANSGATE
MANCHESTER 3 TEL. DEA. 4121-2

Electronics in the Factory

Edited by Professor H. F. Trewman, M.A. (Cantab.), M.I.Mech.E., M.Brit.I.R.E., Principal and Managing Director, E.M.I. Institutes, Ltd. This is an extensive and reliable survey of the applications of electronics in modern industry, and is invaluable as a source of ideas on the subject. With numerous illustrations, 20/- net.

Pitman

Parker Street, Kingsway, London, W.C.2.

INDEX TO ADVERTISERS

Advance Components Ltd. 27
Aerialite Ltd. 26
Automatic Coil Winder & Electrical Equipment Co., Ltd. .. .. Cover i

Baldwin Instrument Co., Ltd. 18
Belling & Lee Ltd. 7
British Institute of Engineering Technology 26
British Insulated Callender's Cables Ltd. 6
British Rola Ltd. 25
British Thomson-Houston Ltd., The .. 4
Brown Ltd., S. G. 30

Chapman & Hall Ltd. 267
Cinema-Television Ltd. 8
Cleveland Art Metal Works 2
Colvern Ltd. 19

Davis, Jack 28
Dawe Instruments Ltd. 23
De La Rue & Co., Ltd., Thomas 20

Edison Swan Electric Co., Ltd., The Cover ii & 5
Electrical Sound & Television Patents Ltd. 28
Electronic Instruments Ltd. 27
Erie Resistor Ltd. .. .. .. Cover iv

Ferranti Ltd. 10
Fluxite Ltd. 30
Fox Ltd., P. X. 24
Furzehill Laboratories Ltd. 27

General Accessories Co., Ltd. 14

Henley's Telegraph Works Co., Ltd., W. T. 31
Holiday & Hemmerdinger Ltd. 32

Johnson Matthey & Co., Ltd. 17

Kerry's (Great Britain) Ltd. 29

Leland Instruments Ltd. .. .. Cover iii
Lewis & Co., Ltd., H. K. 267
Londex Ltd. 32
London Transformer Products Ltd. .. 32
Lydiate Ash Laboratories 22

Marconi Instruments Ltd. 21
Marconi's Wireless Telegraph Co., Ltd. .. 17
Measuring Instruments (Pullin) Ltd. .. 31
Modern Book Co. 266
Mond Nickel Co., Ltd., The 21
Muirhead & Co., Ltd. 9
Mullard Electronic Products Ltd. .. 16 & 20

Nagard Ltd. 28
Nife Batteries 31

Painton & Co., Ltd. .. .. .. 19 & 22
Pell Control Ltd., Oliver 32
Pitman & Sons, Ltd., Sir Isaac 32

Radio & Electronic Development Co. .. 26
RCA Photophone Ltd. 266
Reosound Engineering & Electrical Co. .. 28
Robinson & Partners Ltd., F. C. 32

Salford Electrical Instruments Ltd. .. 25
Southern Instruments Ltd. 18
Steatite & Porcelain Products Ltd. .. 12
Sullivan Ltd., H. W. 23
Sunvic Controls Ltd. 11

Telegraph Construction & Maintenance Co., Ltd. The .. .. 26 & 29
Tele-Radio (1943) Ltd. 24
Transradio Ltd. 31
Tufnol Ltd. 3

University Radio Ltd. 32

Victoria Instruments 30
Vortexion Ltd. 13

Walpole Norman Engineering Co., Ltd. .. 2
Walter Instruments Ltd. 15
West & Partners Ltd., A. 30
Westinghouse Brake & Signal Co., Ltd. .. 29

L.T.P. REWIND SERVICE

All rewinds are Layer Wound, Vacuum Impregnated, Pressure tested at 2,000 volts and guaranteed for three months. 48 hour service.

Enquiries:

London Transformer Products Ltd.
L.T.P. Works, Cobbold Estate, Willesden, London, N.W.10

Telephone WILlesden 6486

WE OFFER

A large range of used and new Test Equipment, Converters, Recorders, Amplifiers, Motors, Transformers, etc.

All guaranteed and at very attractive prices.

We buy good modern used equipment of all types for spot cash.

UNIVERSITY RADIO LTD.
22 LISLE STREET, LONDON, W.C.2.
Tel. GER 4447 and GER 8582.

Varley

QUALITY RELIABILITY

MAINS TRANSFORMERS
A.F. TRANSFORMERS
SMOOTHING CHOKES
THERMAL DELAY SWITCHES
SLIDER RESISTANCES

Made by

OLIVER PELL CONTROL LTD
CAMBRIDGE ROW BURRAGE ROAD S.E.18
Telephone Woolwich 1422

NEW *SMALL* PROCESS TIMERS

$5\frac{1}{4}$" x 6" x $5\frac{1}{2}$"

For flush or wall mounting.

Type SRJ. Automatically Resetting Timer.

Type JPS. Hand Resetting Timer.

BOTH SYNCHRONOUS

SRJ. *Ask for Lists 120 & 121/EO*

LONDEX LTD

Manufacturers of Relays

207, ANERLEY RD., LONDON, S.E.20. SYDenham 6258-9

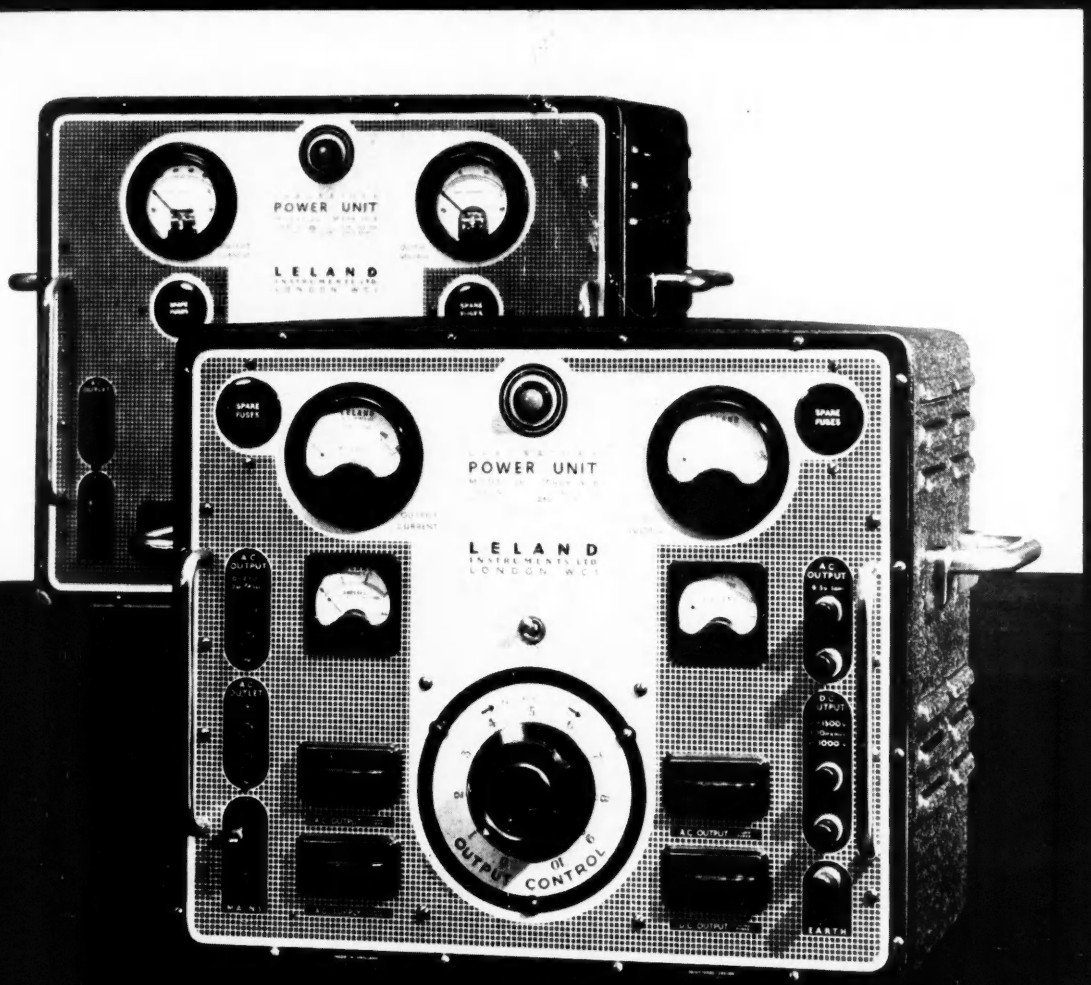

LABORATORY POWER UNITS SERIES 26

Originally designed to meet Royal Aircraft Establishment specifications this range of Power Units now includes an instrument for almost every need in the laboratory. New versions are continually being added to the range to meet special requirements.

- Output voltages continuously variable between zero and 1500 volts D.C., max. 500 watts, output smooth to .1% (Model 26 Mk III-B illustrated above, back).
- Power Supply is normally 110/230 volts A.C. but units are available for operation from D.C. mains or accumulator sources. Any type can be supplied to order on 19" panel for standard rack mounting.
- Types with input voltage stabilizers and fixed or variable output voltages up to 10,000 volts A.C. or D.C. are available, also sources of high power Radio Frequency voltages.
- Supplementary independent outputs, for example 0-270 A.C. volts 2 amps. variable, 6.3 volts. 1 amp fixed, are provided (Model 26 Mk IV-B illustrated above, front).
- You are invited to write for data sheets which give the full specification of the Models 26 Mk III-B, Mk III-C and Mk IV-B and stating your particular requirements. Technical information on other instruments is also available in the ranges of BOONTON, CLOUGH-BRENGLE, BALLANTINE, FERRIS, MERVYN and MIDGLEY-HARMER.

LELAND
INSTRUMENTS LTD.
Electronic Engineers & Consultants
TELEPHONE: CHANCERY 8765 and 8766

21 JOHN STREET • BEDFORD ROW • LONDON W.C.1

ERIE Stud Potentiometer

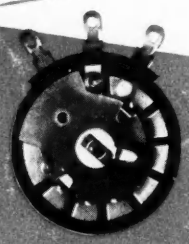

Internal View of Contacts

This neat, totally enclosed Potentiometer with its smooth movement, has many advantages over the conventional wafer switch with its often untidy array of external resistors and its stiff, jerky movement. Its few moving parts give long life and low contact resistance, and simplicity and economy in design lend themselves to rapid bulk production at very low cost.

Abridged Specification and Data

Series :	SKC 2100.
Resistor Elements :	Erie Type 58. Any standard value 10 ohms to 10 megohms. Tolerance ±20%.
Types Available :	Non-switch 9 steps; DPST switch 7 steps.
Tappings :	A tapping can be provided at any step except the 3rd and 6th.
Diameter :	1–$\frac{9}{16}$" excluding tags.
Bush :	0.375" 32 T.P.I. 0.263" 32 T.P.I.
Spindle :	With standard Erie and RECMF flats in $\frac{1}{2}$" integers up to 2$\frac{1}{2}$" maximum inclusive of bush.

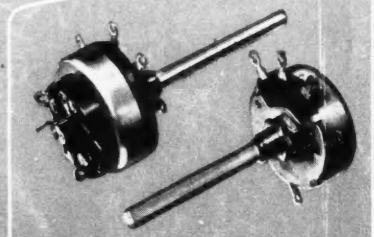

ERIE

Resistor Ltd

CARLISLE ROAD, THE HYDE.
LONDON, N.W.9, ENGLAND.

Telephone : COLindale 8011
Cables : Resistor, London.

Factories : London and Great Yarmouth Toronto, Canada ; Erie, Penna., U.S.A.

5374

Printed in Great Britain by The Press at Coombelands, Ltd., Addlestone, Surrey, for the Proprietors, Morgan Brothers (Publishers) Ltd., 28, Essex Street, Strand, W.C.2.
Registered for Transmission by Canadian Magazine Post